

Interactive Formal Verification

/ 2: Modelling Hardware

Tjark Weber
(Slides: Lawrence C Paulson)
Computer Laboratory
University of Cambridge

Basic Principles of Modelling

Basic Principles of Modelling

- Define *mathematical abstractions* of the objects of interest (systems, hardware, protocols,...).

Basic Principles of Modelling

- Define *mathematical abstractions* of the objects of interest (systems, hardware, protocols,...).
- Whenever possible, use *definitions* — not axioms!

Basic Principles of Modelling

- Define *mathematical abstractions* of the objects of interest (systems, hardware, protocols,...).
- Whenever possible, use *definitions* — not axioms!
- Ensure that the abstractions capture enough detail.
 - Unrealistic models have unrealistic properties.
 - Inconsistent models will satisfy *all* properties.

Basic Principles of Modelling

- Define *mathematical abstractions* of the objects of interest (systems, hardware, protocols,...).
- Whenever possible, use *definitions* — not axioms!
- Ensure that the abstractions capture enough detail.
 - Unrealistic models have unrealistic properties.
 - Inconsistent models will satisfy *all* properties.

All models involving the real world are *approximate*!

Hardware Verification

Hardware Verification

- Pioneered by M. J. C. Gordon and his students, using successive versions of the HOL system.

Hardware Verification

- Pioneered by M. J. C. Gordon and his students, using successive versions of the HOL system.
- Used to model substantial hardware designs, including the ARM6 processor.

Hardware Verification

- Pioneered by M. J. C. Gordon and his students, using successive versions of the HOL system.
- Used to model substantial hardware designs, including the ARM6 processor.
- Works *hierarchically* from arithmetic units and memories right down to flip-flops and transistors.


Hardware Verification

- Pioneered by M. J. C. Gordon and his students, using successive versions of the HOL system.
- Used to model substantial hardware designs, including the ARM6 processor.
- Works *hierarchically* from arithmetic units and memories right down to flip-flops and transistors.
- Crucially uses *higher-order logic*, modelling signals as boolean-valued functions over time.

Devices as Relations



A relation in a, b, c, d

 



$$g \rightarrow s = d$$

The relation describes the possible combinations of values on the ports.

Values could be bits, words, signals (functions from time to bits), etc


Relational Composition

Relational Composition

  


two devices modelled
by two formulas

Relational Composition

 


two devices modelled
by two formulas

 


the connected ports
have the *same* value


Relational Composition

 

two devices modelled
by two formulas

 

 the connected ports
have the *same* value



the connected ports
have *some* value

Specifications and Correctness

Specifications and Correctness

- The *implementation* of a device in terms of other devices can be expressed by composition.

Specifications and Correctness

- The *implementation* of a device in terms of other devices can be expressed by composition.
- The *specification* of the device's intended behaviour can be given by an abstract formula.

Specifications and Correctness

- The *implementation* of a device in terms of other devices can be expressed by composition.
- The *specification* of the device's intended behaviour can be given by an abstract formula.
- Sometimes the implementation and specification can be proved *equivalent*: $Imp \Leftrightarrow Spec$.

Specifications and Correctness


- The *implementation* of a device in terms of other devices can be expressed by composition.
- The *specification* of the device's intended behaviour can be given by an abstract formula.
- Sometimes the implementation and specification can be proved *equivalent*: $Imp \Leftrightarrow Spec$.
- The property $Imp \Rightarrow Spec$ ensures that every possible behaviour of the *Imp* is permitted by *Spec*.


Specifications and Correctness


- The *implementation* of a device in terms of other devices can be expressed by composition.
- The *specification* of the device's intended behaviour can be given by an abstract formula.
- Sometimes the implementation and specification can be proved *equivalent*: $Imp \Leftrightarrow Spec$.
- The property $Imp \Rightarrow Spec$ ensures that every possible behaviour of the *Imp* is permitted by *Spec*.


Impossible implementations satisfy all specifications!

The *Switch Model* of CMOS

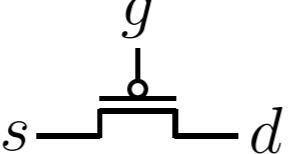

$$\text{Ptran}(g, s, d) = (\neg g \Rightarrow (d = s))$$

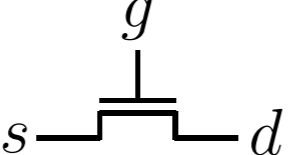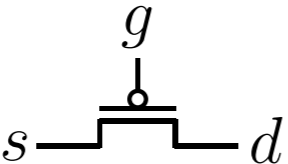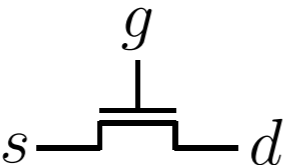

$$\text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$



$$\text{Gnd } g = (g = \mathbf{F})$$



$$\text{Pwr } p = (p = \mathbf{T})$$

The *Switch Model* of CMOS


$$\text{Ptran}(g, s, d) = (\neg g \Rightarrow (d = s))$$


$$\text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$


$$\text{Gnd } g = (g = \mathbf{F})$$


$$\text{Pwr } p = (p = \mathbf{T})$$

```
subsection{* Specification of CMOS primitives *}
```

```
text{* P and N transistors *}
```

```
definition "Ptran = ( $\lambda(g,a,b). (\sim g \longrightarrow a = b)$ )"
```


```
definition "Ntran = ( $\lambda(g,a,b). (g \longrightarrow a = b)$ )"
```

```
text{* Power and Ground*}
```

```
definition "Pwr p = (p = True)"
```


```
definition "Gnd p = (p = False)"
```


Full Adder: Specification

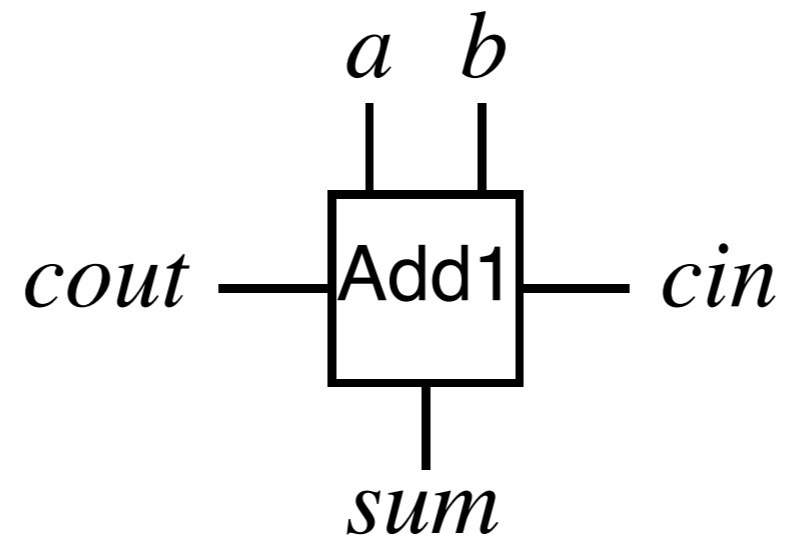

$$2 \times \text{cout} + \text{sum} = a + b + \text{cin}$$

Full Adder: Specification

 

$$2 \times \text{cout} + \text{sum} = a + b + \text{cin}$$


```
text{* 1-bit full adder specification *}
```

```
text{* Convert boolean to number (0 or 1) *}
```

```
definition bit_val :: "bool  $\Rightarrow$  nat" where  
  "bit_val p = (if p then 1 else 0)"
```

```
definition "Add1Spec = ( $\lambda$ (a,b,cin,sum,cout).  
  2*(bit_val cout) + bit_val sum =  
  bit_val a + bit_val b + bit_val cin)"
```

Full Adder: Implementation

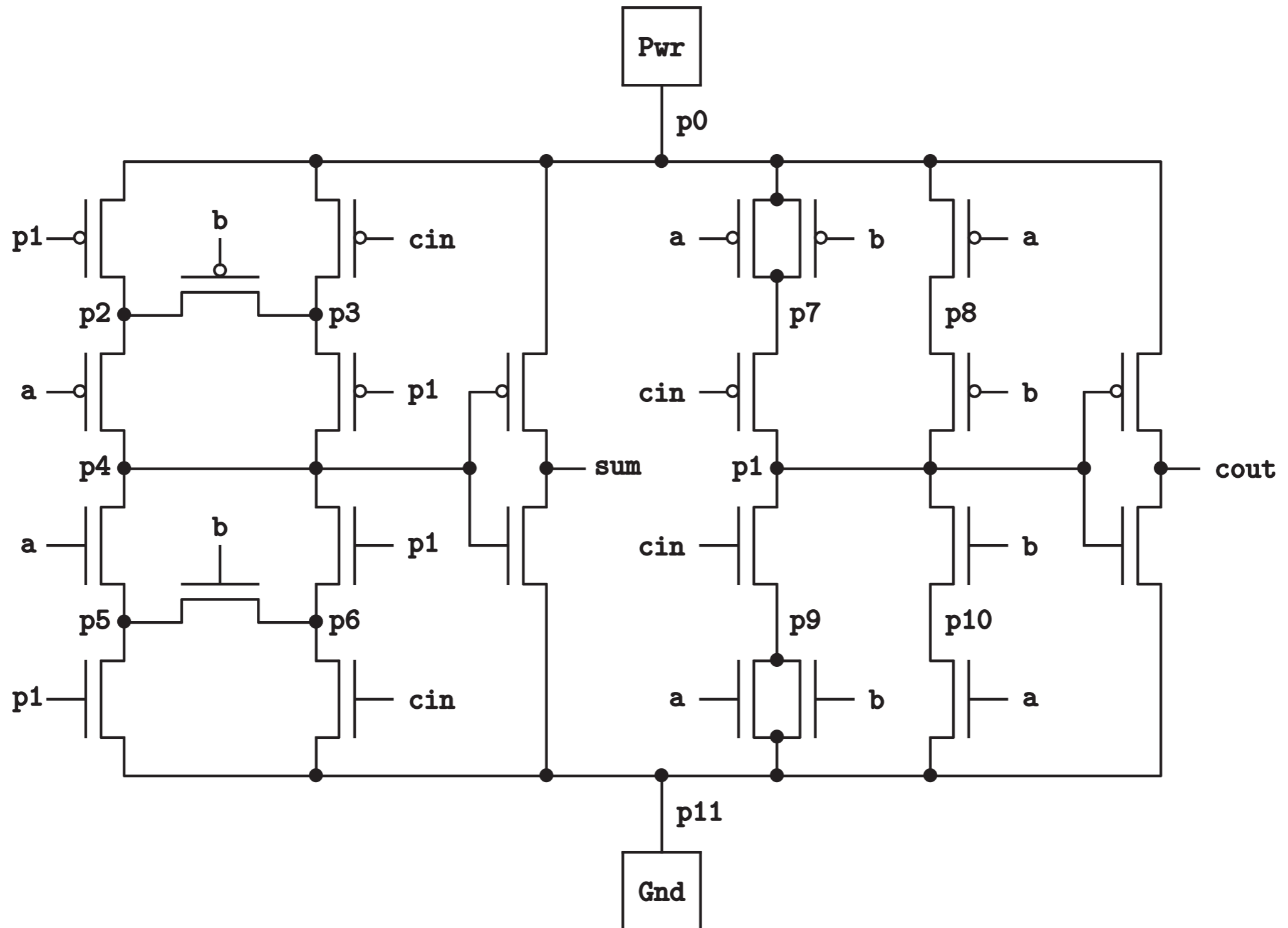

Full Adder in Isabelle

```
Adder.thy
text{* 1-bit CMOS full adder implementation *}

definition "Add1Imp = (λ(a,b,cin,sum,cout).
  ∃p0 p1 p2 p3 p4 p5 p6 p7 p8 p9 p10 p11.
    Ptran(p1,p0,p2) ^ Ptran(cin,p0,p3) ^
    Ptran(b,p2,p3) ^ Ptran(a,p2,p4) ^
    Ptran(p1,p3,p4) ^ Ntran(a,p4,p5) ^
    Ntran(p1,p4,p6) ^ Ntran(b,p5,p6) ^
    Ntran(p1,p5,p11) ^ Ntran(cin,p6,p11) ^
    Ptran(a,p0,p7) ^ Ptran(b,p0,p7) ^
    Ptran(a,p0,p8) ^ Ptran(cin,p7,p1) ^
    Ptran(b,p8,p1) ^ Ntran(cin,p1,p9) ^
    Ntran(b,p1,p10) ^ Ntran(a,p9,p11) ^
    Ntran(b,p9,p11) ^ Ntran(a,p10,p11) ^
    Pwr(p0) ^ Ptran(p4,p0,sum) ^
    Ntran(p4,sum,p11) ^ Gnd(p11) ^
    Ptran(p1,p0,cout) ^ Ntran(p1,cout,p11))"

text{* Verification of CMOS full adder *}
lemma Add1Correct:
  "Add1Imp(a,b,cin,sum,cout) = Add1Spec(a,b,cin,sum,cout)"
by (simp add: Pwr_def Gnd_def Ntran_def Ptran_def Add1Spec_def
    Add1Imp_def bit_val_def ex_bool_eq)

-u-:***- Adder.thy 27% L53 (Isar Utoks Abbrev; Scripting )-----
```

Full Adder in Isabelle

```
text{* 1-bit CMOS full adder implementation *}


definition "Add1Imp = (λ(a,b,cin,sum,cout).
  ∃p0 p1 p2 p3 p4 p5 p6 p7 p8 p9 p10 p11.
    Ptran(p1,p0,p2)    ^    Ptran(cin,p0,p3)    ^
    Ptran(b,p2,p3)     ^    Ptran(a,p2,p4)       ^
    Ptran(p1,p3,p4)    ^    Ntran(a,p4,p5)       ^
    Ntran(p1,p4,p6)    ^    Ntran(b,p5,p6)       ^
    Ntran(p1,p5,p11)   ^    Ntran(cin,p6,p11)    ^
    Ptran(a,p0,p7)     ^    Ptran(b,p0,p7)       ^
    Ptran(a,p0,p8)     ^    Ptran(cin,p7,p1)     ^
    Ptran(b,p8,p1)     ^    Ntran(cin,p1,p9)     ^
    Ntran(b,p1,p10)    ^    Ntran(a,p9,p11)     ^
    Ntran(b,p9,p11)   ^    Ntran(a,p10,p11)    ^
    Pwr(p0)            ^    Ptran(p4,p0,sum)     ^
    Ntran(p4,sum,p11) ^    Gnd(p11)             ^
    Ptran(p1,p0,cout) ^    Ntran(p1,cout,p11))"

text{* Verification of CMOS full adder *}
lemma Add1Correct:
  "Add1Imp(a,b,cin,sum,cout) = Add1Spec(a,b,cin,sum,cout)"
by (simp add: Pwr_def Gnd_def Ntran_def Ptran_def Add1Spec_def
      Add1Imp_def bit_val_def ex_bool_eq)

-u-:***- Adder.thy 27% L53 (Isar Utoks Abbrev; Scripting )-----
```


$$(\exists b. P b) = (P \text{ True} \vee P \text{ False})$$


An n -bit Ripple-Carry Adder

 

$$(2^n \times cout) + s = a + b + cin$$


An n -bit Ripple-Carry Adder

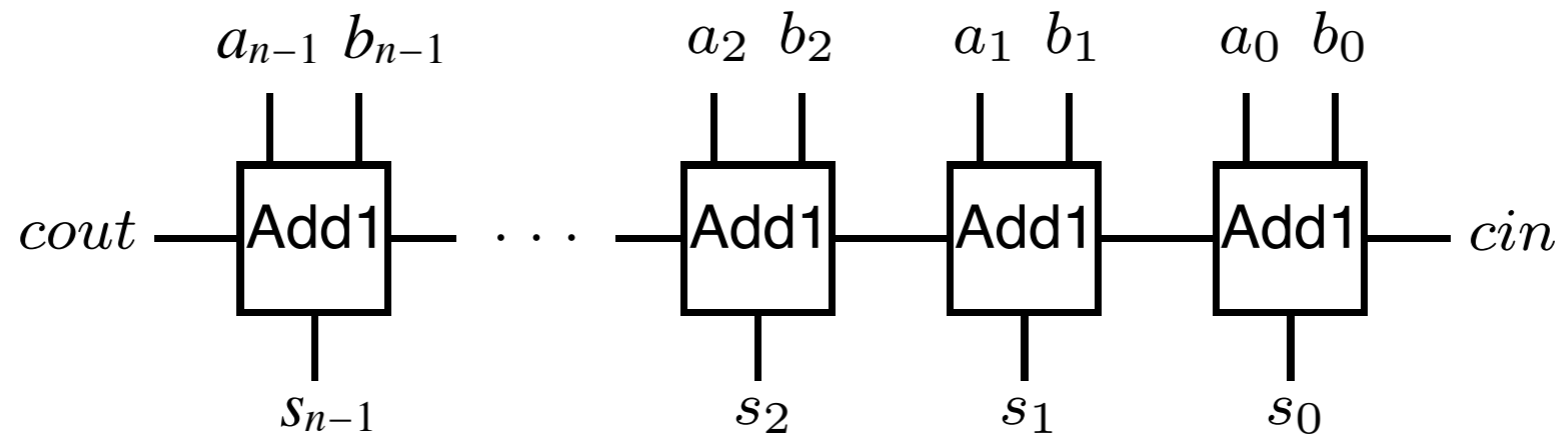

$$(2^n \times cout) + s = a + b + cin$$

- Cascading several full adders yields an n -bit adder.


An n -bit Ripple-Carry Adder

 

$$(2^n \times cout) + s = a + b + cin$$

- Cascading several full adders yields an n -bit adder.
- The implementation is expressed recursively.

An n -bit Ripple-Carry Adder

 

$$(2^n \times cout) + s = a + b + cin$$


- Cascading several full adders yields an n -bit adder.
- The implementation is expressed recursively.
- The specification is obvious mathematics.

Adder Specification

$$(2^n \times cout) + s = a + b + cin$$

Adder Specification

$$(2^n \times cout) + s = a + b + cin$$

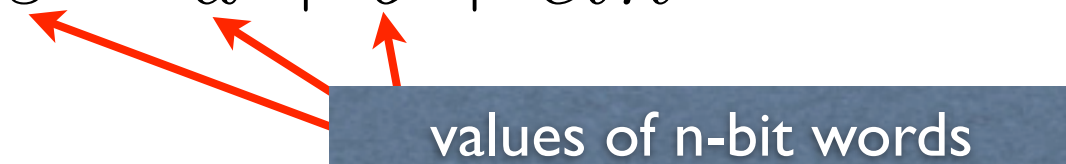

values of n-bit words

Adder Specification

$$(2^n \times cout) + s = a + b + cin$$

values of n-bit words

```
text{* Unsigned number denoted by bitstring f(n-1)...f(0) *}

fun bits_val where
  "bits_val f 0 = 0"
| "bits_val f (Suc n) = 2^n * bit_val(f n) + bits_val f n"

text{* Specification of an n-bit adder *}
□
definition
  "AdderSpec n = (λ(a, b, cin, sum, cout).
    2^n * bit_val cout + bits_val sum n =
    bits_val a n + bits_val b n + bit_val cin)"
```

Adder Specification

$$(2^n \times cout) + s = a + b + cin$$

values of n-bit words

```
text{* Unsigned number denoted by bitstring f(n-1)...f(0) *}

fun bits_val where
  "bits_val f 0 = 0"
| "bits_val f (Suc n) = 2^n * bit_val(f n) + bits_val f n"

text{* Specification of an n-bit adder *}
□
definition
  "AdderSpec n = (λ a, b, cin, sum, cout).
    2^n * bit_val cout + bits_val sum n =
    bits_val a n + bits_val b n + bit_val cin)"
```

Adder Specification

$$(2^n \times cout) + s = a + b + cin$$

values of n-bit words

```
text{* Unsigned number denoted by bitstring f(n-1)...f(0) *}

fun bits_val where
  "bits_val f 0 = 0"
| "bits_val f (Suc n) = 2^n * bit_val(f n) + bits_val f n"

text{* Specification of an n-bit adder *}
□
definition
  "AdderSpec n = (λ a, b, cin, sum, cout).
    2^n * bit_val cout + bits_val sum n =
    bits_val a n + bits_val b n + bit_val cin)"
```


Adder Specification

$$(2^n \times cout) + s = a + b + cin$$


values of n-bit words

```
text{* Unsigned number denoted by bitstring f(n-1)...f(0) *}
fun bits_val where
  "bits_val f 0 = 0"
| "bits_val f (Suc n) = 2^n * bit_val(f n) + bits_val f n"
text{* Specification of an n-bit adder *}
definition
  "AdderSpec n = ( $\lambda$ a, b, cin, sum, cout).
  2^n * bit_val cout + bits_val sum n =
  bits_val a n + bits_val b n + bit_val cin)"
```

Adder Implementation

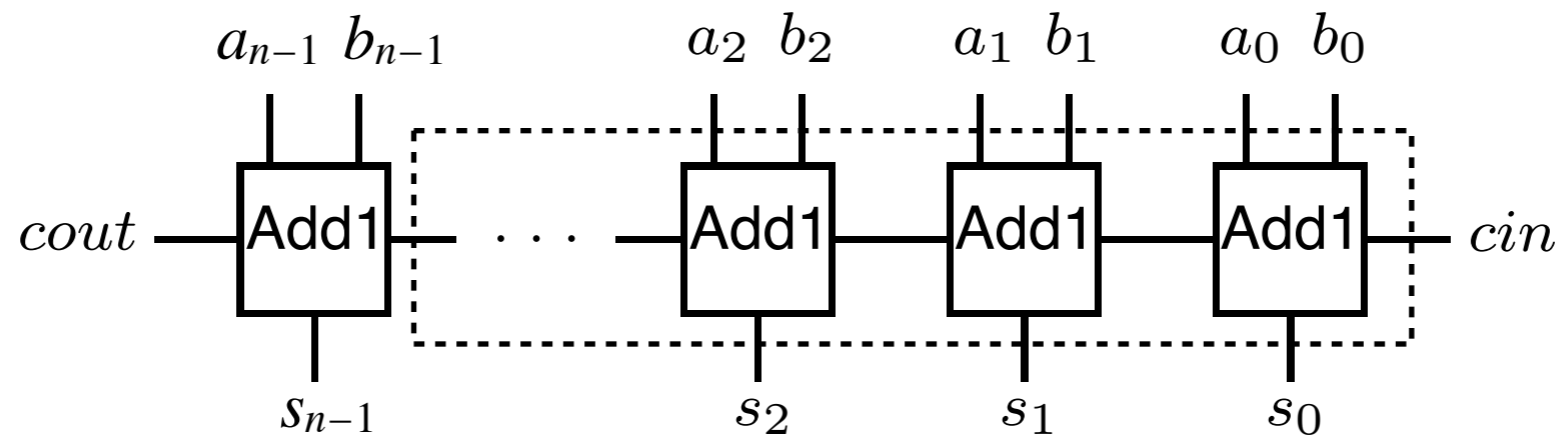

Adder Implementation

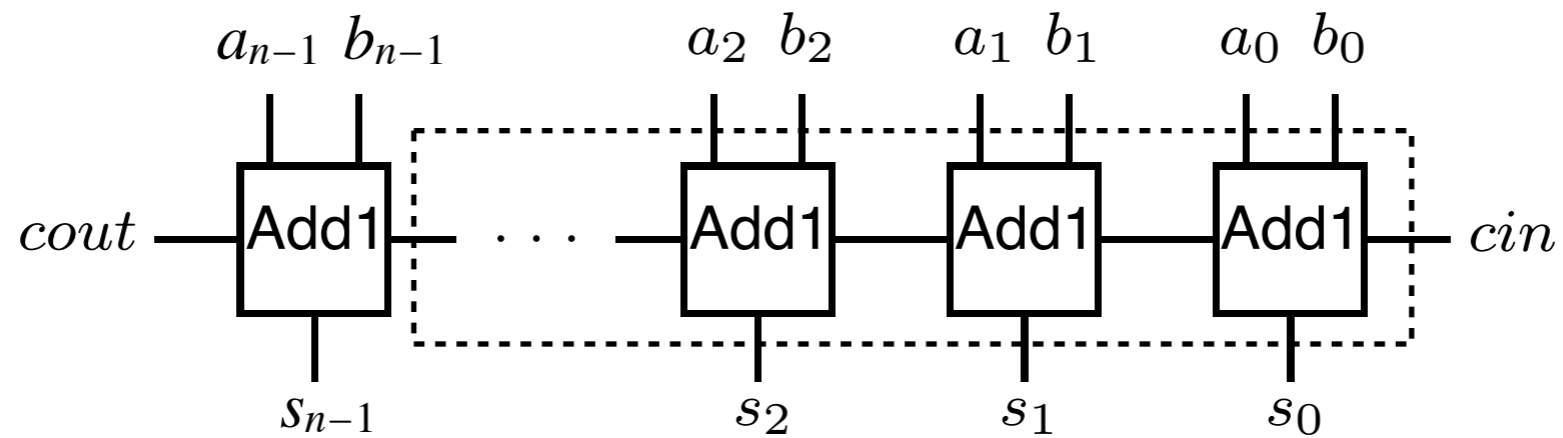


```
text{* Implementation of an n-bit ripple-carry adder*}
```

```
fun AdderImp where
```

```
  "AdderImp 0 (a, b, cin, sum, cout) = (cout = cin)"
```

```
| "AdderImp (Suc n) (a, b, cin, sum, cout) =  
  (∃c. AdderImp n (a, b, cin, sum, c) ^  
    Add1Imp (a n, b n, c, sum n, cout))"
```

Adder Implementation

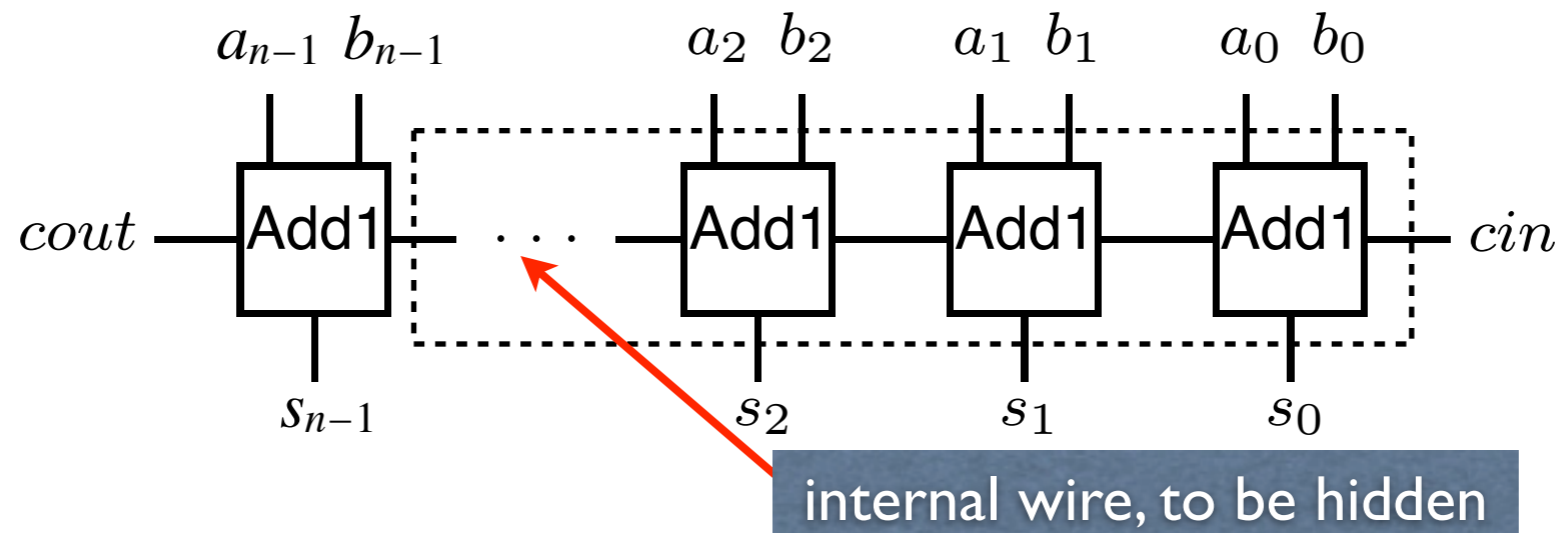


```
text{* Implementation of an n-bit ripple-carry adder*}
```

```
fun AdderImp where
```

```
  "AdderImp 0 (a, b, cin, sum, cout) = (cout = cin)"
```

```
  | "AdderImp (Suc n) (a, b, cin, sum, cout) =  
    (∃c. AdderImp n (a, b, cin, sum, c) ^  
      Add1Imp (a n, b n, c, sum n, cout))"
```


Adder Implementation

 

internal wire, to be hidden

```
text{* Implementation of an n-bit ripple-carry adder*}
fun AdderImp where
  "AdderImp 0 (a, b, cin, sum, cout) = (cout = cin)"
  | "AdderImp (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderImp n (a, b, cin, sum, c) ^
     Add1Imp (a n, b n, c, sum n, cout))"
```

Adder Implementation

 

internal wire, to be hidden

```
text{* Implementation of an n-bit ripple-carry adder*}  
  
fun AdderImp where  
  "AdderImp 0 (a, b, cin, sum, cout) = (cout = cin)"  
  | "AdderImp (Suc n) (a, b, cin, sum, cout) =  
    (∃c. AdderImp n (a, b, cin, sum, c) ^  
      Add1Imp (a n, b n, c, sum n, cout))"
```

a zero-bit adder simply connects the carry lines!

Partial Correctness Proof

```

Adder.thy
[Navigation icons]

lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\implies$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
    where AddS: "AdderSpec n (a, b, cin, sum, c)"
    and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
    by (auto intro: Suc)
- u-:--- Adder.thy 53% L85 (Isar Utoks Abbrev; Scripting )-----
this:
  AdderImp n (a, b, cin, sum, ?cout)  $\implies$  AdderSpec n (a, b, cin, sum, ?cout)
  AdderImp (Suc n) (a, b, cin, sum, cout)

goal (1 subgoal):
  1.  $\bigwedge n$  cout.
     [[ $\bigwedge$ cout.
       AdderImp n (a, b, cin, sum, cout)  $\implies$ 
       AdderSpec n (a, b, cin, sum, cout);
       AdderImp (Suc n) (a, b, cin, sum, cout)]
      $\implies$  AdderSpec (Suc n) (a, b, cin, sum, cout)
- u-:%%- *goals* 5% L4 (Isar Proofstate Utoks Abbrev;)------
```

Partial Correctness Proof

```

Adder.thy
[Navigation icons]

lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\implies$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
    where AddS: "AdderSpec n (a, b, cin, sum, c)"
    and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
    by (auto intro: Suc)
- u-:--- Adder.thy 53% L85 (Isar Utoks Abbrev; Scripting )-----
this:
  AdderImp n (a, b, cin, sum, ?cout)  $\implies$  AdderSpec n (a, b, cin, sum, ?cout)
  AdderImp (Suc n) (a, b, cin, sum, cout)
goal (1 subgoal):
  1.  $\bigwedge n$  cout.
     [[ $\bigwedge$  cout.
       AdderImp n (a, b, cin, sum, cout)  $\implies$ 
       AdderSpec n (a, b, cin, sum, cout);
       AdderImp (Suc n) (a, b, cin, sum, cout)]]
      $\implies$  AdderSpec (Suc n) (a, b, cin, sum, cout)
- u-:%%- *goals* 5% L4 (Isar Proofstate Utoks Abbrev;)-

```

assumptions



Partial Correctness Proof

```

Adder.thy
[Navigation icons]


lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\implies$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
    where AddS: "AdderSpec n (a, b, cin, sum, c)"
    and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
    by (auto intro: Suc)
- u-:--- Adder.thy 53% L85 (Isar Utoks Abbrev; Scripting )-----
this:
  AdderImp n (a, b, cin, sum, ?cout)  $\implies$  AdderSpec n (a, b, cin, sum, ?cout)
  AdderImp (Suc n) (a, b, cin, sum, cout)
goal (1 subgoal):
  1.  $\bigwedge n$  cout.
    [[ $\bigwedge$  cout.
      AdderImp n (a, b, cin, sum, cout)  $\implies$ 
      AdderSpec n (a, b, cin, sum, cout);
      AdderImp (Suc n) (a, b, cin, sum, cout)]]
 $\implies$  AdderSpec (Suc n) (a, b, cin, sum, cout)
- u-:%%- *goals* 5% L4 (Isar Proofstate Utoks Abbrev;)-

```

assumptions

conclusion

Using the Induction Hypothesis

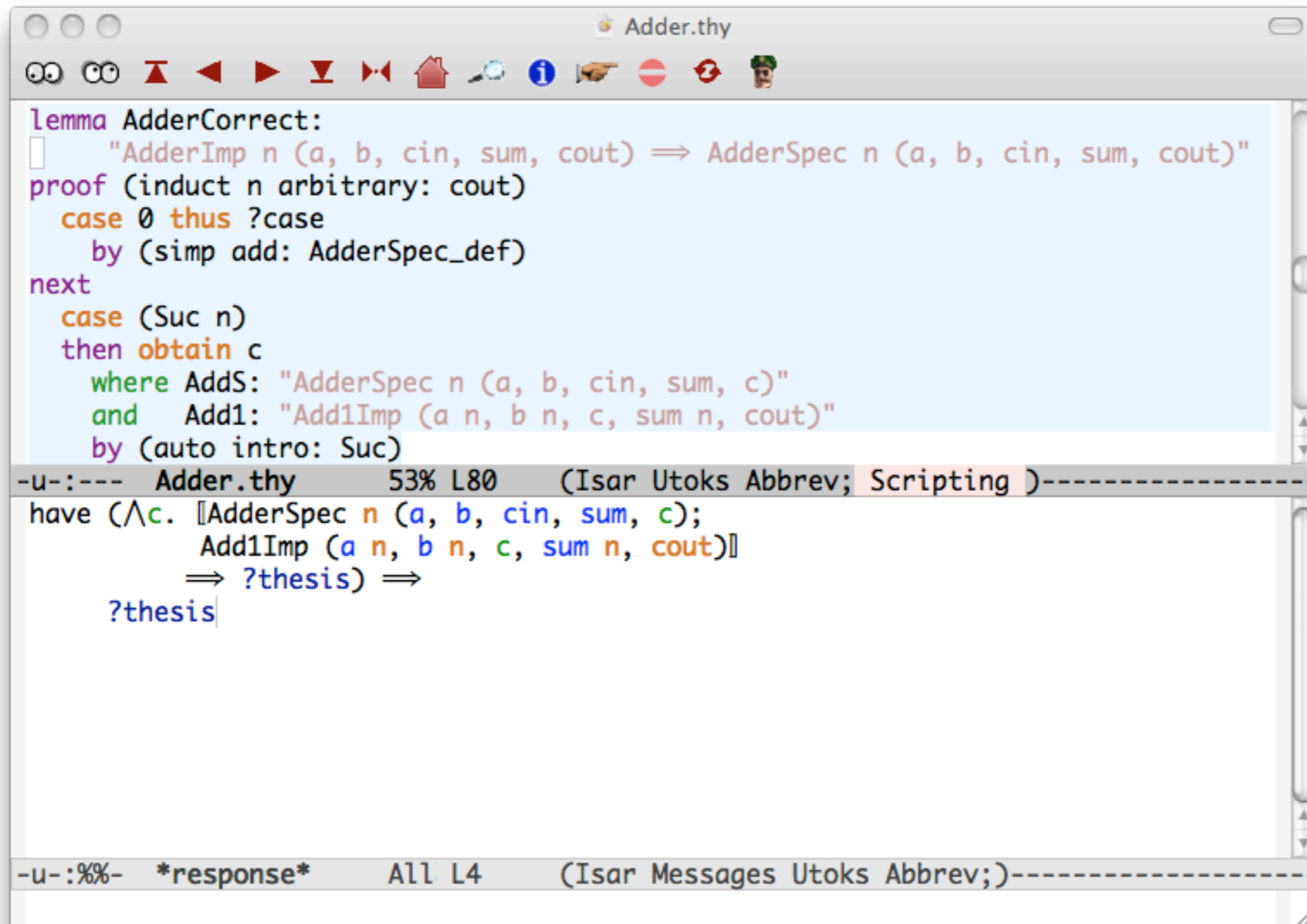

```

Adder.thy
[
  Lemma AdderCorrect:
  | "AdderImp n (a, b, cin, sum, cout)  $\Rightarrow$  AdderSpec n (a, b, cin, sum, cout)"
  proof (induct n arbitrary: cout)
    case 0 thus ?case
      by (simp add: AdderSpec_def)
    next
      case (Suc n)
      then obtain c
        where AddS: "AdderSpec n (a, b, cin, sum, c)"
        and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
        by (auto intro: Suc)
  ]
]

```

-u-:--- Adder.thy 53% L80 (Isar Utoks Abbrev; Scripting)-----


```


have ( $\wedge$ c. [AdderSpec n (a, b, cin, sum, c);
  Add1Imp (a n, b n, c, sum n, cout)]
 $\Rightarrow$  ?thesis)  $\Rightarrow$ 
  ?thesis

```

-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)-----

Using the Induction Hypothesis

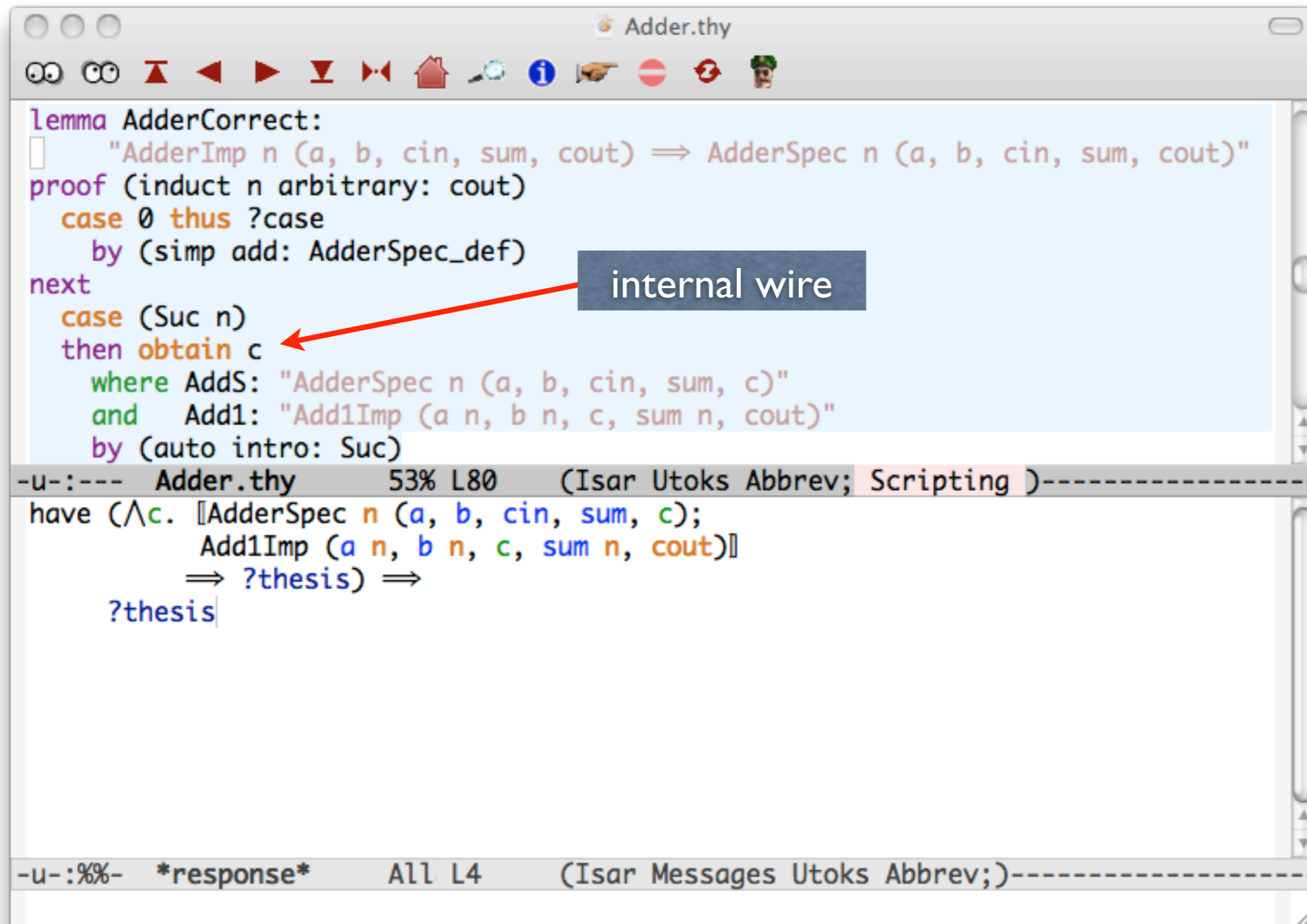

```
Lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\Rightarrow$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c 
    where AddS: "AdderSpec n (a, b, cin, sum, c)"
    and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
    by (auto intro: Suc)

```

-u-:--- Adder.thy 53% L80 (Isar Utoks Abbrev; Scripting)-----

```
have ( $\wedge$ c. [AdderSpec n (a, b, cin, sum, c);
  Add1Imp (a n, b n, c, sum n, cout)]
 $\Rightarrow$  ?thesis)  $\Rightarrow$ 
  ?thesis|

```

-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)

Using the Induction Hypothesis

```
Lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\Rightarrow$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
    where AddS: "AdderSpec n (a, b, cin, sum, c)"
    and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
    by (auto intro: Suc)
  have ( $\wedge$ c. [AdderSpec n (a, b, cin, sum, c);
    Add1Imp (a n, b n, c, sum n, cout)]
     $\Rightarrow$  ?thesis)  $\Rightarrow$ 
    ?thesis
```

-u-:--- Adder.thy 53% L80 (Isar Utoks Abbrev; Scripting)-----

-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)-----

Using the Induction Hypothesis

```
Lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\Rightarrow$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
    by (simp add: AdderSpec_def)
  next
    case (Suc n)
    then obtain c
      where AddS: "AdderSpec n (a, b, cin, sum, c)"
      and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
      by (auto intro: Suc)
    have ( $\wedge$ c. [AdderSpec n (a, b, cin, sum, c);
      Add1Imp (a n, b n, c, sum n, cout)]
       $\Rightarrow$  ?thesis)  $\Rightarrow$ 
      ?thesis
```

internal wire


holds by ind hyp

name of ind hyp

-u-:--- Adder.thy 53% L80 (Isar ... ting)-----

-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)-----

A Tiresome Calculation

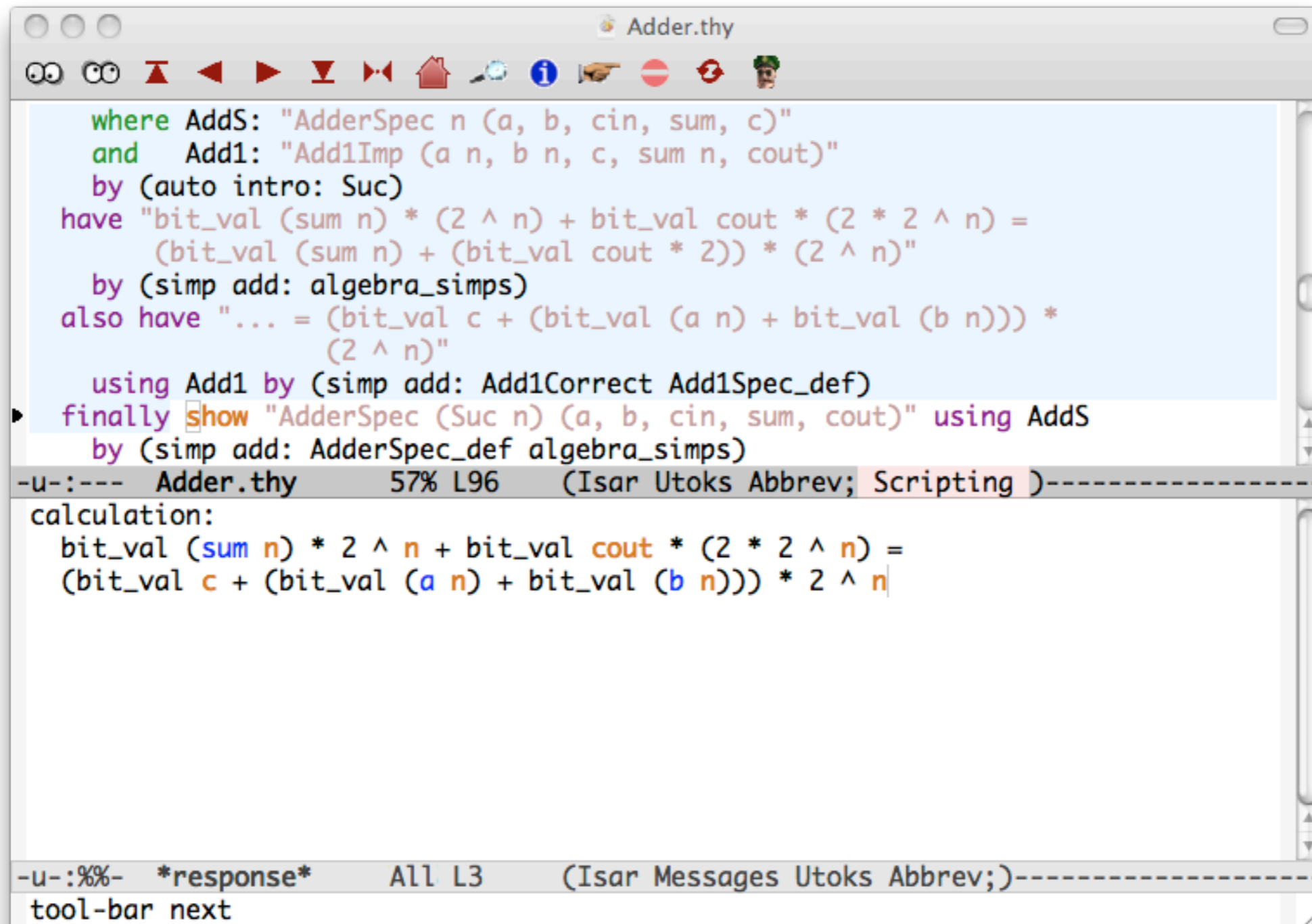

```
where AddS: "AdderSpec n (a, b, cin, sum, c)"
and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
by (auto intro: Suc)
have "bit_val (sum n) * (2 ^ n) + bit_val cout * (2 * 2 ^ n) =
      (bit_val (sum n) + (bit_val cout * 2)) * (2 ^ n)"
  by (simp add: algebra_simps)
also have "... = (bit_val c + (bit_val (a n) + bit_val (b n))) *
              (2 ^ n)"
  using Add1 by (simp add: Add1Correct Add1Spec_def)
finally show "AdderSpec (Suc n) (a, b, cin, sum, cout)" using AddS
  by (simp add: AdderSpec_def algebra_simps)
-u-:--- Adder.thy 57% L96 (Isar Utoks Abbrev; Scripting )-----
calculation:
bit_val (sum n) * 2 ^ n + bit_val cout * (2 * 2 ^ n) =
(bit_val c + (bit_val (a n) + bit_val (b n))) * 2 ^ n
-u-:%%- *response* All L3 (Isar Messages Utoks Abbrev;)-----
tool-bar next
```

A Tiresome Calculation

```
where AddS: "AdderSpec n (a, b, cin, sum, c)"
and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
by (auto intro: Suc)
have "bit_val (sum n) * (2 ^ n) + bit_val cout * (2 * 2 ^ n) =
      (bit_val (sum n) + (bit_val cout * 2)) * (2 ^ n)"
  by (simp add: algebra_simps)
also have "... = (bit_val c + (bit_val (a n) + bit_val (b n))) *
              (2 ^ n)"
  using Add1 by (simp add: Add1Correct Add1Spec_def)
finally show "AdderSpec (Suc n) (a, b, cin, sum, cout)" using AddS
  by (simp add: AdderSpec_def algebra_simps)
```

-u-:--- Adder.thy 57% L96 (Isar Utoks Abbrev; Scripting)-----

calculation:
bit_val (sum n) * 2 ^ n + bit_val cout * (2 * 2 ^ n) =
(bit_val c + (bit_val (a n) + bit_val (b n))) * 2 ^ n

-u-:%%- *response* All L3 (Isar Messages Utoks Abbrev;)-----
tool-bar next

rearranging the terms

A Tiresome Calculation

```
where AddS: "AdderSpec n (a, b, cin, sum, c)"
and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
by (auto intro: Suc)
have "bit_val (sum n) * (2 ^ n) + bit_val cout * (2 * 2 ^ n) =
      (bit_val (sum n) + (bit_val cout * 2)) * (2 ^ n)"
  by (simp add: algebra_simps)
also have "... = (bit_val c + (bit_val (a n) + bit_val (b n))) *
              (2 ^ n)"
  using Add1 by (simp add: Add1Correct Add1Spec_def)
finally show "AdderSpec (Suc n) (a, b, cin, sum, cout)" u
  by (simp add: AdderSpec_def algebra_simps)
```

-u-:--- Adder.thy 57% L96 (Isar Utoks Abbrev; Scripting)-----


calculation:
bit_val (sum n) * 2 ^ n + bit_val cout * (2 * 2 ^ n) =
(bit_val c + (bit_val (a n) + bit_val (b n))) * 2 ^ n

-u-:%%- *response* All L3 (Isar Messages Utoks Abbrev;)-----
tool-bar next

rearranging the terms

replacing outputs by inputs

The Finished Proof

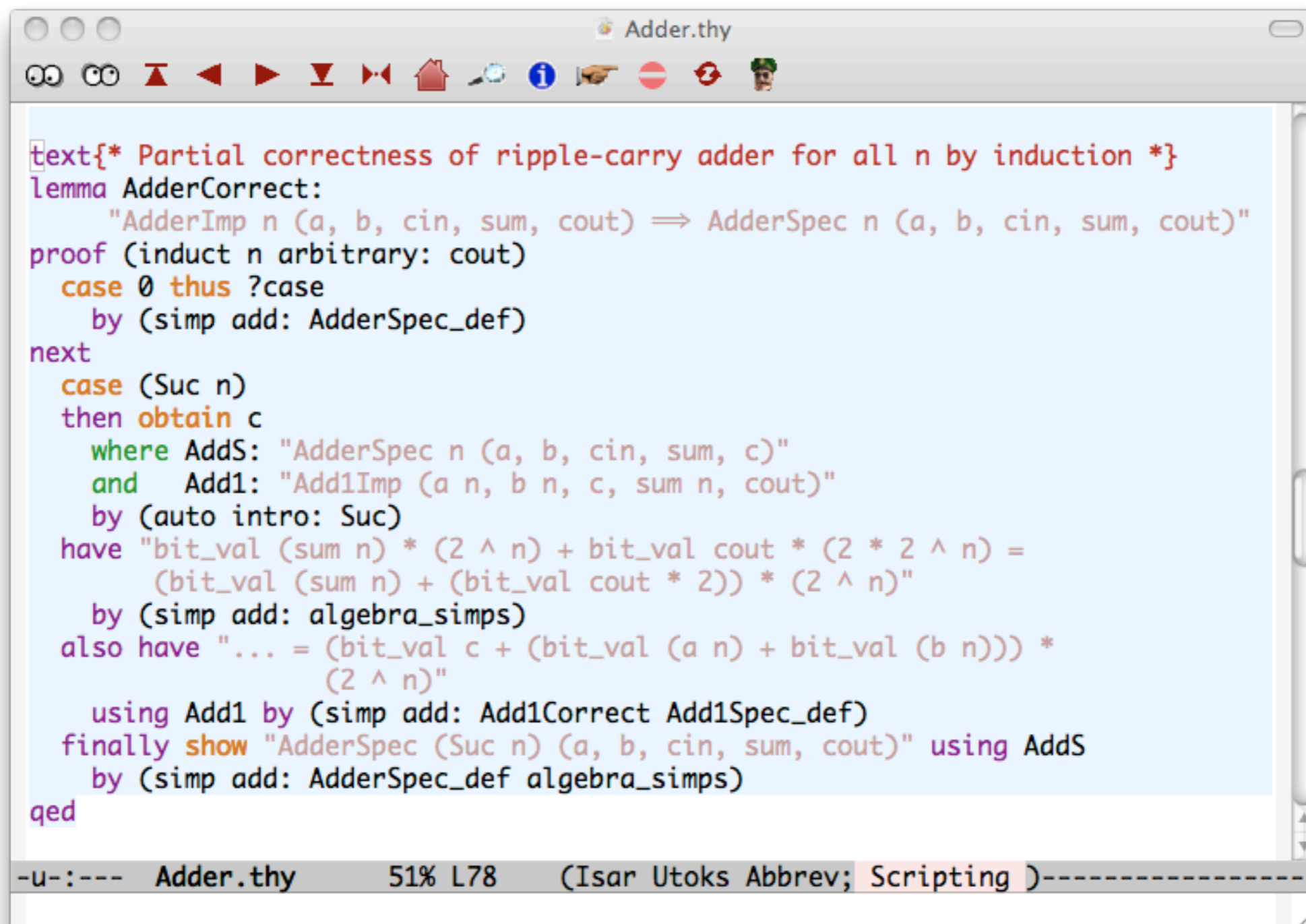

```
text{* Partial correctness of ripple-carry adder for all n by induction *}
lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\implies$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
  by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
  where AddS: "AdderSpec n (a, b, cin, sum, c)"
  and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
  by (auto intro: Suc)
  have "bit_val (sum n) * (2 ^ n) + bit_val cout * (2 * 2 ^ n) =
    (bit_val (sum n) + (bit_val cout * 2)) * (2 ^ n)"
  by (simp add: algebra_simps)
  also have "... = (bit_val c + (bit_val (a n) + bit_val (b n))) *
    (2 ^ n)"
  using Add1 by (simp add: Add1Correct Add1Spec_def)
  finally show "AdderSpec (Suc n) (a, b, cin, sum, cout)" using AddS
  by (simp add: AdderSpec_def algebra_simps)
qed
```

-u-:--- Adder.thy 51% L78 (Isar Utoks Abbrev; Scripting)-----

The Finished Proof

```
text{* Partial correctness of ripple-carry adder for all n by induction *}
lemma AdderCorrect:
  "AdderImp n (a, b, cin, sum, cout)  $\Rightarrow$  AdderSpec n (a, b, cin, sum, cout)"
proof (induct n arbitrary: cout)
  case 0 thus ?case
  by (simp add: AdderSpec_def)
next
  case (Suc n)
  then obtain c
  where AddS: "AdderSpec n (a, b, cin, sum, c)"
  and Add1: "Add1Imp (a n, b n, c, sum n, cout)"
  by (auto intro: Suc)
  have "bit_val (sum n) * (2 ^ n) + bit_val cout * (2 * 2 ^ n) =
    (bit_val (sum n) + (bit_val cout * 2)) * (2 ^ n)"
  by (simp add: algebra_simps)
  also have "... = (bit_val c + (bit_val (a n) + bit_val (b n))) *
    (2 ^ n)"
  using Add1 by (simp add: Add1Correct Add1Spec_def)
  finally show "AdderSpec (Suc n) (a, b, cin, sum, cout)" using AddS
  by (simp add: AdderSpec_def algebra_simps)
qed
```

implementation \Rightarrow specification

-u-:--- Adder.thy 51% L78 (Isar Utoks Abbrev; Scripting)-----


Proving Equivalence

```

Adder.thy
[Lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout))"
apply (auto simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)
-u-:***- Adder.thy      82% L130  (Isar Utoks Abbrev; Scripting )-----
goal (16 subgoals):
1. [[a n; b n; sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + (bits_val a n + bits_val b n))]
   ⇒ False
2. [[a n; b n; sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + (bits_val a n + bits_val b n)]
   ⇒ False
3. [[a n; b n; ¬ sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + bits_val a n + (2 ^ n + bits_val b n))]
   ⇒ False
4. [[a n; b n; ¬ sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + bits_val a n + (2 ^ n + bits_val b n)]
   ⇒ False
5. [[a n; ¬ b n; sum n; cout; cin;
   2 * 2 ^ n + bits_val sum n = Suc (bits_val a n + bits_val b n)]
   ⇒ False
6. [[a n; ¬ b n; sum n; cout; ¬ cin;
   2 * 2 ^ n + bits_val sum n = bits_val a n + bits_val b n]
-u-:%%- *goals*      2% L4  (Isar Proofstate Utoks Abbrev;)-----

```

Proving Equivalence

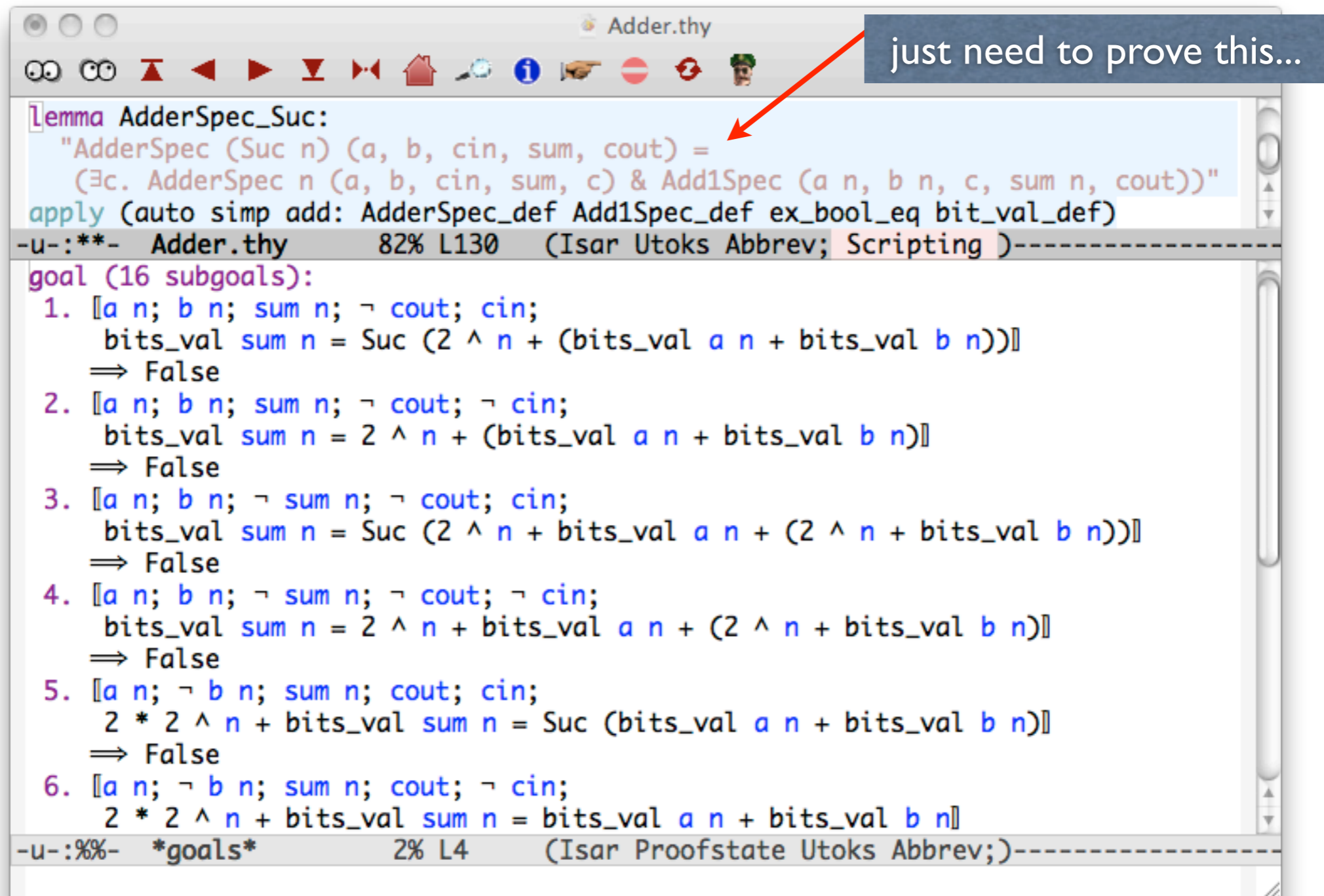

The screenshot shows a theorem prover interface with a toolbar at the top and a main text area. A red arrow points from a blue callout box containing the text "just need to prove this..." to the lemma definition in the code. The code defines a lemma named "AdderSpec_Suc" and applies it to a goal. The goal is a list of 16 subgoals, with the first six shown. Each subgoal is a logical formula involving variables a, b, cin, sum, and cout, and the function bits_val. The subgoals are numbered 1 through 6.

```

Adder.thy
[Lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout))"
apply (auto simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)
-u-:***- Adder.thy      82% L130  (Isar Utoks Abbrev; Scripting )-----
goal (16 subgoals):
1. [[a n; b n; sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + (bits_val a n + bits_val b n))]
   ⇒ False
2. [[a n; b n; sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + (bits_val a n + bits_val b n)]
   ⇒ False
3. [[a n; b n; ¬ sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + bits_val a n + (2 ^ n + bits_val b n))]
   ⇒ False
4. [[a n; b n; ¬ sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + bits_val a n + (2 ^ n + bits_val b n)]
   ⇒ False
5. [[a n; ¬ b n; sum n; cout; cin;
   2 * 2 ^ n + bits_val sum n = Suc (bits_val a n + bits_val b n)]
   ⇒ False
6. [[a n; ¬ b n; sum n; cout; ¬ cin;
   2 * 2 ^ n + bits_val sum n = bits_val a n + bits_val b n]
-u-:%%-  *goals*      2% L4  (Isar Proofstate Utoks Abbrev;)-----

```

Proving Equivalence

```

Adder.thy
[Lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout))"
  apply (auto simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)
-u-:***- Adder.thy      82% L130  (Isar Utoks Abbrev; Scripting )-----
goal (16 subgoals):
1. [[a n; b n; sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + (bits_val a n + bits_val b n))]
  ⇒ False
2. [[a n; b n; sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + (bits_val a n + bits_val b n)]
  ⇒ False
3. [[a n; b n; ¬ sum n; ¬ cout; cin;
   bits_val sum n = Suc (2 ^ n + bits_val a n + (2 ^ n + bits_val b n))]
  ⇒ False
4. [[a n; b n; ¬ sum n; ¬ cout; ¬ cin;
   bits_val sum n = 2 ^ n + bits_val a n + (2 ^ n + bits_val b n)]
  ⇒ False
5. [[a n; ¬ b n; sum n; cout; cin;
   2 * 2 ^ n + bits_val sum n = Suc (bits_val a n + bits_val b n)]
  ⇒ False
6. [[a n; ¬ b n; sum n; cout; ¬ cin;
   2 * 2 ^ n + bits_val sum n = bits_val a n + bits_val b n]
-u-:%%-  *goals*      2% L4  (Isar Proofstate Utoks Abbrev; )-----

```

just need to prove this...

HELP!!

A Crucial Lemma

```

Adder.thy
[lemma bits_val_less: "bits_val f n < 2^n"
by (induct n, auto simp add: bit_val_def)

lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout
))"
using bits_val_less [of a n] bits_val_less [of b n] bits_val_less [of sum n]
by (simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)


-u:---- Adder.thy      85% L139  (Isar Utoks Abbrev; Scripting )-----
proof (prove): step 1

using this:
  bits_val a n < 2 ^ n
  bits_val b n < 2 ^ n
  bits_val sum n < 2 ^ n

goal (1 subgoal):
  1. AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) ^
      Add1Spec (a n, b n, c, sum n, cout))

-u:%%- *goals*      1% L2  (Isar Proofstate Utoks Abbrev;)-----
```

A Crucial Lemma

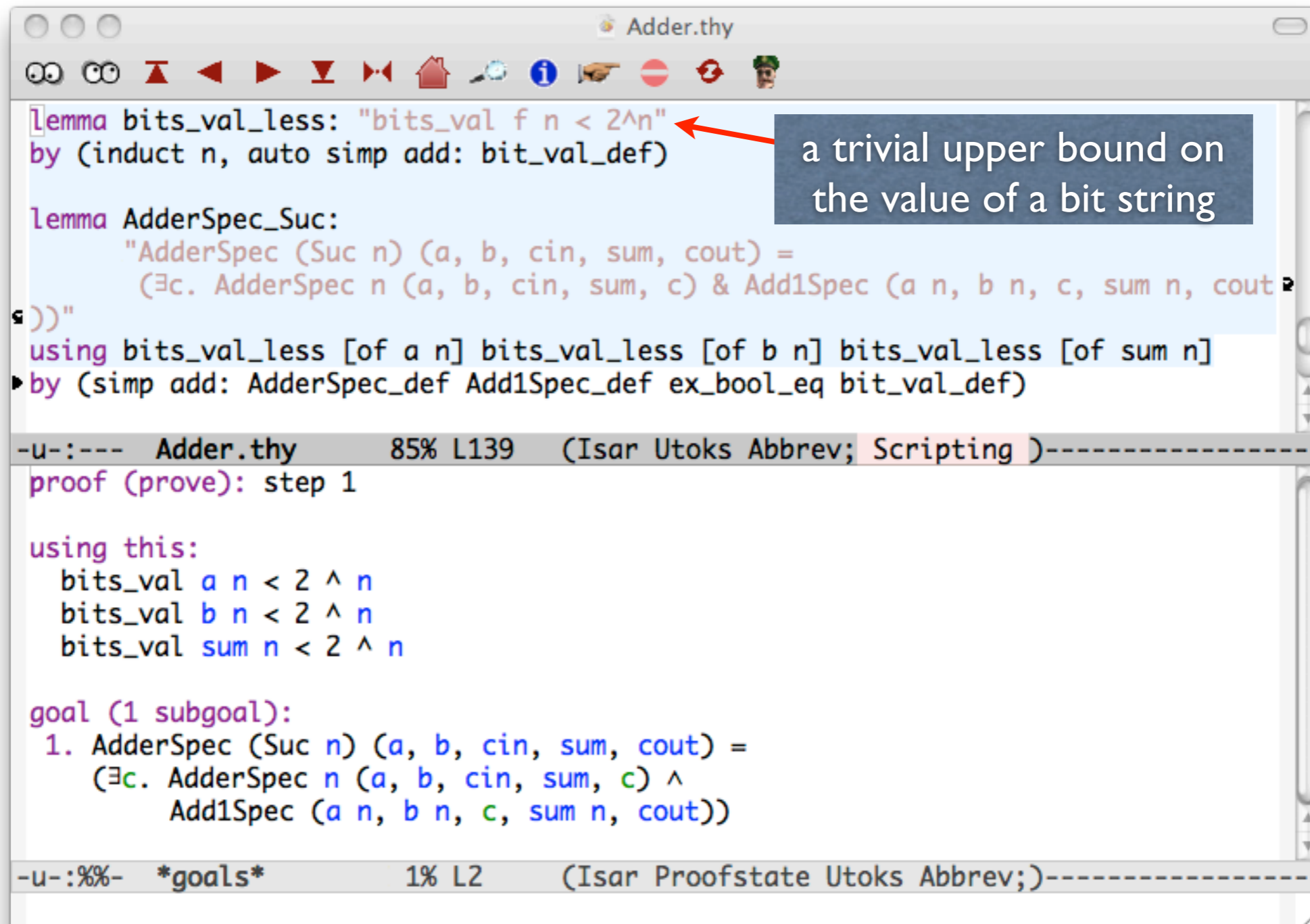

The screenshot shows a window titled "Adder.thy" with a toolbar at the top. The main area contains the following text:

```
lemma bits_val_less: "bits_val f n < 2^n"
by (induct n, auto simp add: bit_val_def)

lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
   (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout
))"
using bits_val_less [of a n] bits_val_less [of b n] bits_val_less [of sum n]
by (simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)
```

A red arrow points from a dark blue box containing the text "a trivial upper bound on the value of a bit string" to the lemma `bits_val_less`.

```
-u-:--- Adder.thy      85% L139  (Isar Utoks Abbrev; Scripting )-----
proof (prove): step 1

using this:
  bits_val a n < 2 ^ n
  bits_val b n < 2 ^ n
  bits_val sum n < 2 ^ n

goal (1 subgoal):
  1. AdderSpec (Suc n) (a, b, cin, sum, cout) =
     (∃c. AdderSpec n (a, b, cin, sum, c) ^
      Add1Spec (a n, b n, c, sum n, cout))
```

```
-u-:%%- *goals*      1% L2  (Isar Proofstate Utoks Abbrev;)-----
```

A Crucial Lemma

```

Adder.thy
[lemma bits_val_less: "bits_val f n < 2^n"
by (induct n, auto simp add: bit_val_def)

lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
  (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout
))"
using bits_val_less [of a n] bits_val_less [of b n] bits_val_less [of sum n]
by (simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)

-u:---- Adder.thy      85% L139  (Isar Utoks Abbrev; Scripting )-----
proof (prove): step 1
using this:
  bits_val a n < 2 ^ n
  bits_val b n < 2 ^ n
  bits_val sum n < 2 ^ n

goal (1 subgoal):
  1. AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) ^
      Add1Spec (a n, b n, c, sum n, cout))

-u:%%- *goals*          1% L2    (Isar Proofstate Utoks Abbrev;)-

```

a trivial upper bound on the value of a bit string

inserting three instances of that fact

A Crucial Lemma

```
lemma bits_val_less: "bits_val f n < 2^n"
by (induct n, auto simp add: bit_val_def)

lemma AdderSpec_Suc:
  "AdderSpec (Suc n) (a, b, cin, sum, cout) =
  (∃c. AdderSpec n (a, b, cin, sum, c) & Add1Spec (a n, b n, c, sum n, cout)
  )"
using bits_val_less [of a n] bits_val_less [of b n] bits_val_less [of sum n]
by (simp add: AdderSpec_def Add1Spec_def ex_bool_eq bit_val_def)

-u:---- Adder.thy      85% L139  (Isar Utoks Abbrev; Scripting )-----
proof (prove): step 1
using this:
  bits_val a n < 2 ^ n
  bits_val b n < 2 ^ n
  bits_val sum n < 2 ^ n

goal (1 subgoal):
  1. AdderSpec (Suc n) (a, b, cin, sum, cout) =
    (∃c. AdderSpec n (a, b, cin, sum, c) ^
    Add1Spec (a n, b n, c, sum n, cout))

-u:%%- *goals*      1% L2  (Isar Proofstate Utoks Abbrev;)
```

a trivial upper bound on the value of a bit string

inserting three instances of that fact

now proof is trivial, by arithmetic

The Opposite Implication

The screenshot shows a window titled "Adder.thy" with a toolbar at the top. The main text area contains the following code:

```
Lemma AdderCorrect2:  
  "AdderSpec n (a, b, cin, sum, cout)  $\Rightarrow$  AdderImp n (a, b, cin, sum, cout)"  
apply (induct n arbitrary: cout)  
apply (simp add: AdderSpec_def)  
apply (auto simp add: AdderSpec_Suc Add1Correct)  
done
```

Below the code is a status bar with the text: "-u-:**- Adder.thy 91% L148 (Isar Utoks Abbrev; Scripting)-----".

Below the status bar is a scrollable area containing the output of the proof:

```
Lemma  
  AdderCorrect2:  
    AdderSpec ?n (?a, ?b, ?cin, ?sum, ?cout)  $\Rightarrow$   
    AdderImp ?n (?a, ?b, ?cin, ?sum, ?cout)
```

At the bottom of the window is another status bar with the text: "-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)-----".

The Opposite Implication

The screenshot shows a window titled "Adder.thy" with a toolbar at the top. The main text area contains the following code:

```
Lemma AdderCorrect2:  
  "AdderSpec n (a, b, cin, sum, cout)  $\Rightarrow$  AdderImp n (a, b, cin, sum, cout)"  
apply (induct n arbitrary: cout)  
apply (simp add: AdderSpec_def)  
apply (auto simp add: AdderSpec_Suc Add1Correct)  
done
```

Below the code is a status bar: "-u-:**- Adder.thy 91% L148 (Isar Utoks Abbrev; Scripting)-----".

The bottom part of the window shows the rendered output of the lemma:

```
Lemma  
  AdderCorrect2:  
  AdderSpec ?n (?a, ?b, ?cin, ?sum, ?cout)  $\Rightarrow$   
  AdderImp ?n (?a, ?b, ?cin, ?sum, ?cout)
```

At the bottom of the window is another status bar: "-u-:%%- *response* All L4 (Isar Messages Utoks Abbrev;)-----".

The implementation and specification are equivalent!

Making Instances of Theorems

Making Instances of Theorems

- *thm* [of *a b c*]
replaces variables by terms from left to right

Making Instances of Theorems

- *thm* [of a b c]
replaces variables by terms from left to right
- *thm* [where $x=a$]
replaces the variable x by the term a

Making Instances of Theorems

- thm [of a b c]
replaces variables by terms from left to right
- thm [where $x=a$]
replaces the variable x by the term a
- thm [OF thm_1 thm_2 thm_3]
discharges premises from left to right

Making Instances of Theorems

- thm [of a b c]
replaces variables by terms from left to right
- thm [where $x=a$]
replaces the variable x by the term a
- thm [OF thm_1 thm_2 thm_3]
discharges premises from left to right
- thm [simplified]
applies the simplifier to thm

Making Instances of Theorems

- *thm* [of *a b c*]
replaces variables by terms from left to right
- *thm* [where *x=a*]
replaces the variable *x* by the term *a*
- *thm* [OF *thm₁ thm₂ thm₃*]
discharges premises from left to right
- *thm* [simplified]
applies the simplifier to *thm*
- *thm* [*attr₁, attr₂, attr₃*]
applying multiple attributes

The End

You know my methods. Apply them!

Sherlock Holmes