

 
 



A Broadside Register

 


A broadside two-to-one multiplexor

 


A dual port register file

 


Read Only Memory (ROM)

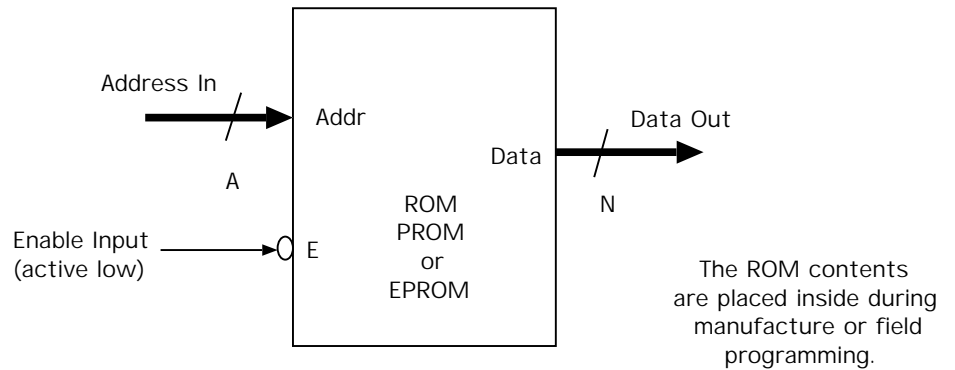

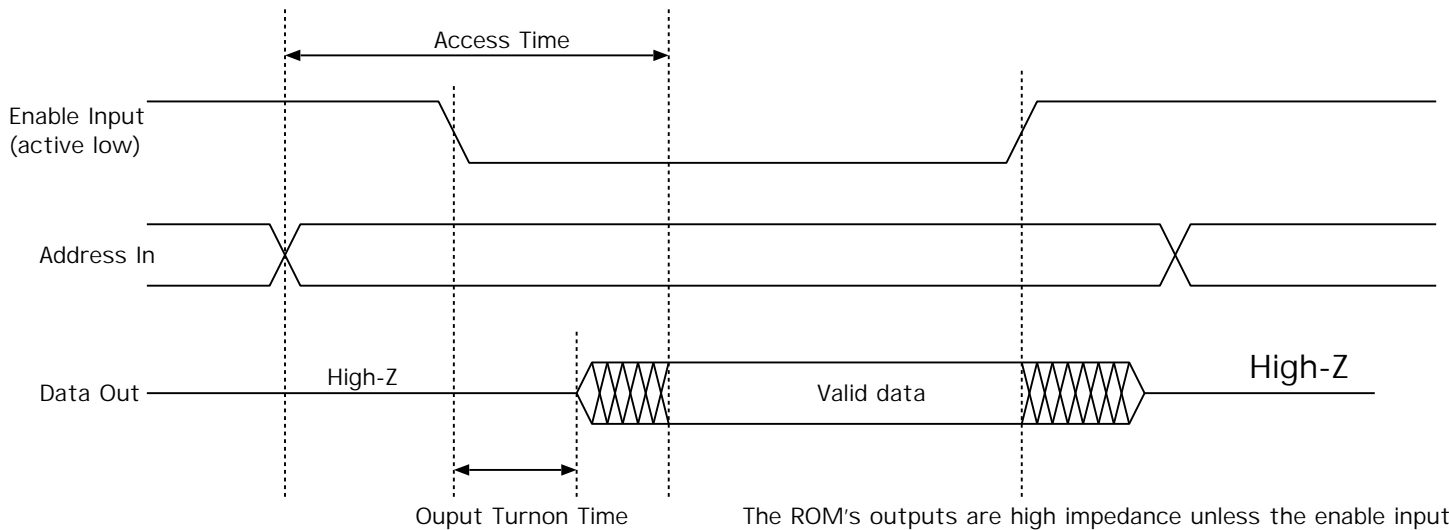
The ROM takes A address bits named A_0 to A_{A-1} and produces data words of N bits wide. For example, if $A=5$ and $D=8$ then the ROM contains 2^5 which is 32 locations of 8 bits each. The address lines are called A_0, A_1, A_2, A_3, A_4 and the data lines D_0, D_1, \dots, D_7



 
The ROM's outputs are high impedance unless the enable input is asserted (low). After the enable is low the output drivers turn on. When the address has been stable sufficiently long, valid data from that address comes out.




Read Cycle - Like the ROM

 


Write Cycle - Data stored internally

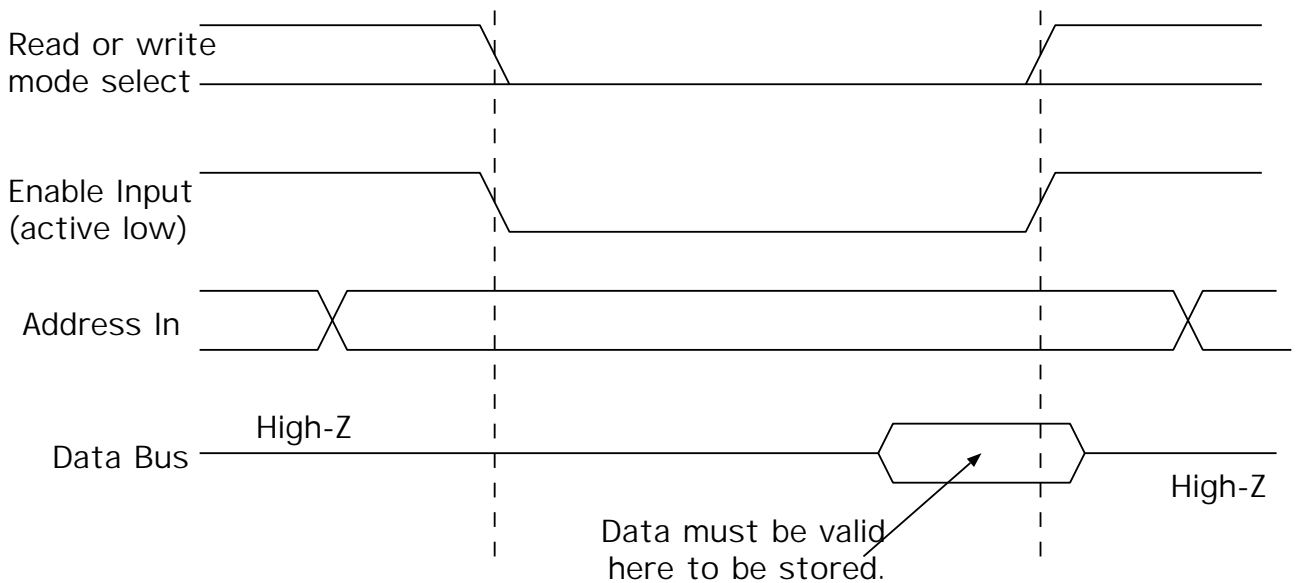

 
Unlike the edge-triggered flip-flop, the transparent latch passes data through in a transparent way when its enable input is high. When its enable input is low, the output stays at the current value.




Transparent latch schematic symbol

 


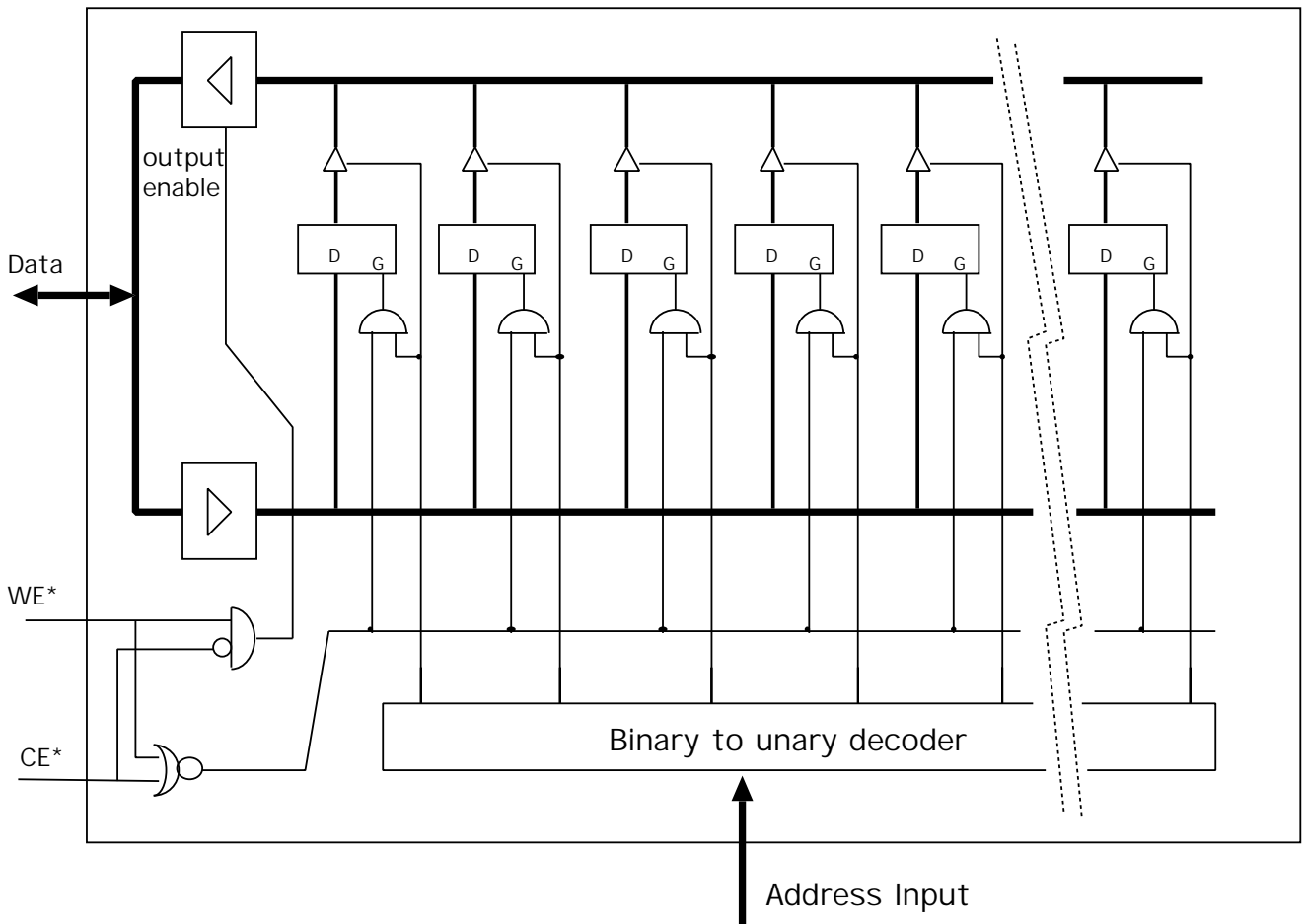Transparent latch implemented from gates.



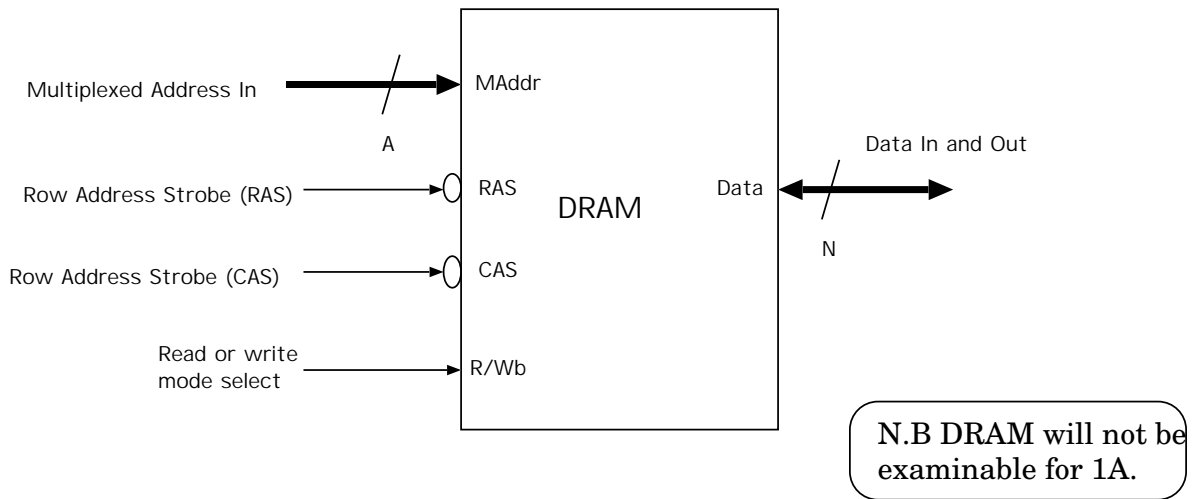

Read Cycle (write is similar)

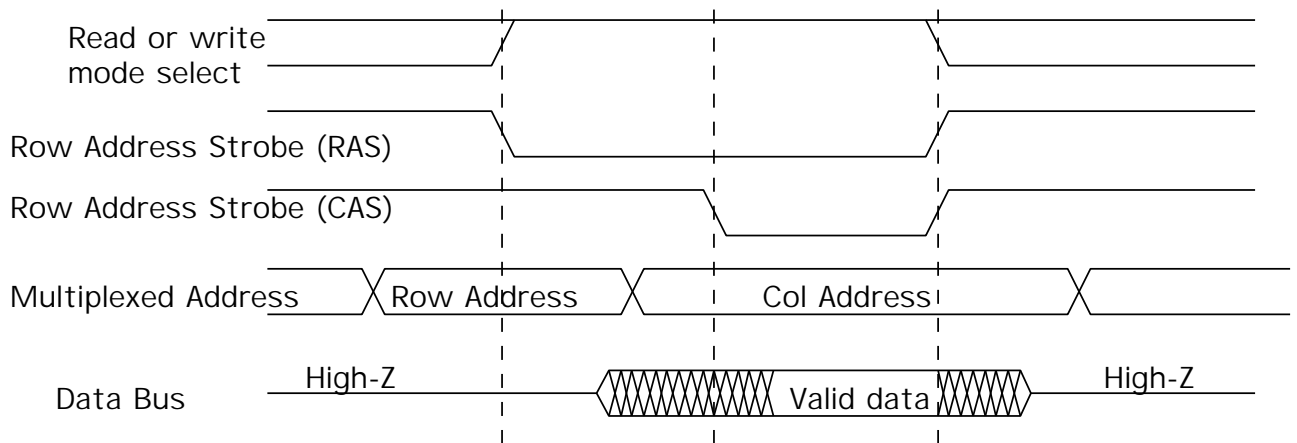


A DRAM has a multiplexed address bus and the address is presented in two halves, known as row and column addresses. So the capacity is $4 \times A \times D$. A 4 Mbit DRAM might have $A=10$ and $D=4$.

When a processor (or its cache) wishes to read many locations in sequence, only one row address needs be given and multiple col addresses can be given quickly to access data in the same row. This is known as 'page mode' access.


EDO (extended data out) DRAM is now quite common. This guarantees data to be valid for an extended period after CAS, thus helping system timing design at high CAS rates.

 Refresh Cycle - must happen sufficiently often!




No data enters or leaves the DRAM during refresh, so it 'eats memory bandwidth'. Typically 512 cycles of refresh must be done every 8 milliseconds.


Crystal oscillator clock source

 


RC oscillator clock source

 


Clock multiplication and distribution

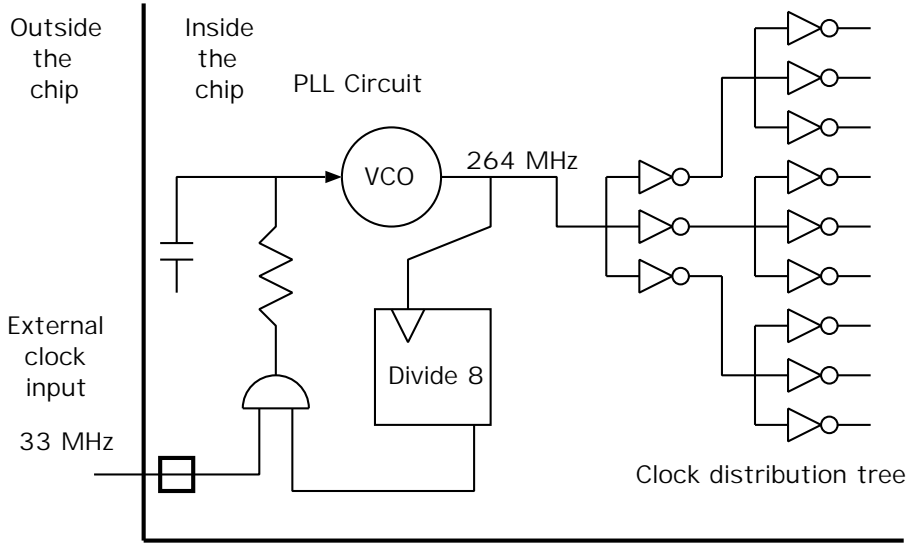



Power-on reset

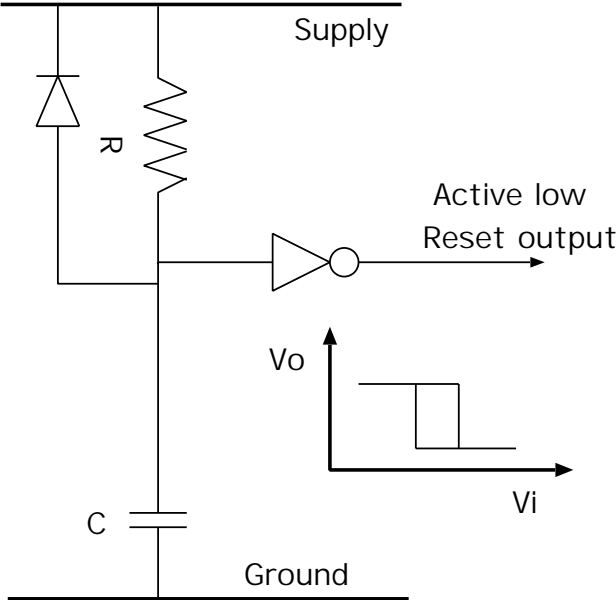

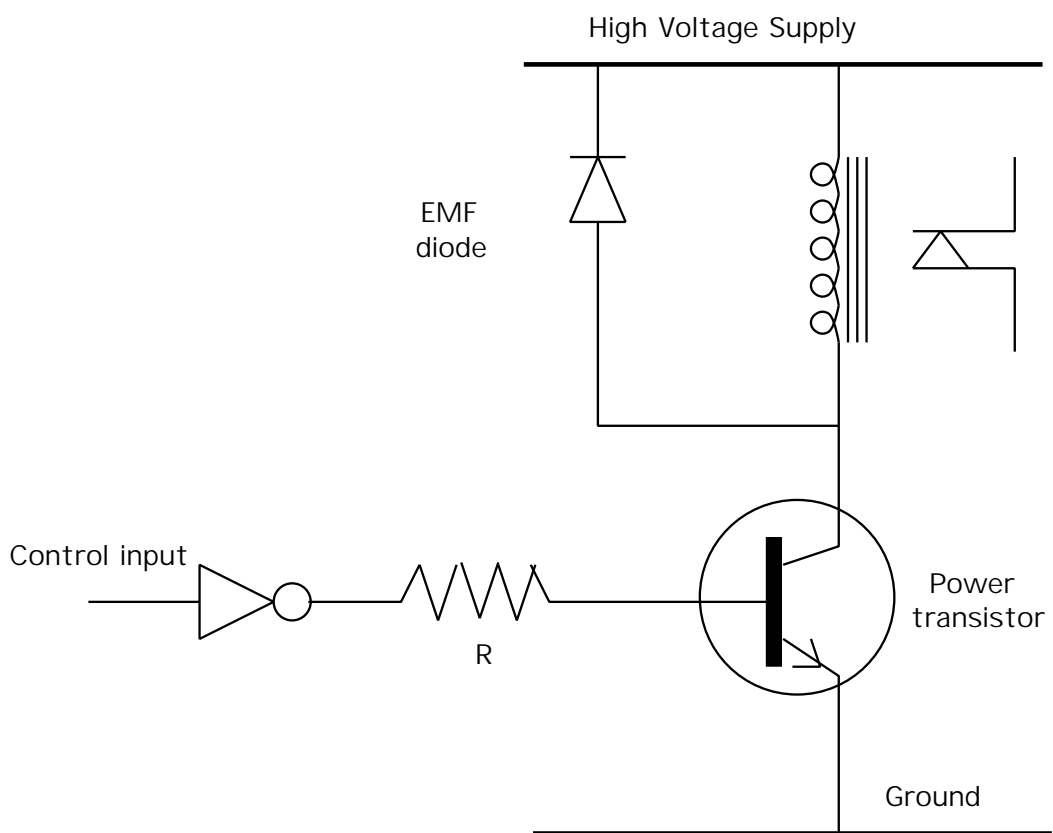
Driving a heavy current or high-voltage load




Debouncer circuit for a two-pole switch

 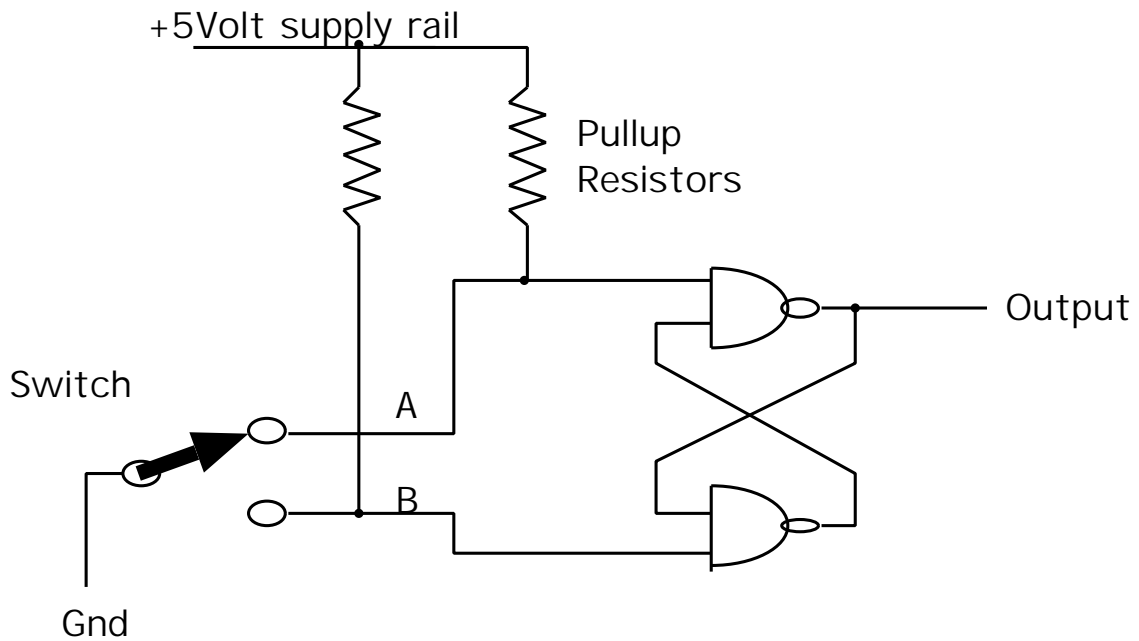


ALU and flags register

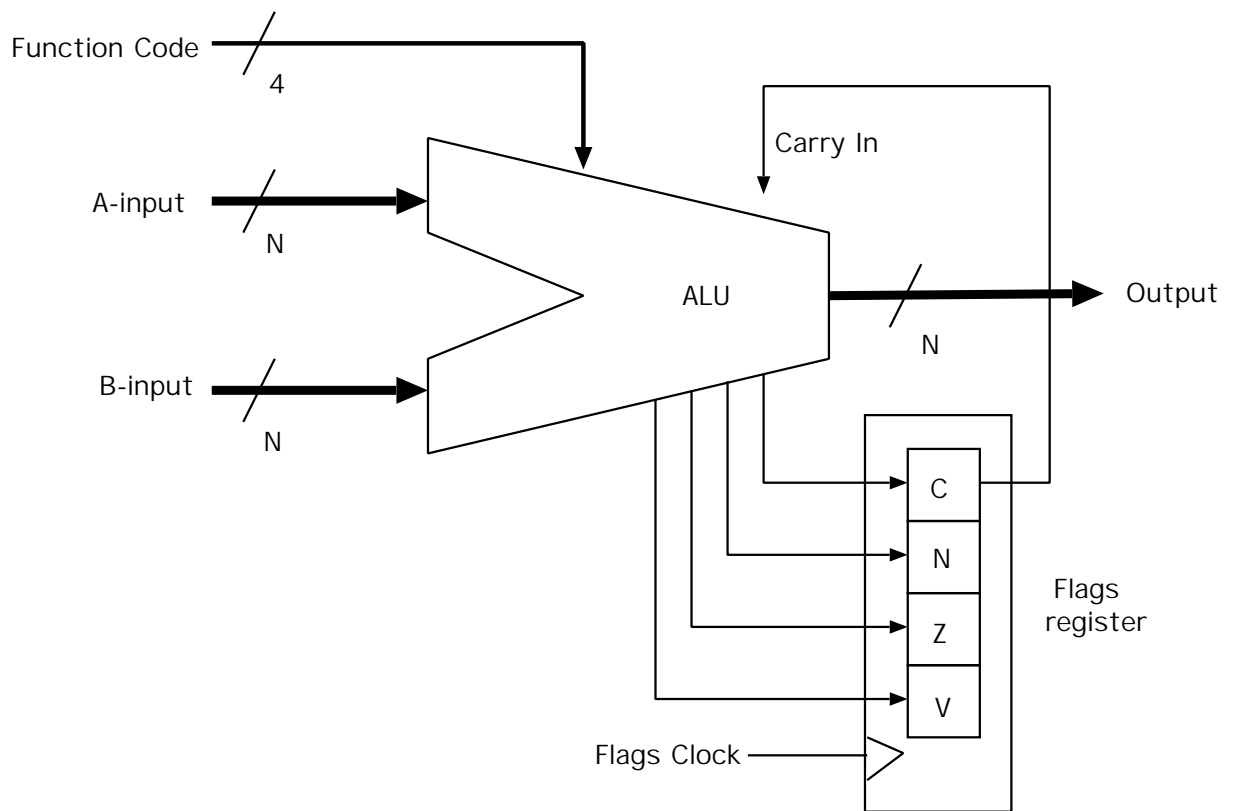

ALU and register file

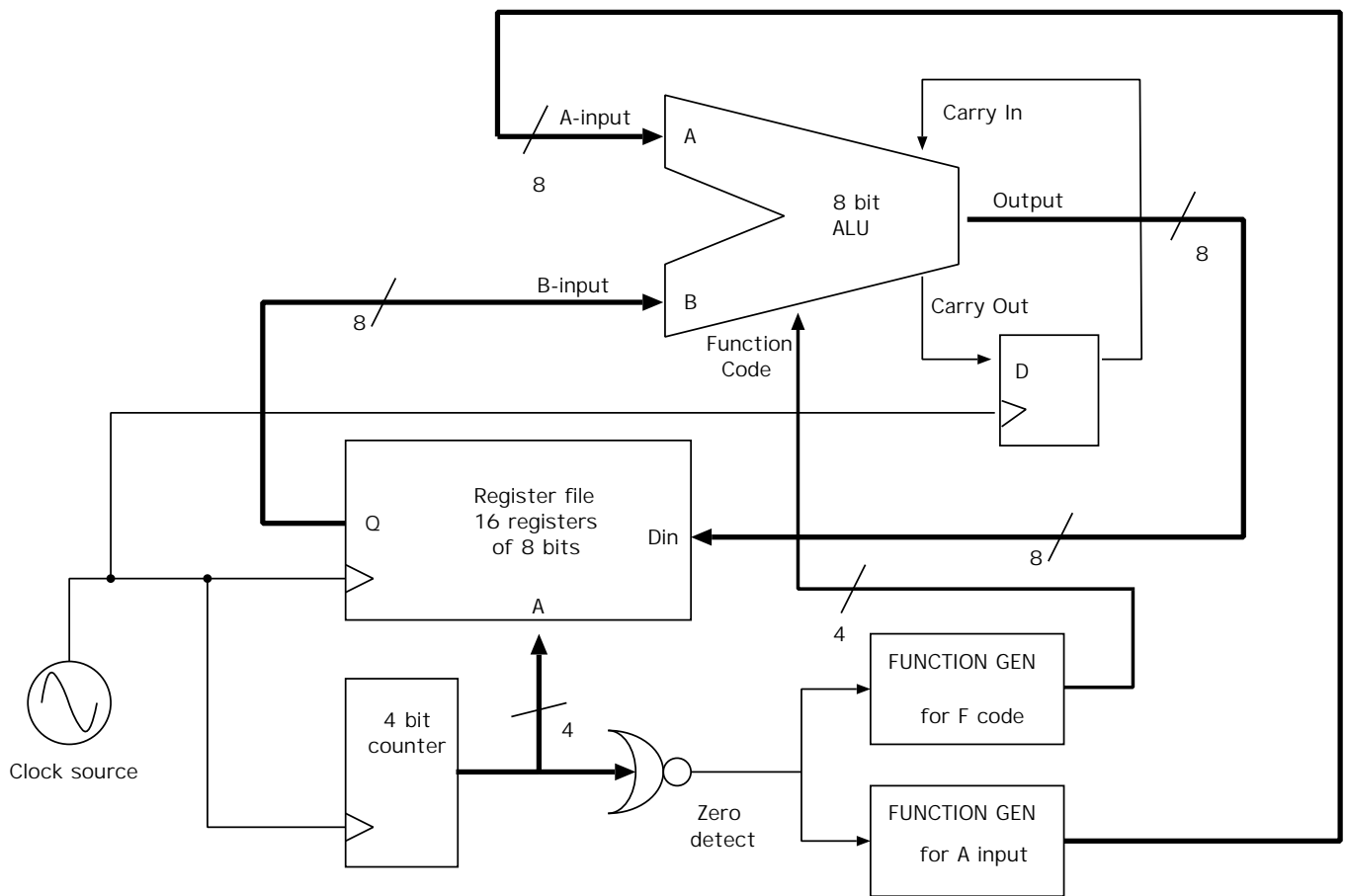



Logic Symbol

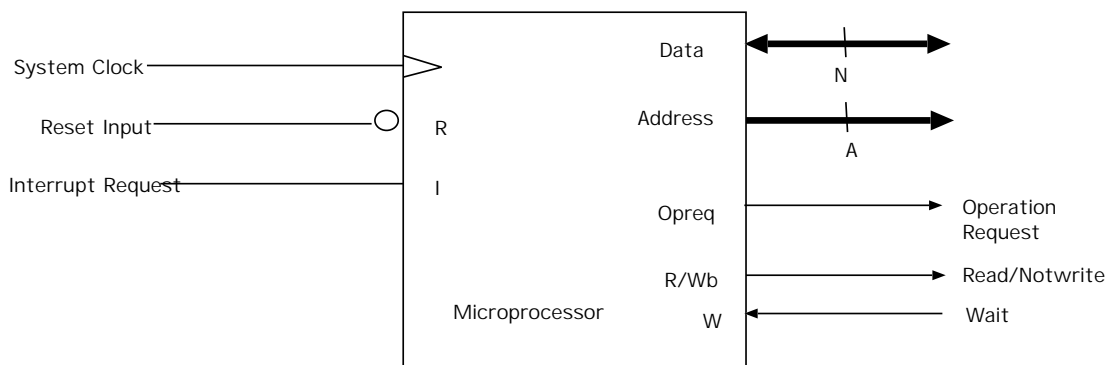

Internal Structure Block Diagram

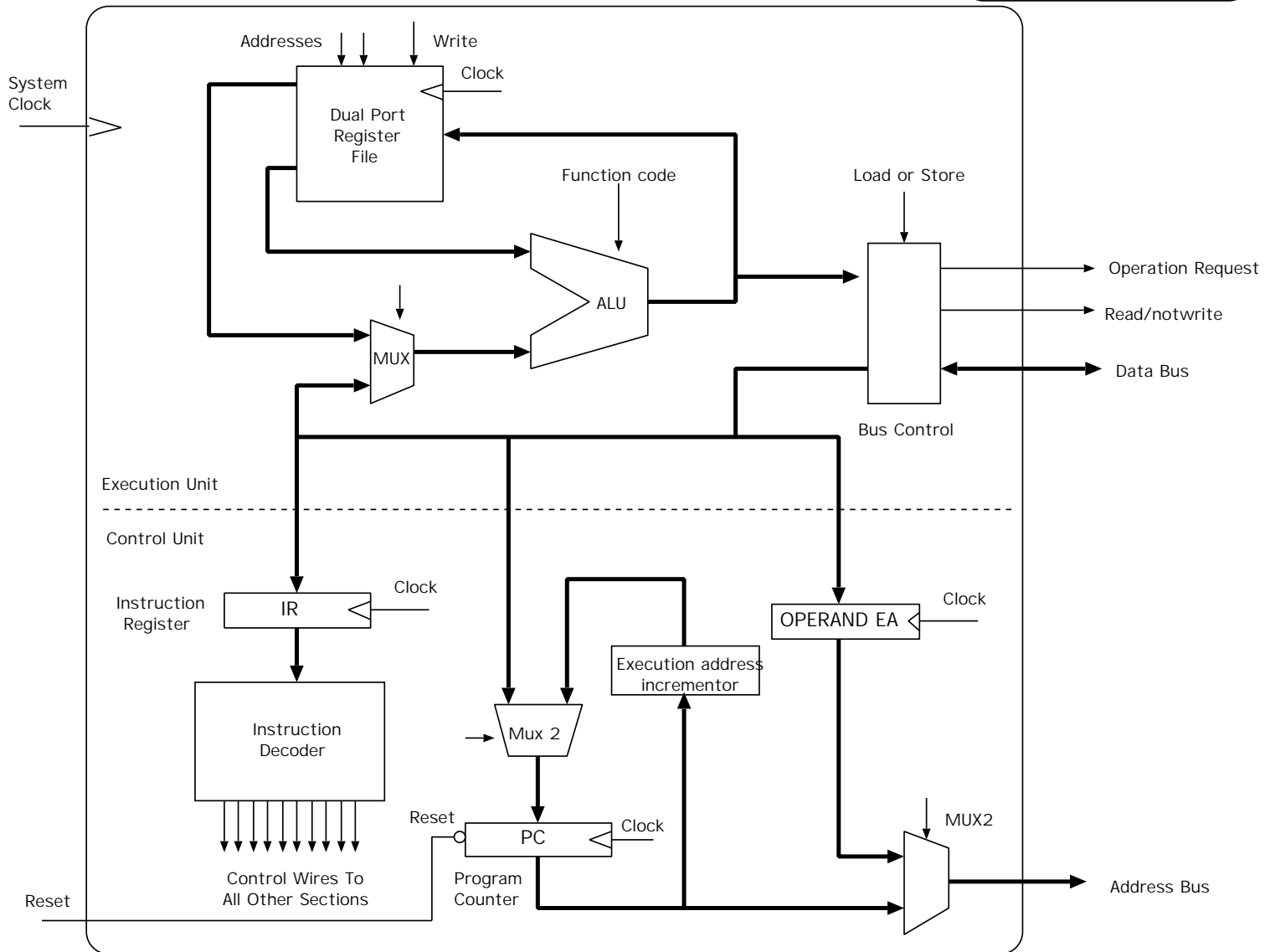
NB: Microprocessor internal details are not examinable for 1A.



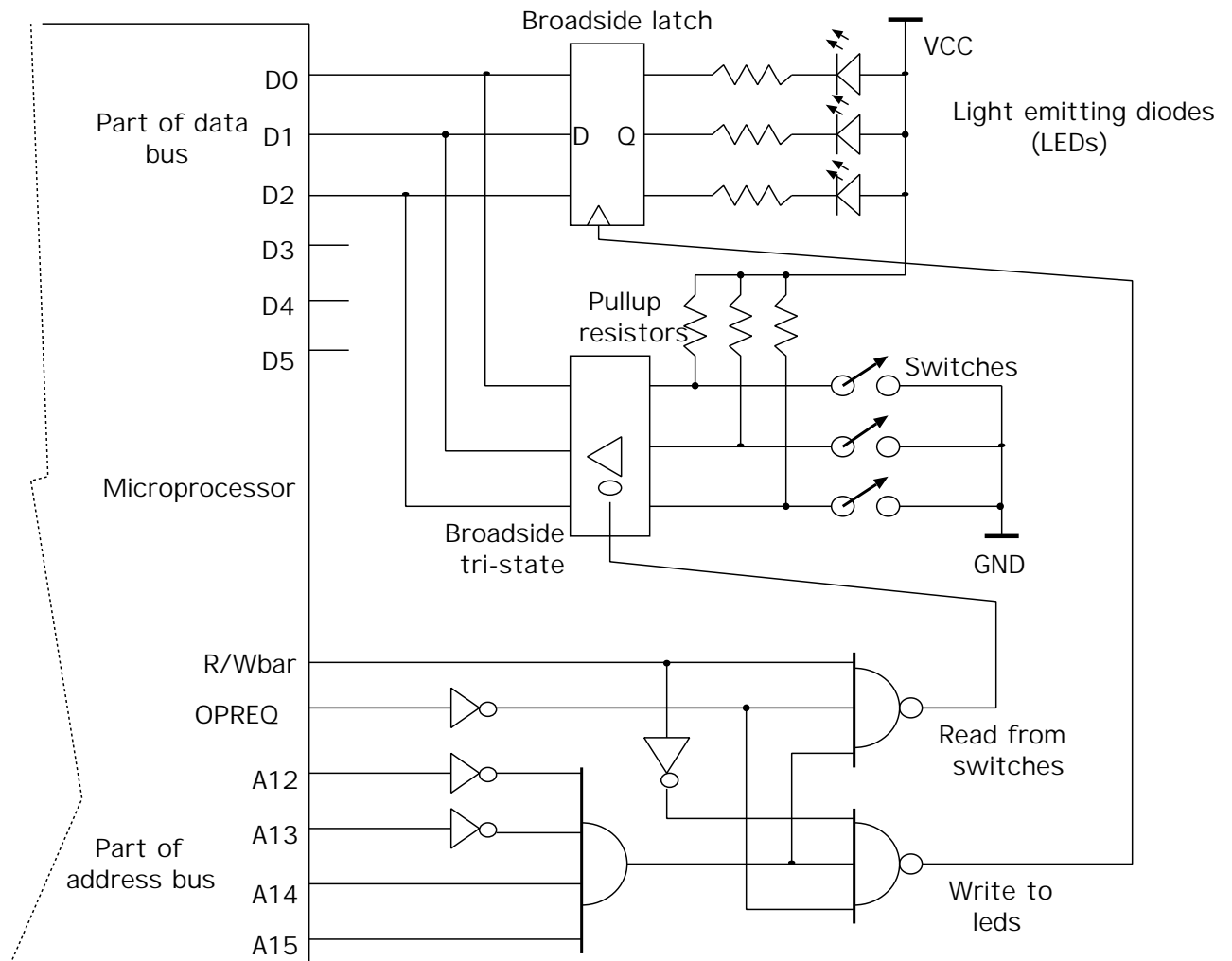


Example of memory address decode and simple LED and switch interfacing for programmed IO (PIO) to a microprocessor.



A small computer

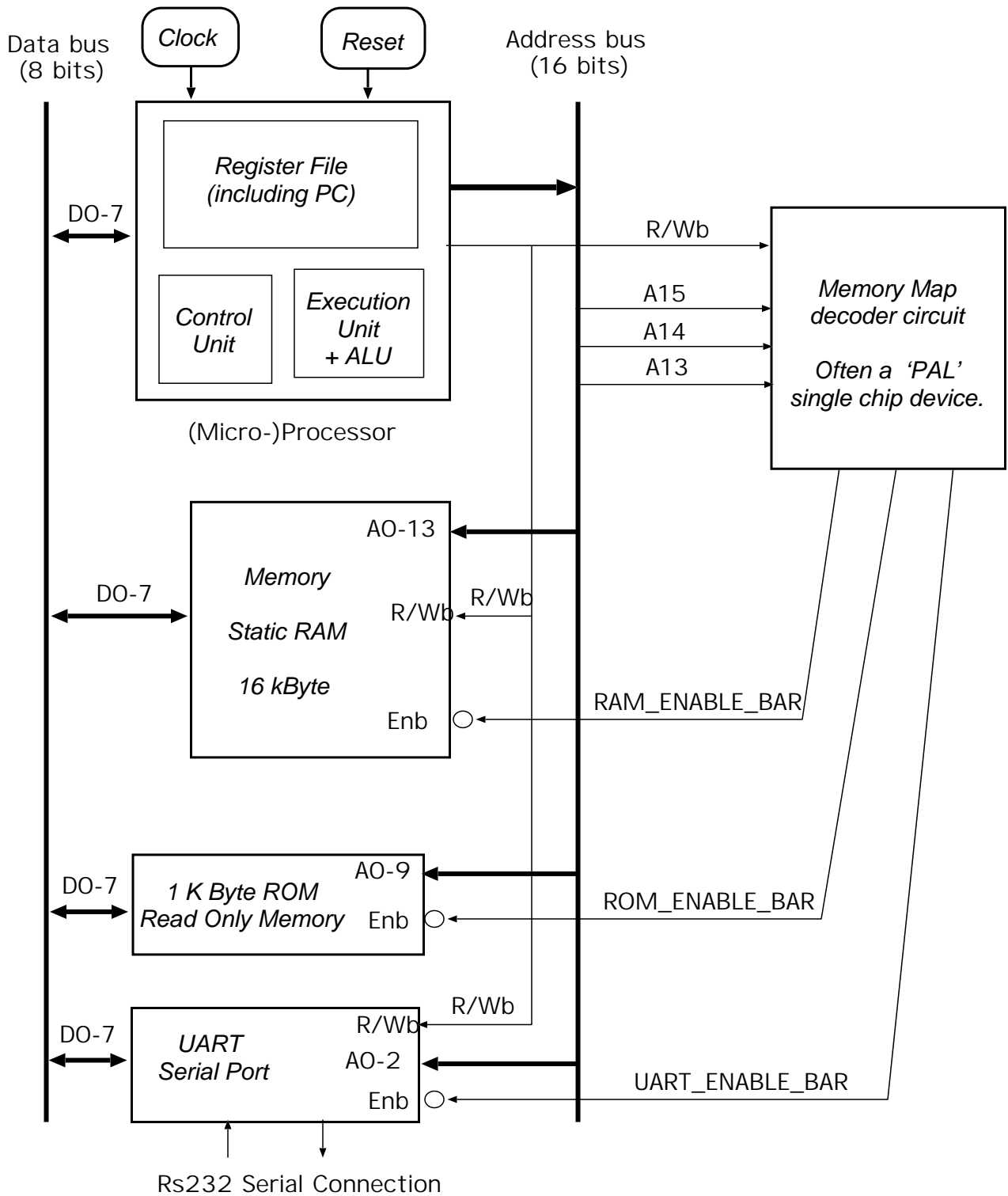

PC Motherboard, 1997 vintage


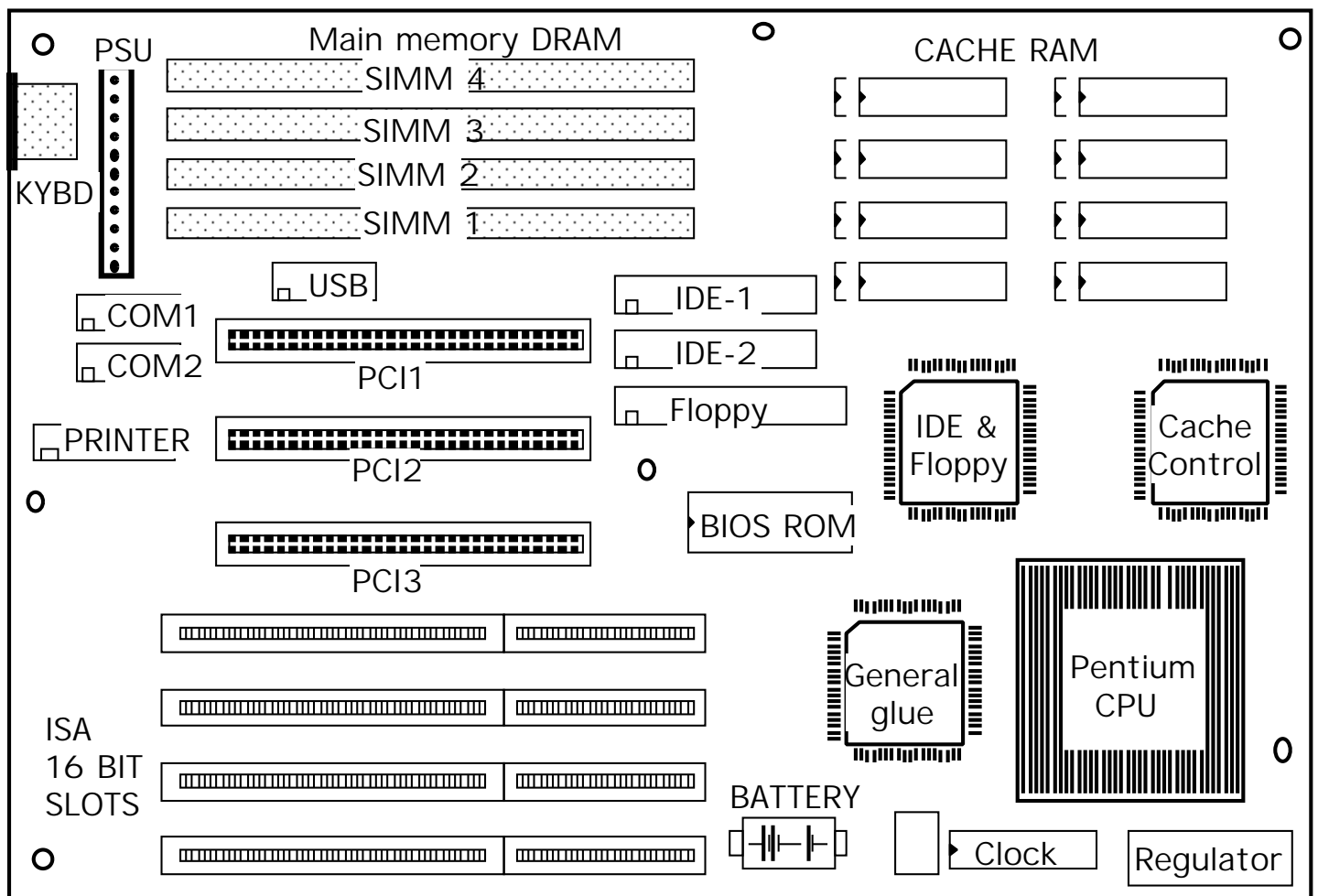


Parallel Port

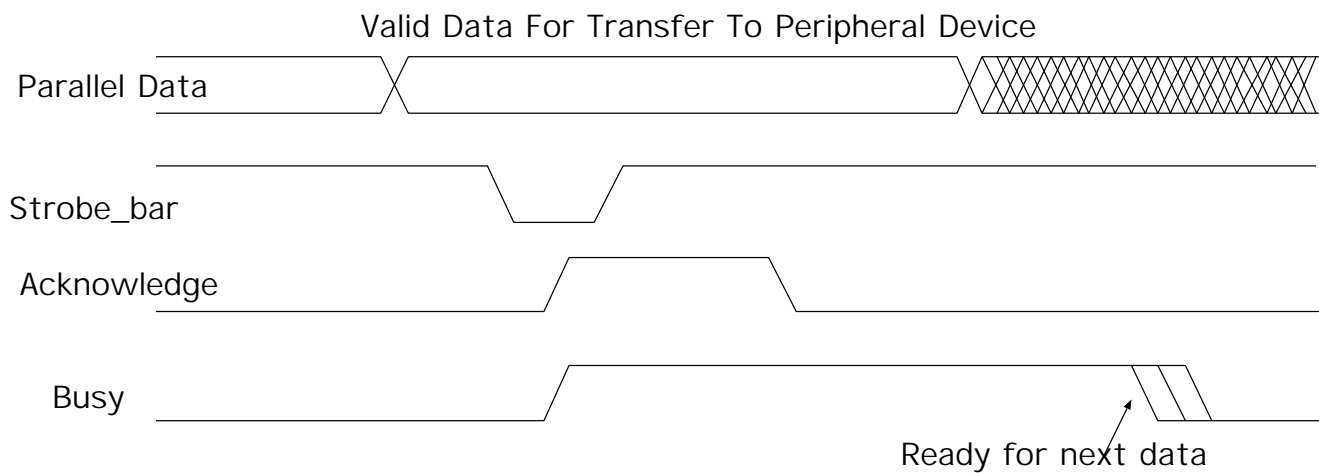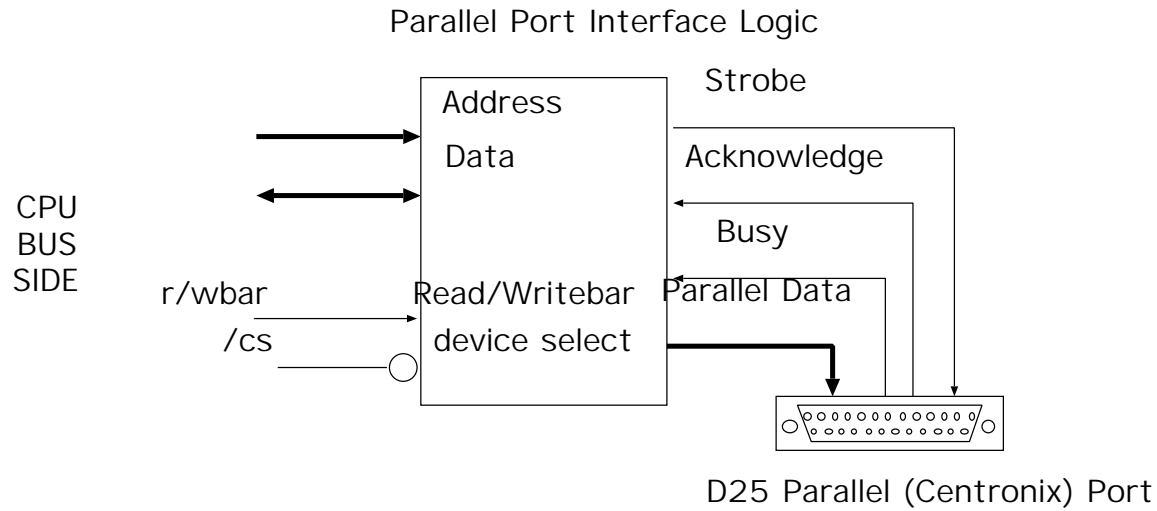



Flow control: New data is not sent while the busy wire is high.

Serial Port (UART)

 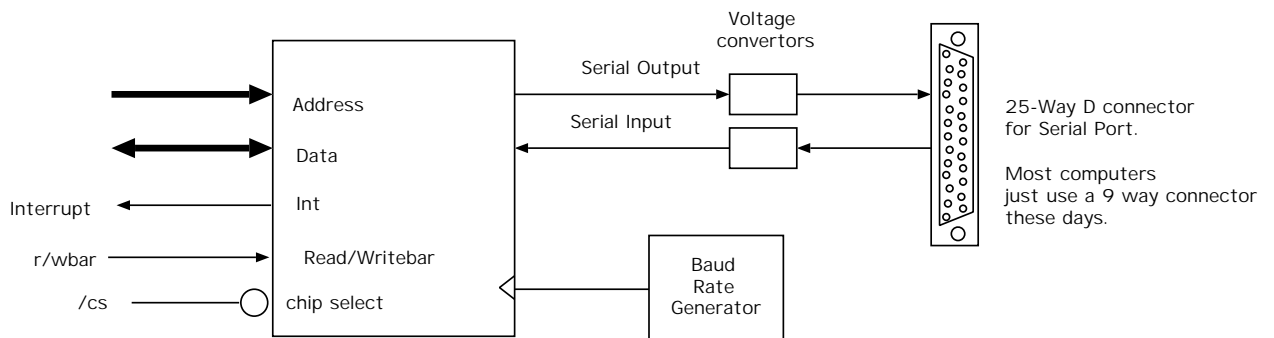


Flow control: New data can be sent at any time unless either:
 additional signals are used to indicate clear to send
 or
 a software protocol is defined to run on top (Xon/Xoff) by reserving certain of the bytes.



Keyboard and/or PS/2 port

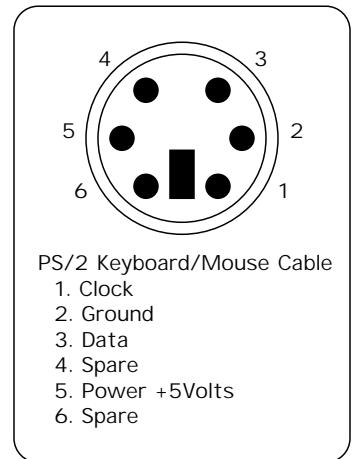 



Canonical synchronous FSM

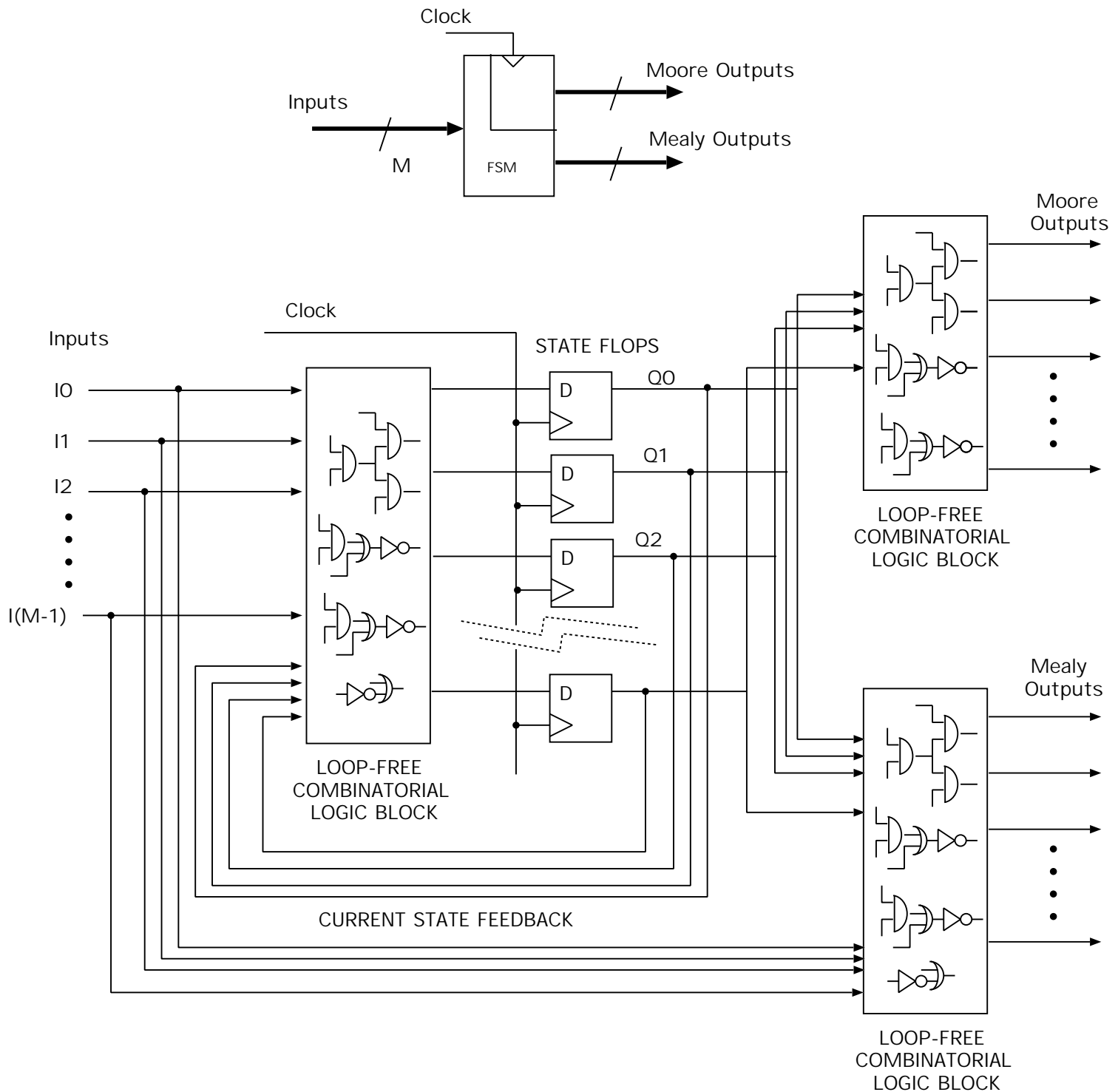


Timing Specifications

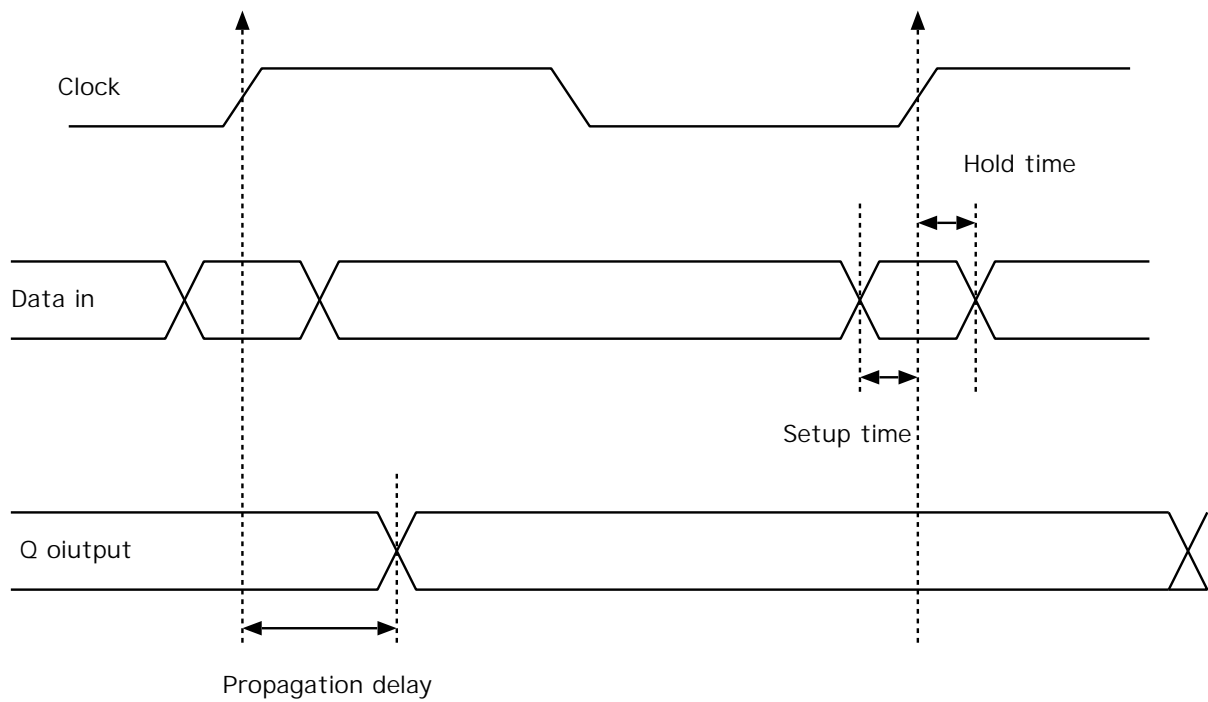 


Typical nature of a critical path

  


Johnson counters

 

Pipelining

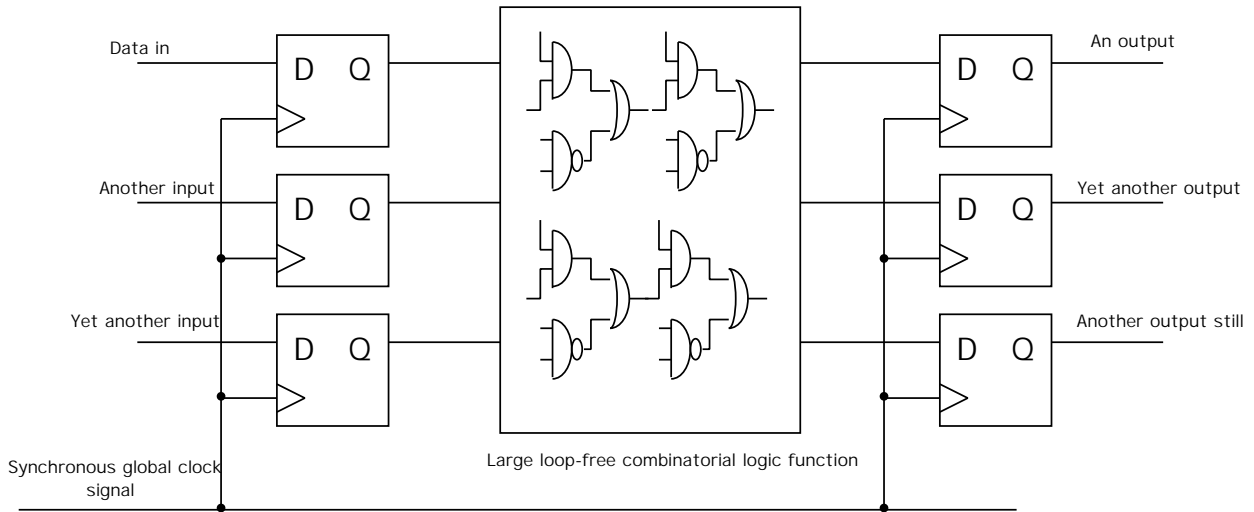


Desired logic function

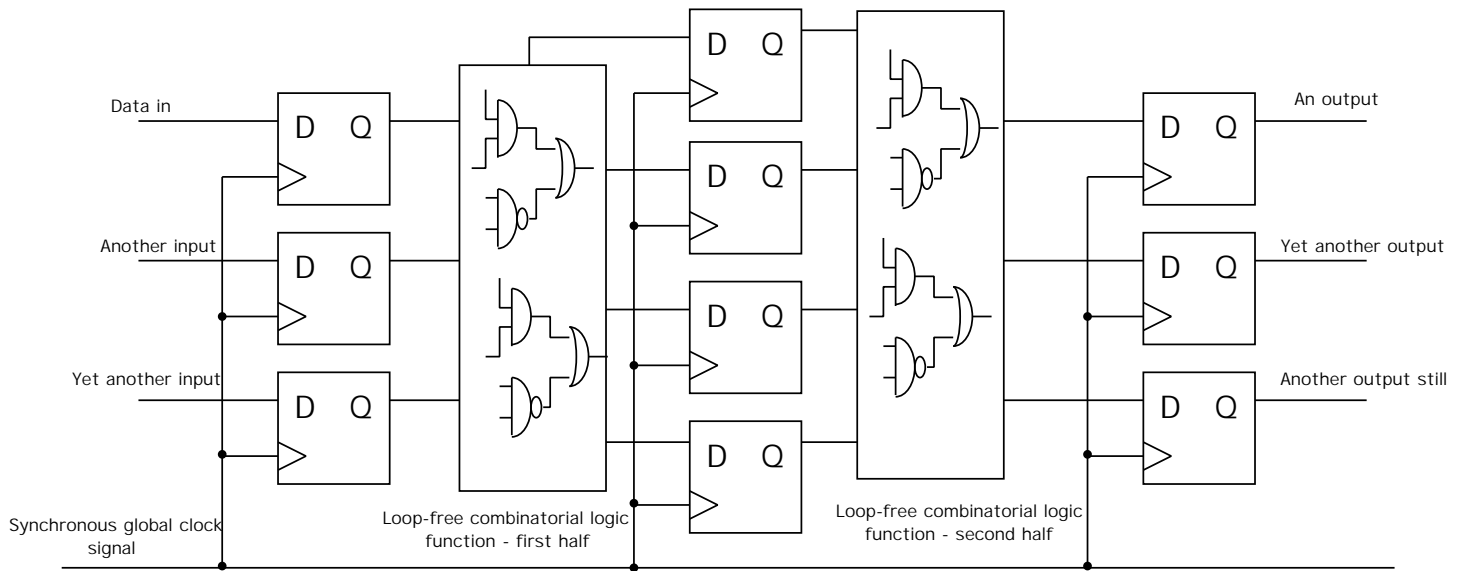


Desired logic function - pipelined version.



Cascading FSMs

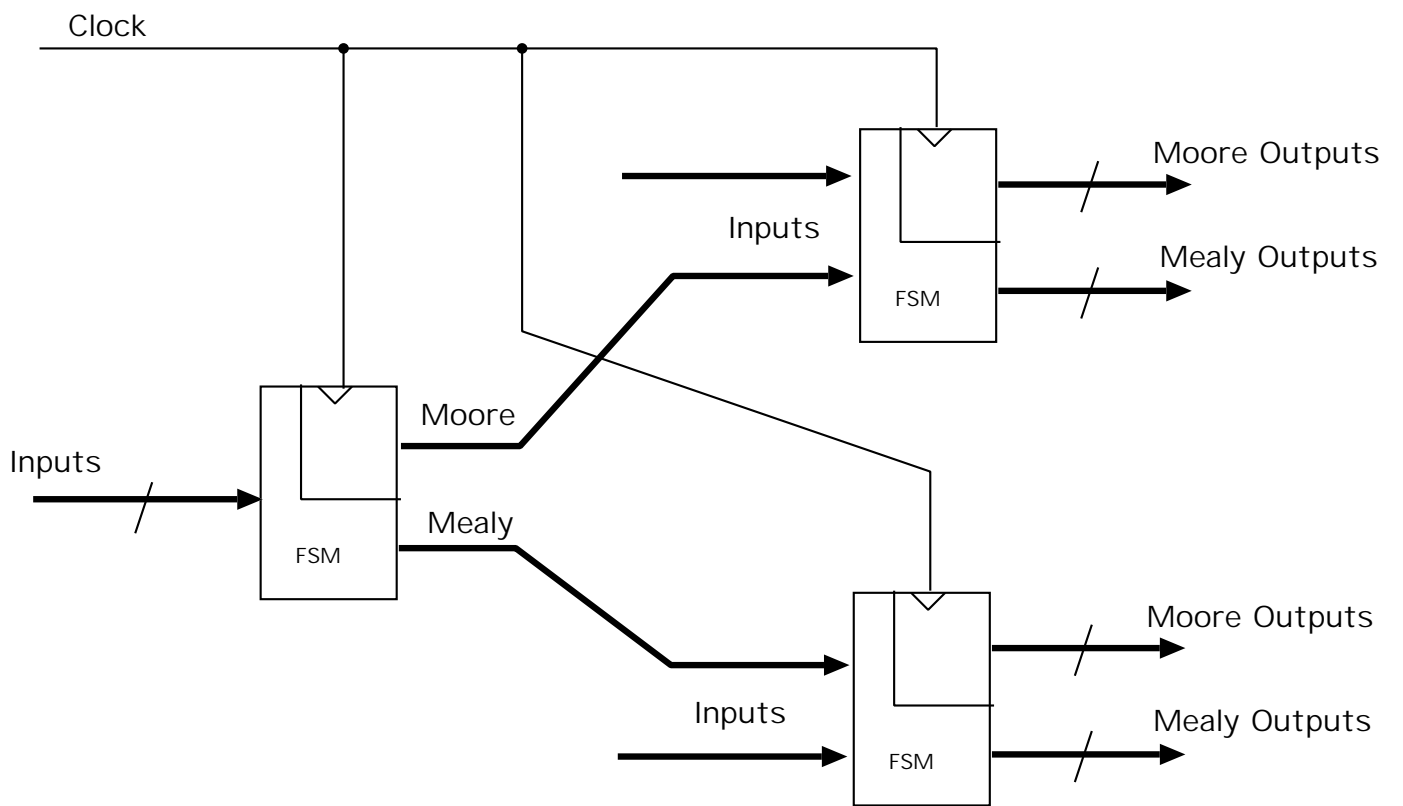

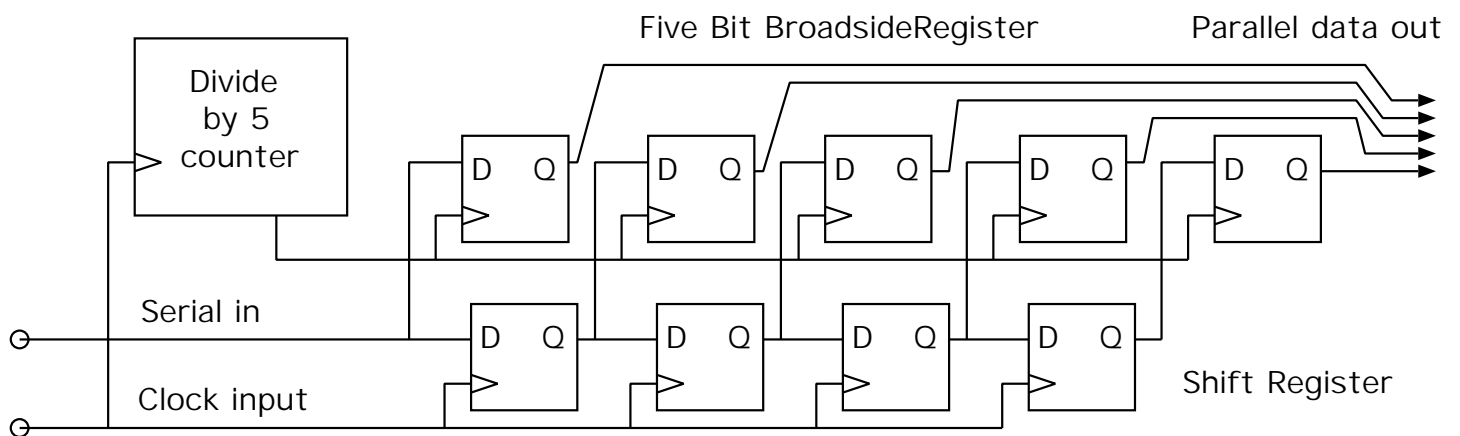
An example that uses (badly) a derived clock:
a serial-to-parallel converter




A D-type with clock-enable

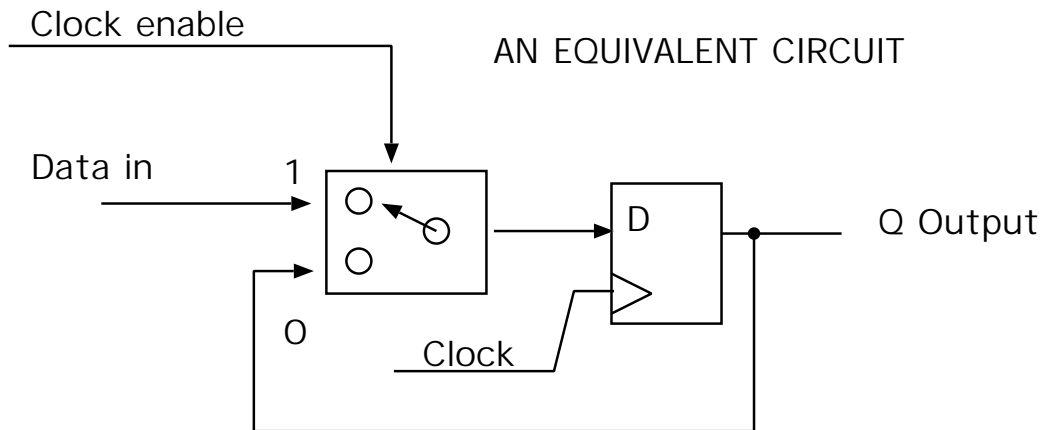 


A Gated Clock

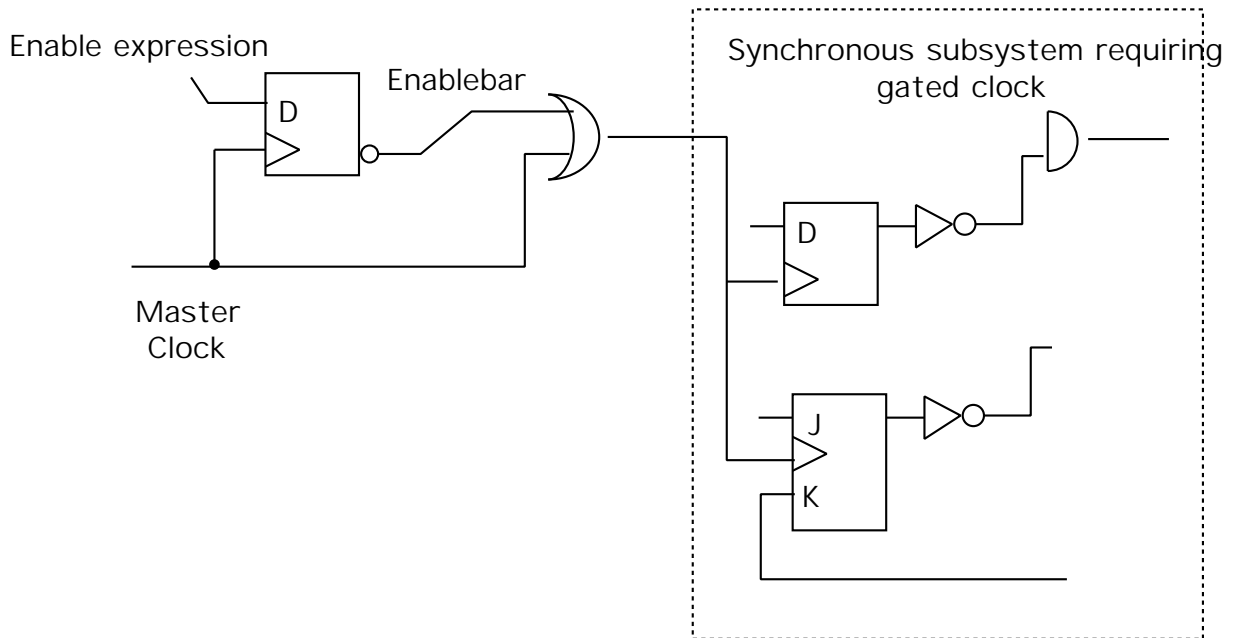


Clock Skew

 

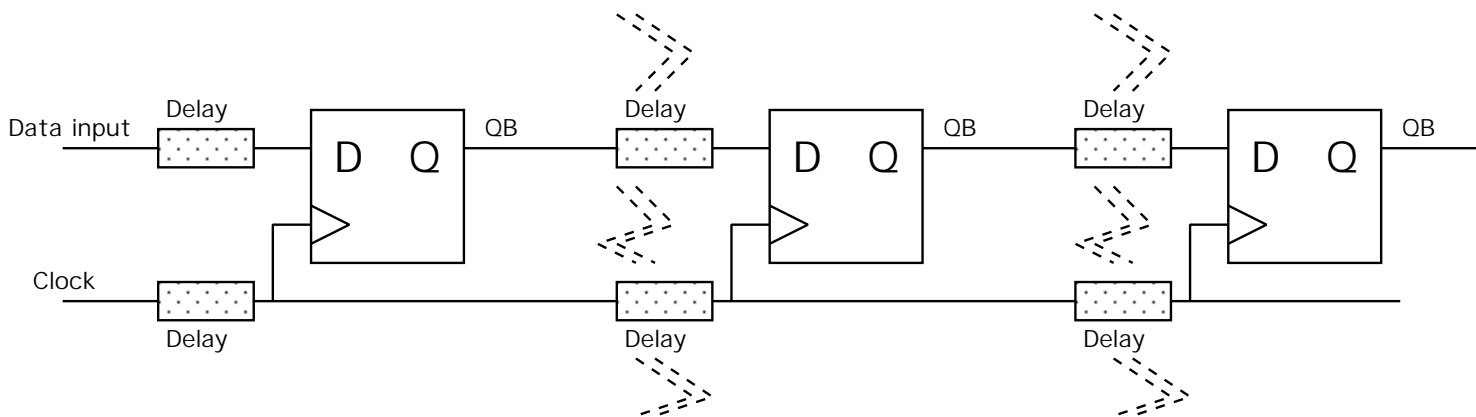a) A three-stage shift register with some clock skew delays.




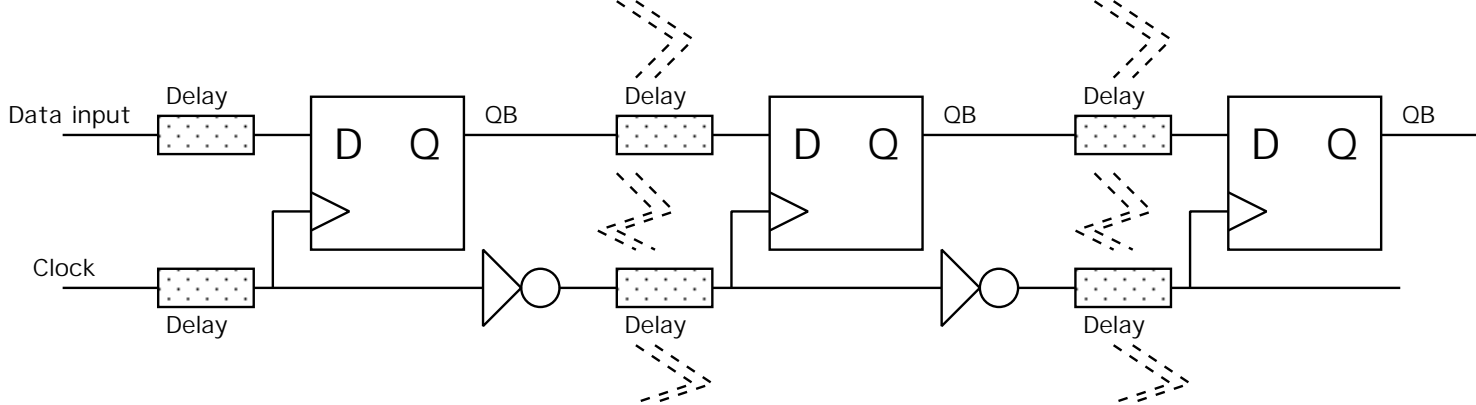b) System interconnection with clock skews




c) A solution for serious skew and delay problems ?


Crossing an async boundary

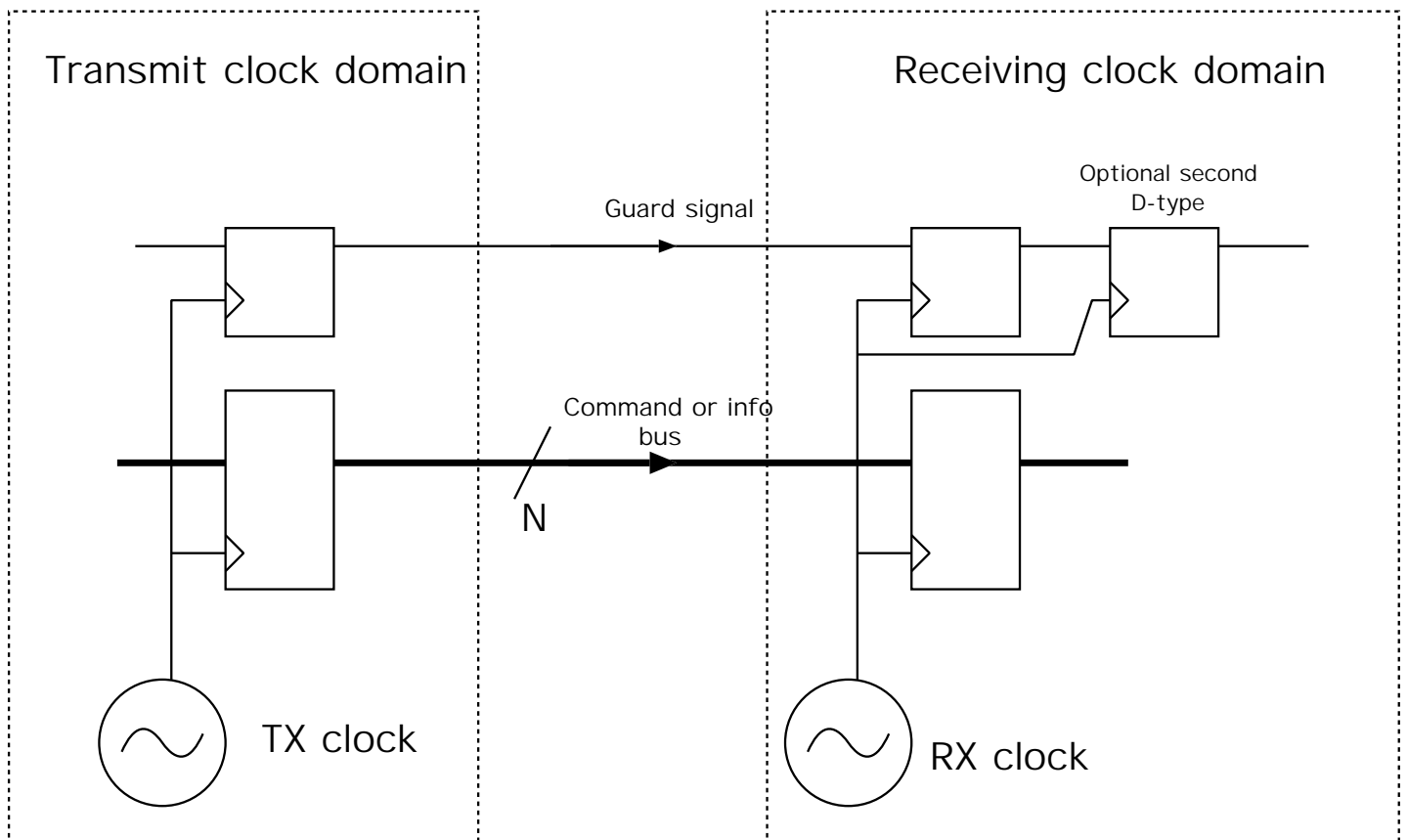

Paths between FSMs w/ derived clocks

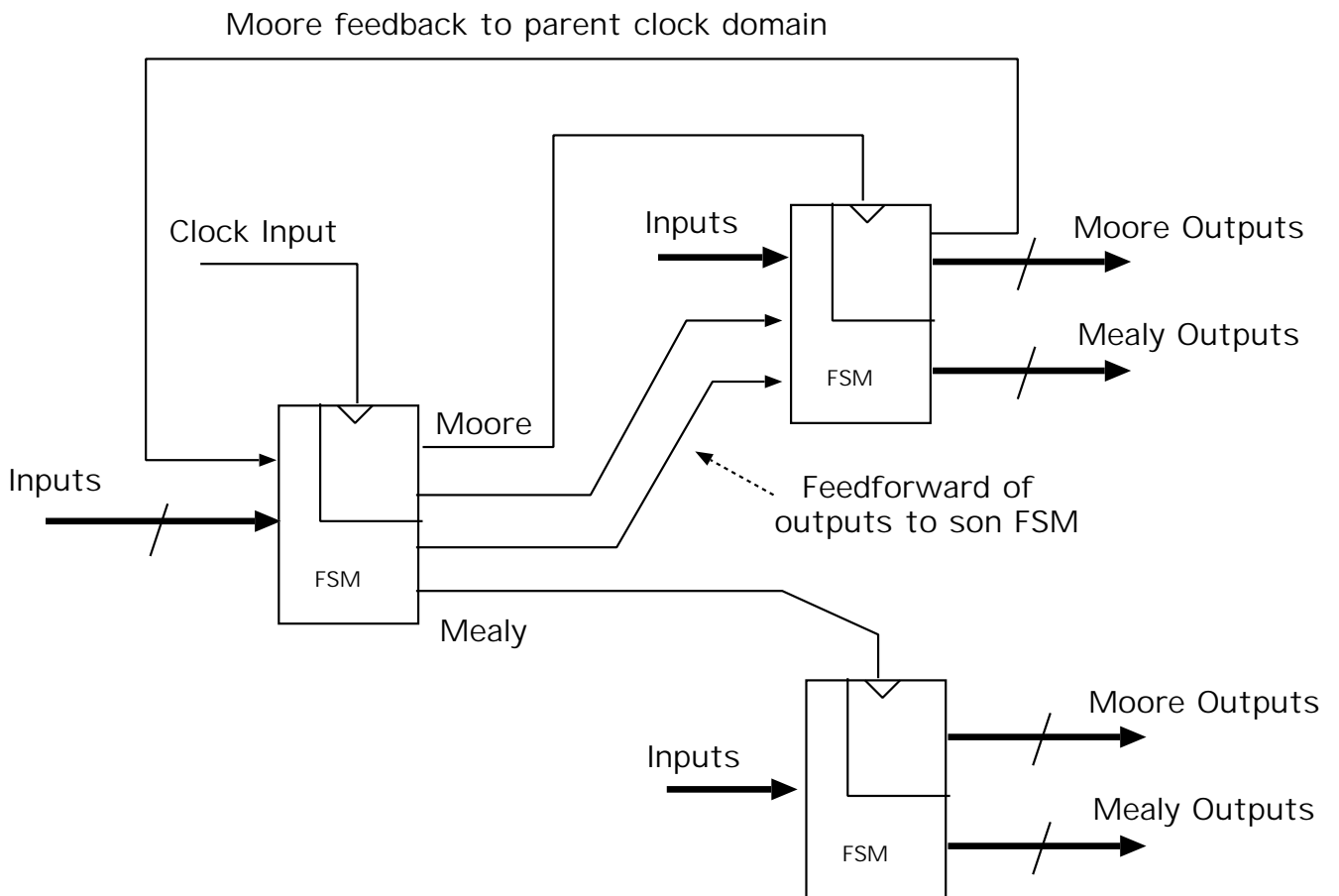


Dicing a wafer

 


(Chips are not always square)

 A chip in its package, ready for bond wires




IO and power pads

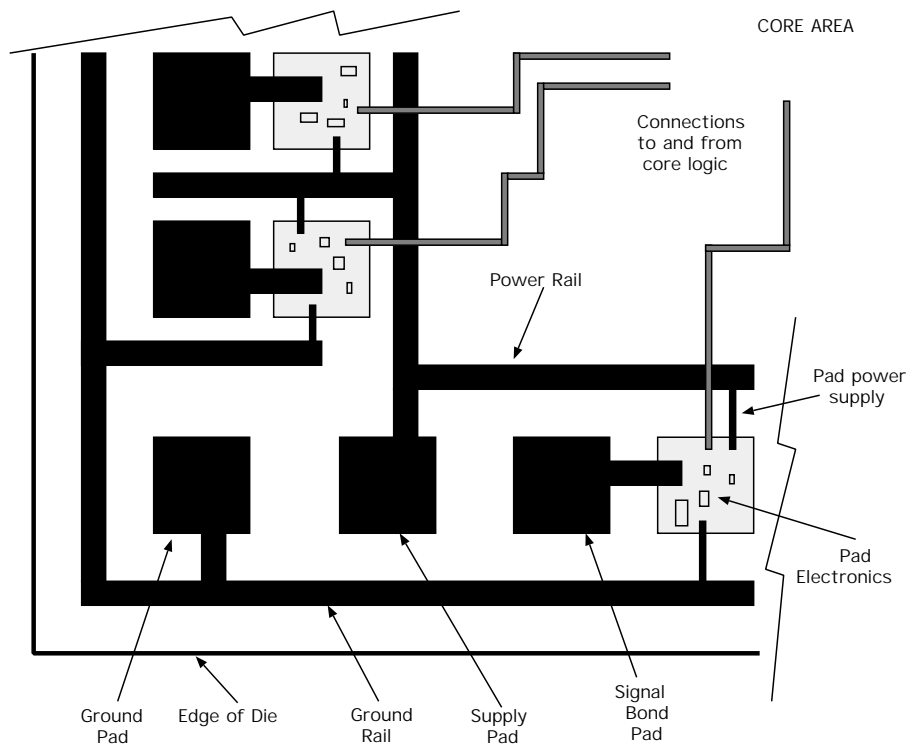


Die cost example

Area	Wafer dies	Working dies	Cost per working die
2	9000	8910	0.56
3	6000	5910	0.85
4	4500	4411	1.13
6	3000	2911	1.72
9	2000	1912	2.62
13	1385	1297	3.85
19	947	861	5.81
28	643	559	8.95
42	429	347	14.40
63	286	208	24.00
94	191	120	41.83
141	128	63	79.41
211	85	30	168.78
316	57	12	427.85
474	38	4	1416.89


A taxonomy of ICs

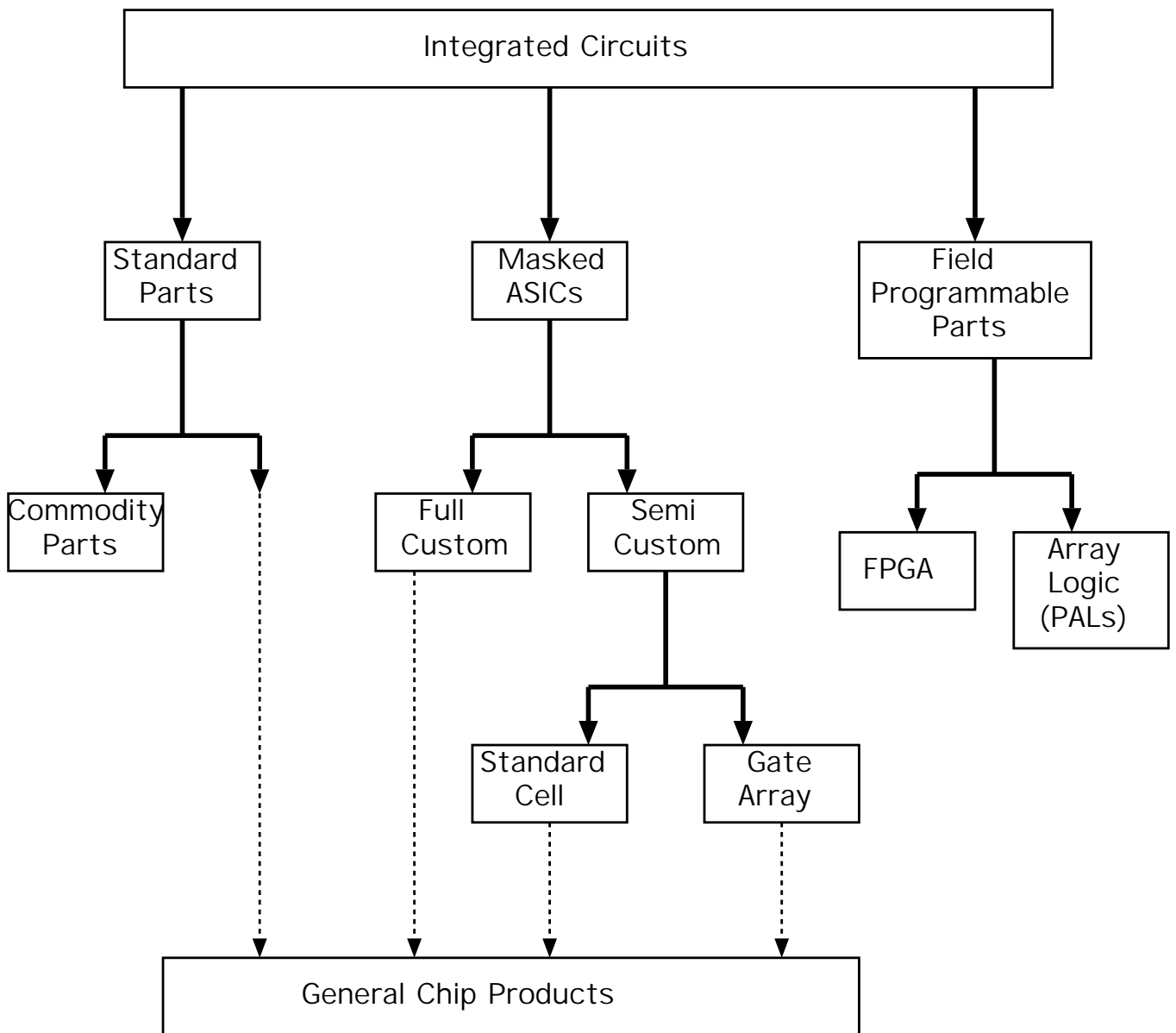


Field Programmable Gate Arrays

 


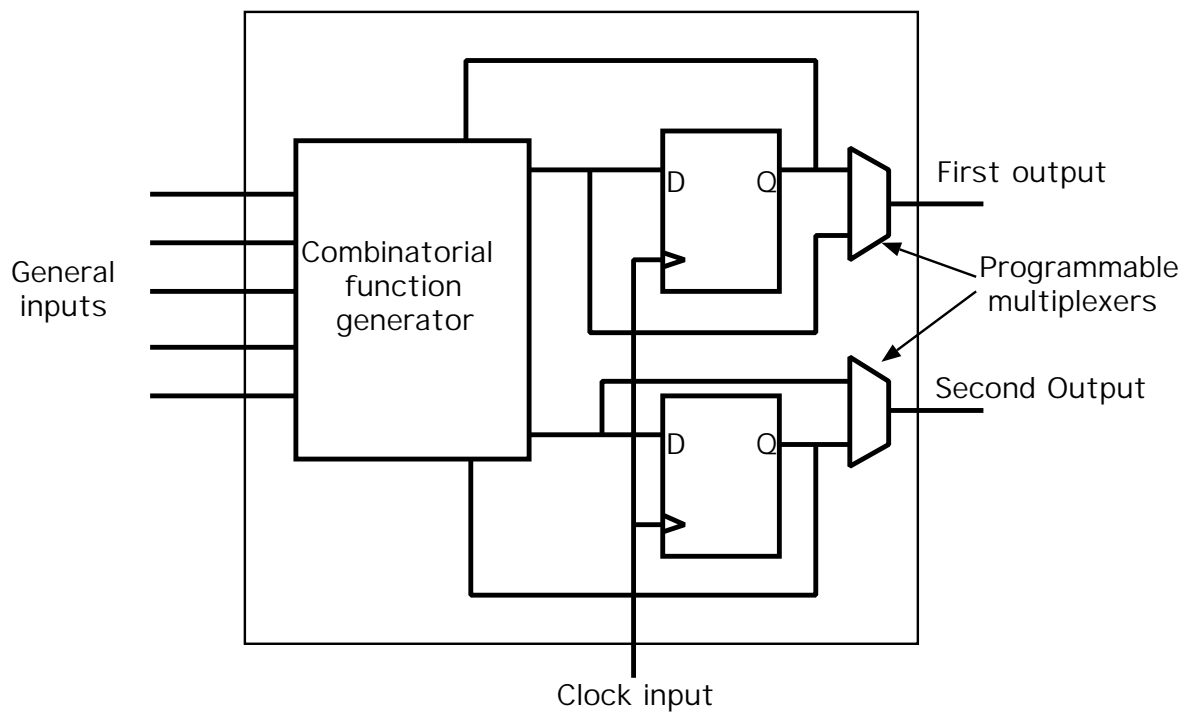A configurable logic block for a look-up-table based FPGA




A simple IO block FPGA

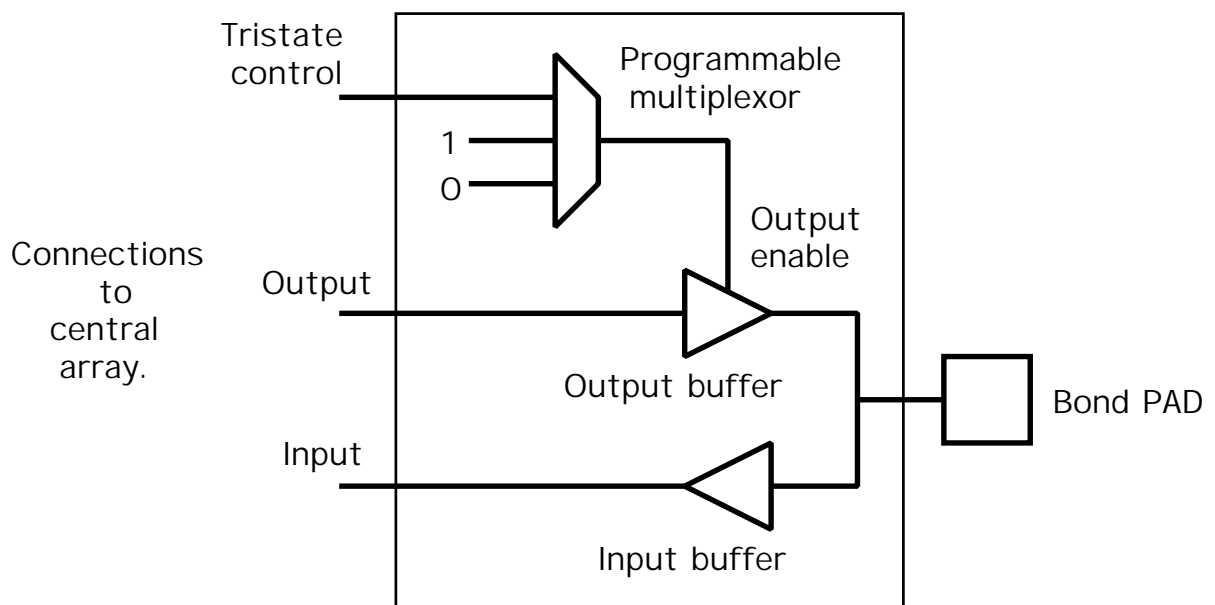

 

Contents of the PAL macrocell

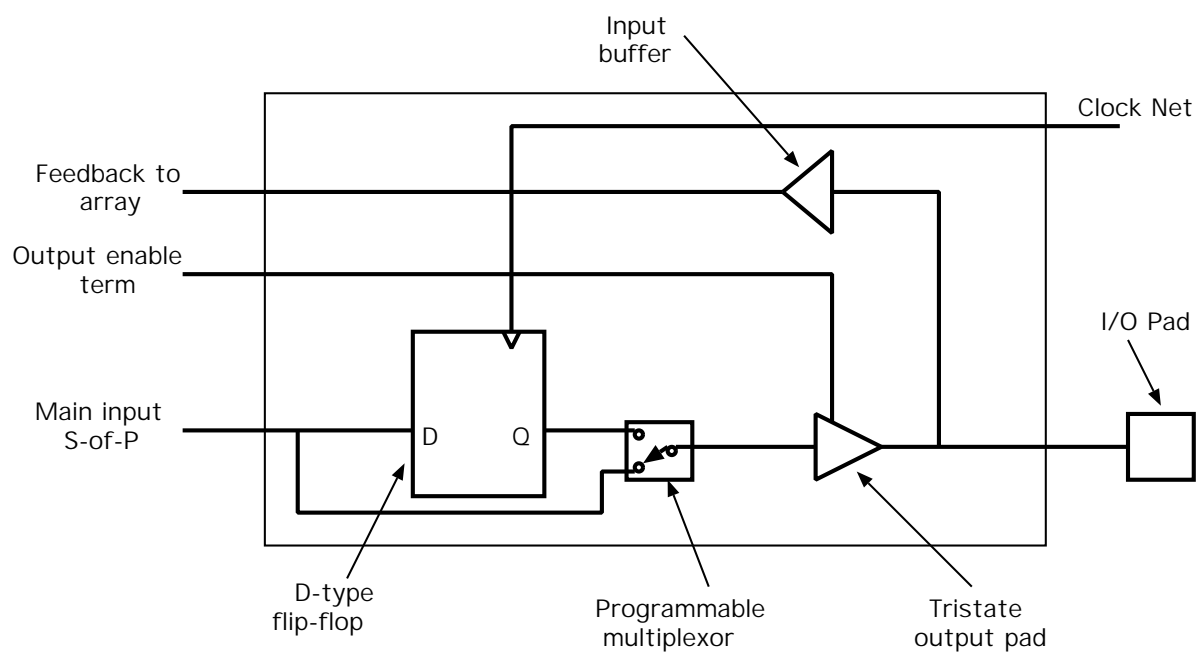


Example programming of a PAL showing only fuses for the top macrocell

```
pin 16 = o1;
pin 2 = a;
pin 3 = b;
pin 4 = c
```

```
o1.oe = ~a;
o1 = (b & o1) | c;
```


```
-x--  ----  ----  ----  ----  ----  ----  (oe term)
--x-  x---  ----  ----  ----  ----  ----  (pin 3 and 16)
----  ----  x---  ----  ----  ----  ----  (pin 4)
xxxx  xxxx  xxxx  xxxx  xxxx  xxxx  xxxx
xxxx  xxxx  xxxx  xxxx  xxxx  xxxx  xxxx
xxxx  xxxx  xxxx  xxxx  xxxx  xxxx  xxxx
xxxx  xxxx  xxxx  xxxx  xxxx  xxxx  xxxx
xxxx  xxxx  xxxx  xxxx  xxxx  xxxx  xxxx
x                                           (macrocell fuse)
```

 Delay-power style of technology comparison chart



technology	device	propagation delay (ns)	power (mW)	product (pJ)
CMOS	74hc00	7 ns	1 mW	7
TTL	74f00	3.4 ns	5 mW	17
ECL	sp92701	0.8 ns	200 mW	160

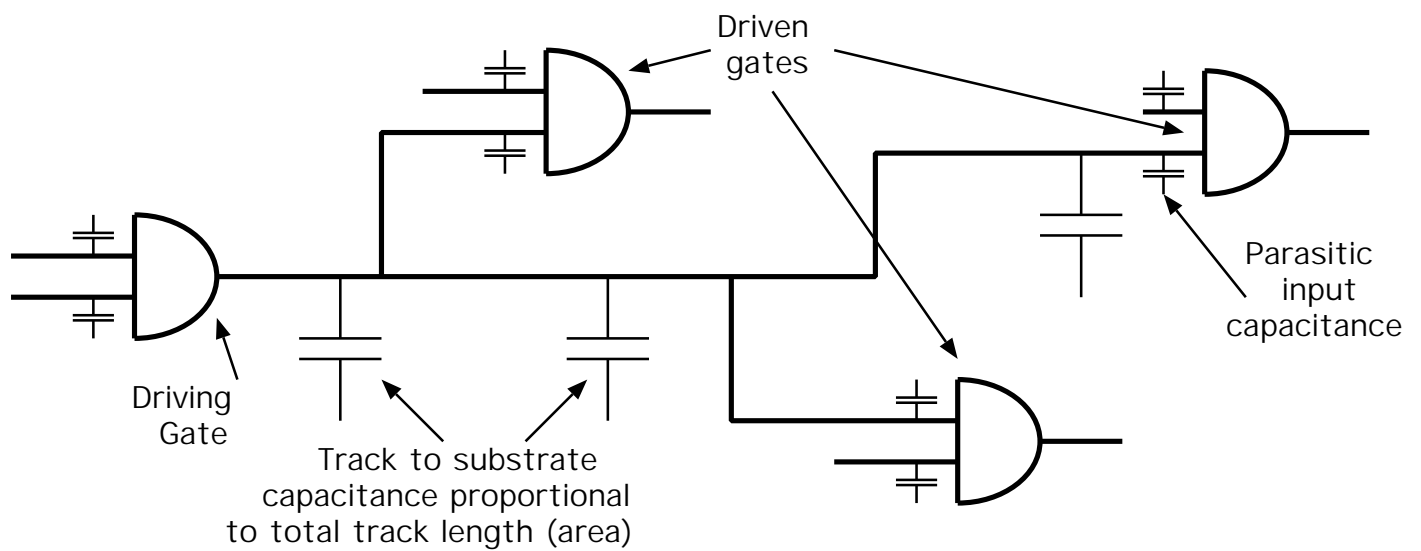Logic net with tracking and input load capacitances




An example cell from a manufacturer's cell library

NAND4 Standard Cell

Library: CBGO.5um

4 input NAND gate with x2 drive

Schematic Symbol

 

Simulator/HDL Call

NAND4X2(f, a, b, c, d);

Logical Function

$F = \text{NOT}(a \& b \& c \& d)$

ELECTRICAL SPECIFICATION

Switching characteristics : Nominal delays (25 deg C, 5 Volt, signal rise and fall 0.5 ns)

Inputs	Outputs	O/P Falling		O/P Rising	
		(ps)	ps/LU	ps	ps/LU
A	F	142	37	198	33
B	F	161	37	249	33
C	F	165	37	293	33
D	F	170	37	326	34

Min and Max delays depend upon temperature range, supply voltage, input edge speed and process spreads. The timing information is for guidance only. Accurate delays are used by the UDC.

CELL PARAMETERS : (One load unit = 49 fF)


Parameters	Pin	Value	Units
Input loading	a	2.1	Load units
	b	2.1	
	c	2.1	
	d	2.0	
Drive capability	f	35	Load units

Comparative view of digital logic technologies

Technology	Maximum clock speed	Maximum gate count	Maximum I/Os
GaAs bipolar	100 GHz	500	30
GaAs fet	30 GHz	10K	300
Si ECL	10 GHz	10M	500
Si CMOS	8 GHz	50M	1000
Within Si CMOS			
Full-custom	8 GHz	50M	1000
Standard cell	4 GHz	25M	1000
Gate array	2 GHz	5M	1000
FPGA	175 MHz	500K	800
CPLD	150 MHz	10K	200
PAL	200 MHz	500	60


Addition of two integers serially, I.s.b first

let $Y = a * 5$ in ...

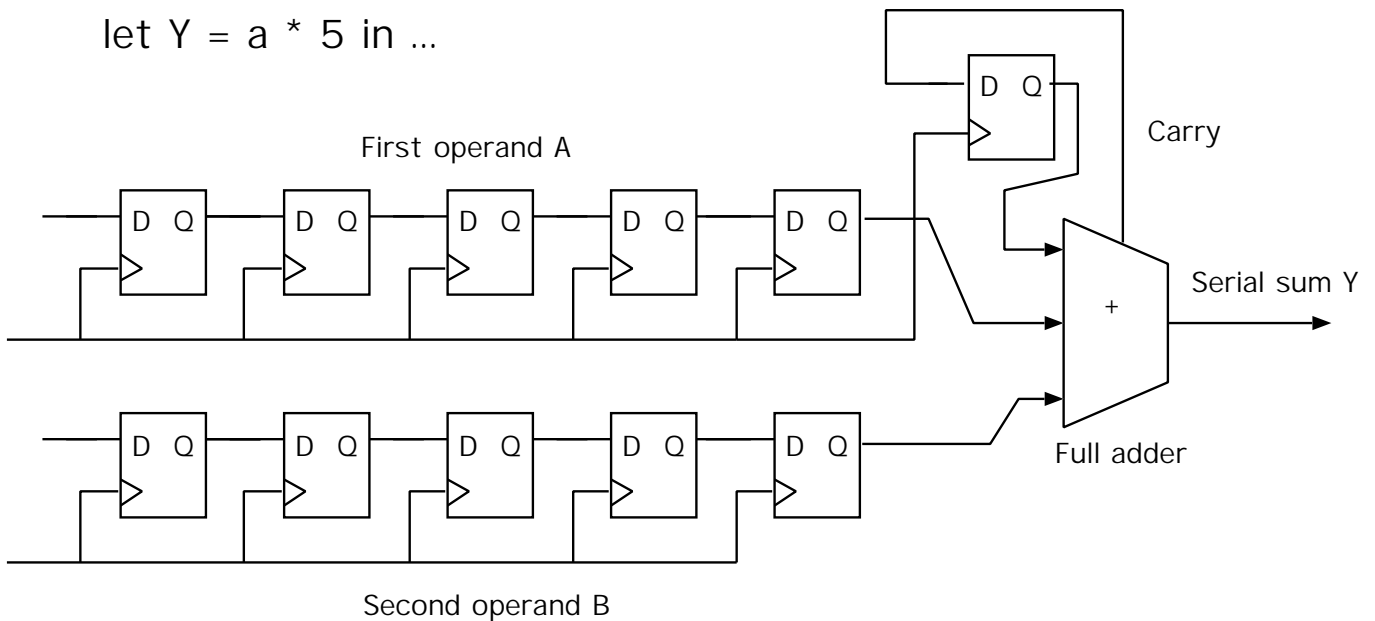


Bit-serial multiplication of an integer by a hardwired constant


let $y = a * 5$ in ...

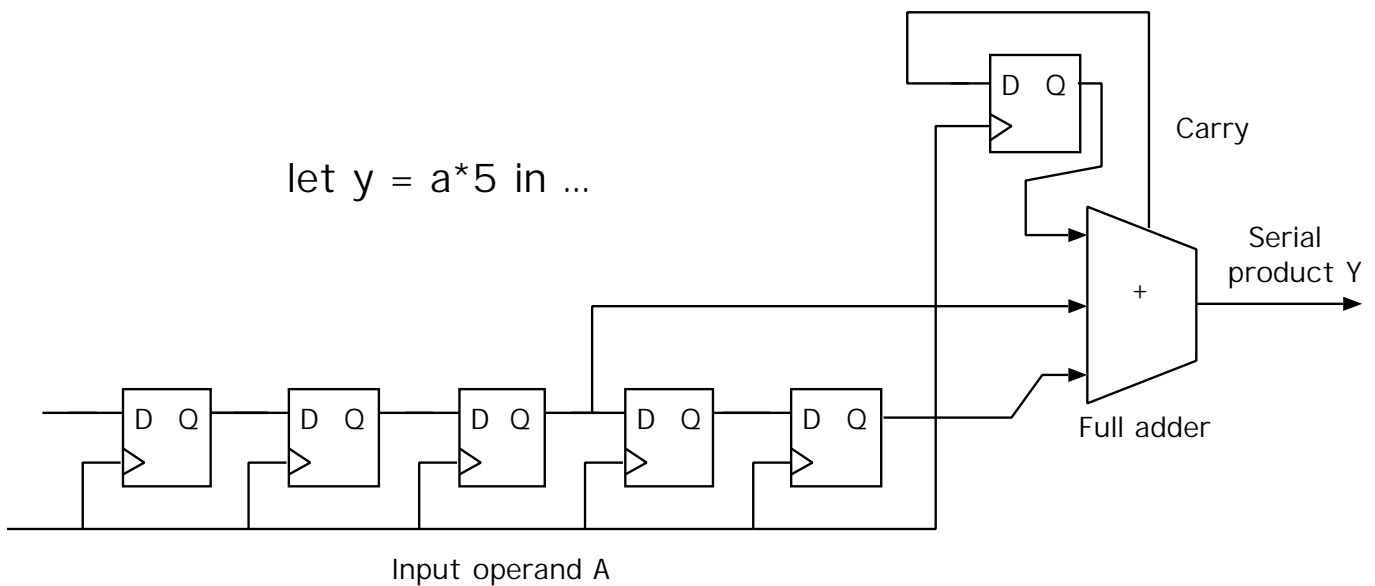

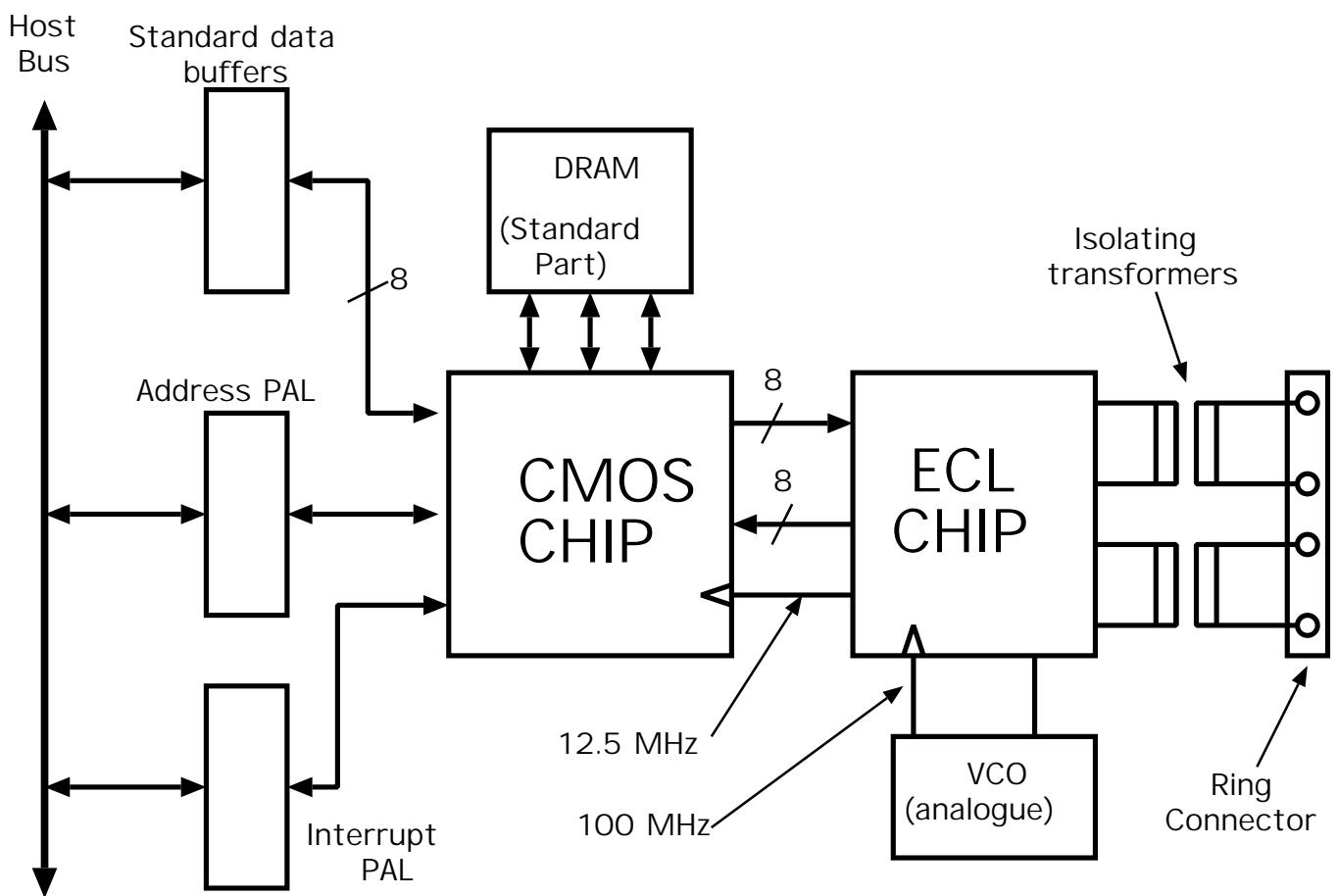
Design partitioning: The Cambridge Fast Ring




Design partitioning: An external modem

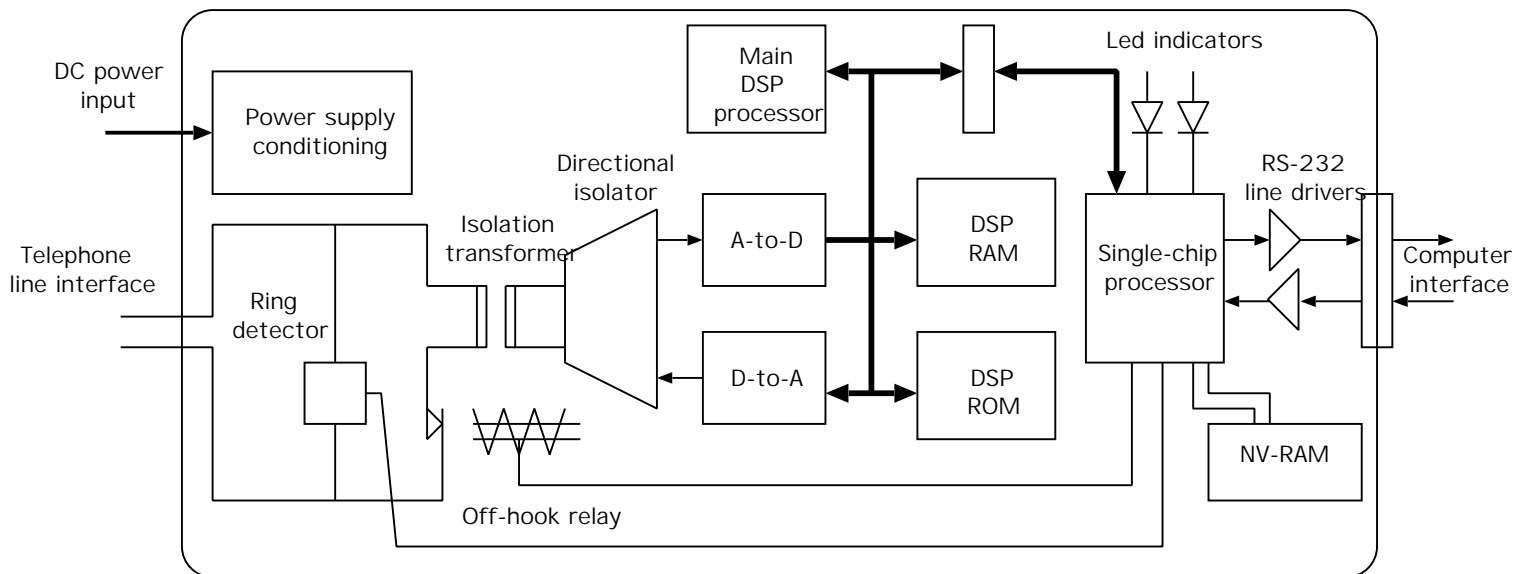

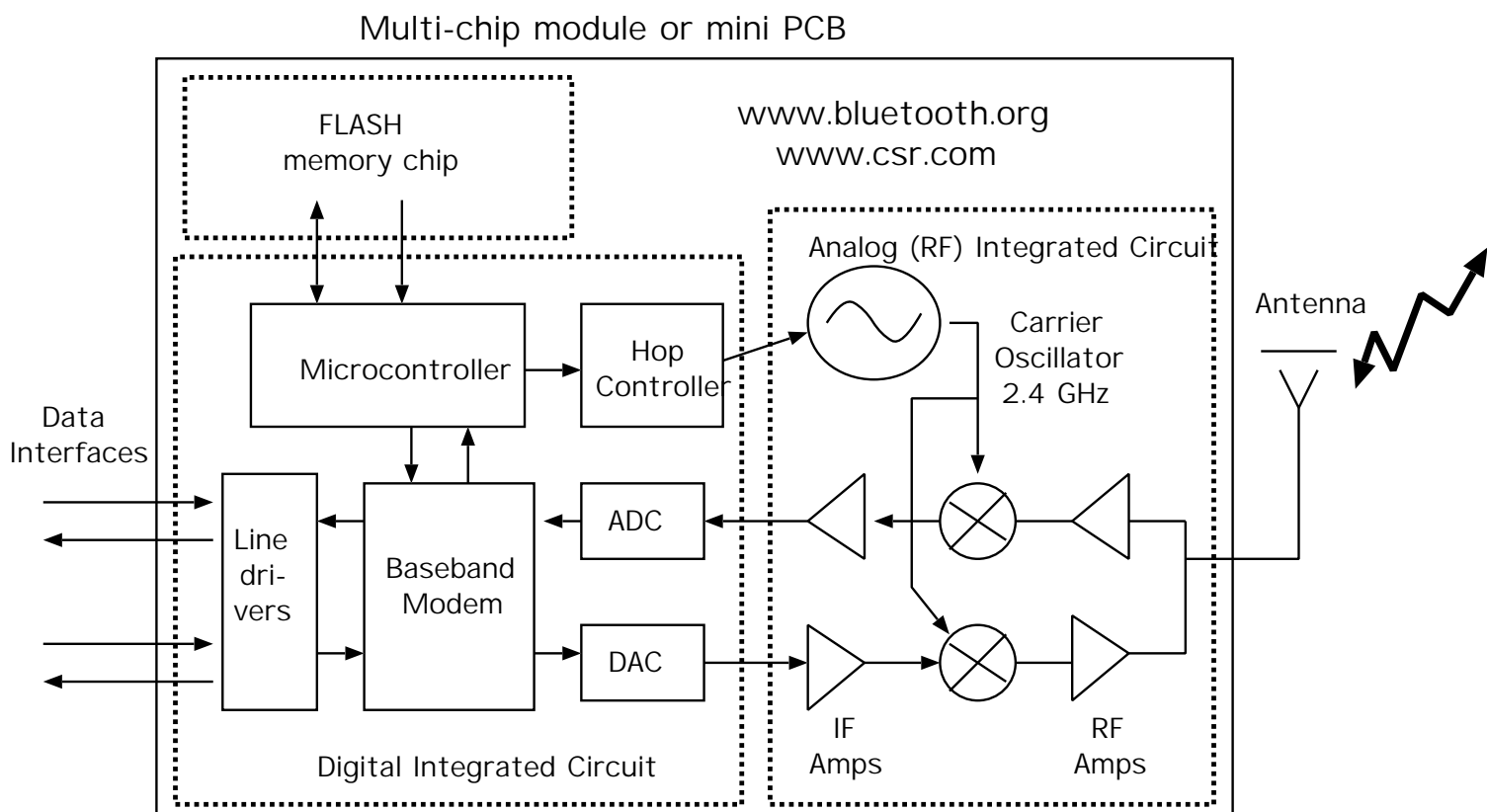
Design partitioning: A Miniature Radio Module




A simple edge detector

 


A Microcontroller

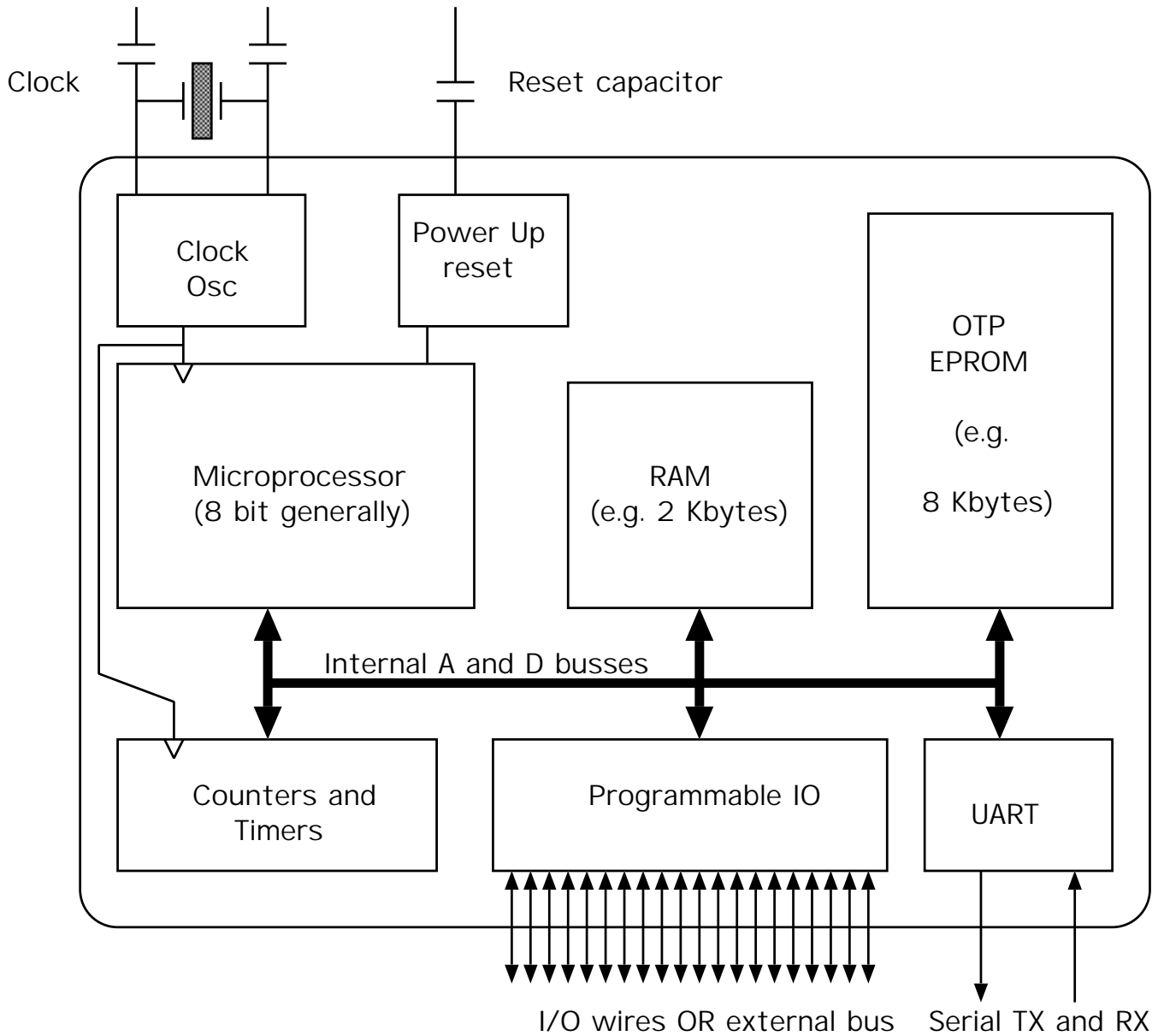

 
LEDs wired in a matrix to reduce external pin count




IR Handset Internal Circuit

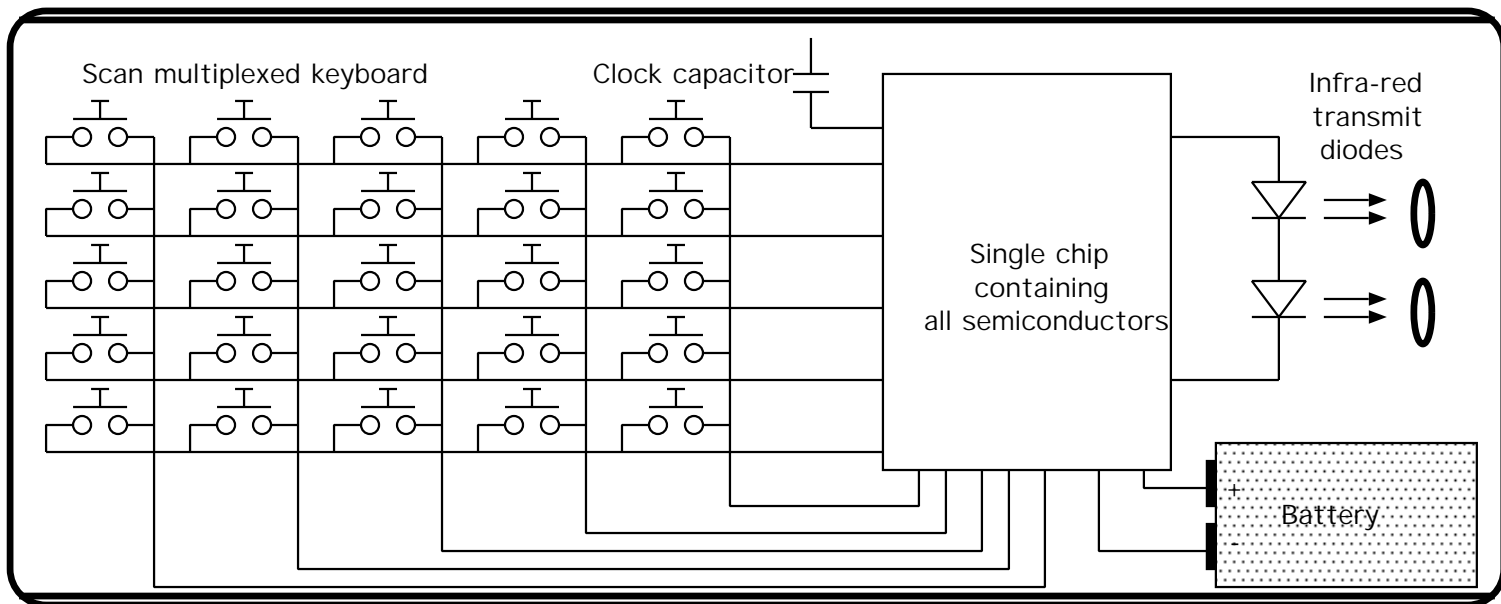

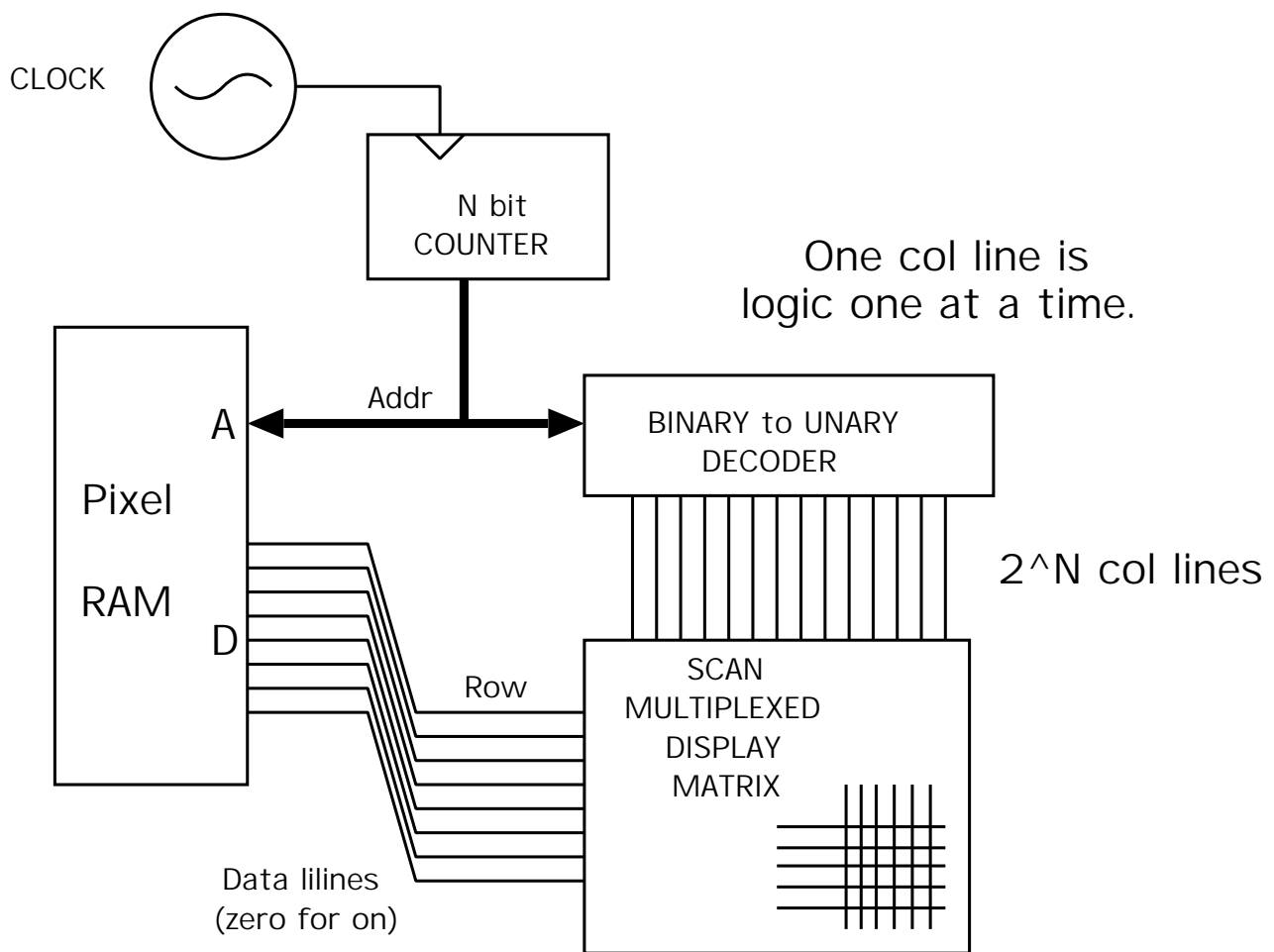
Scan multiplex logic for an LED pixel-mapped display





Addition of psudo dual-porting logic

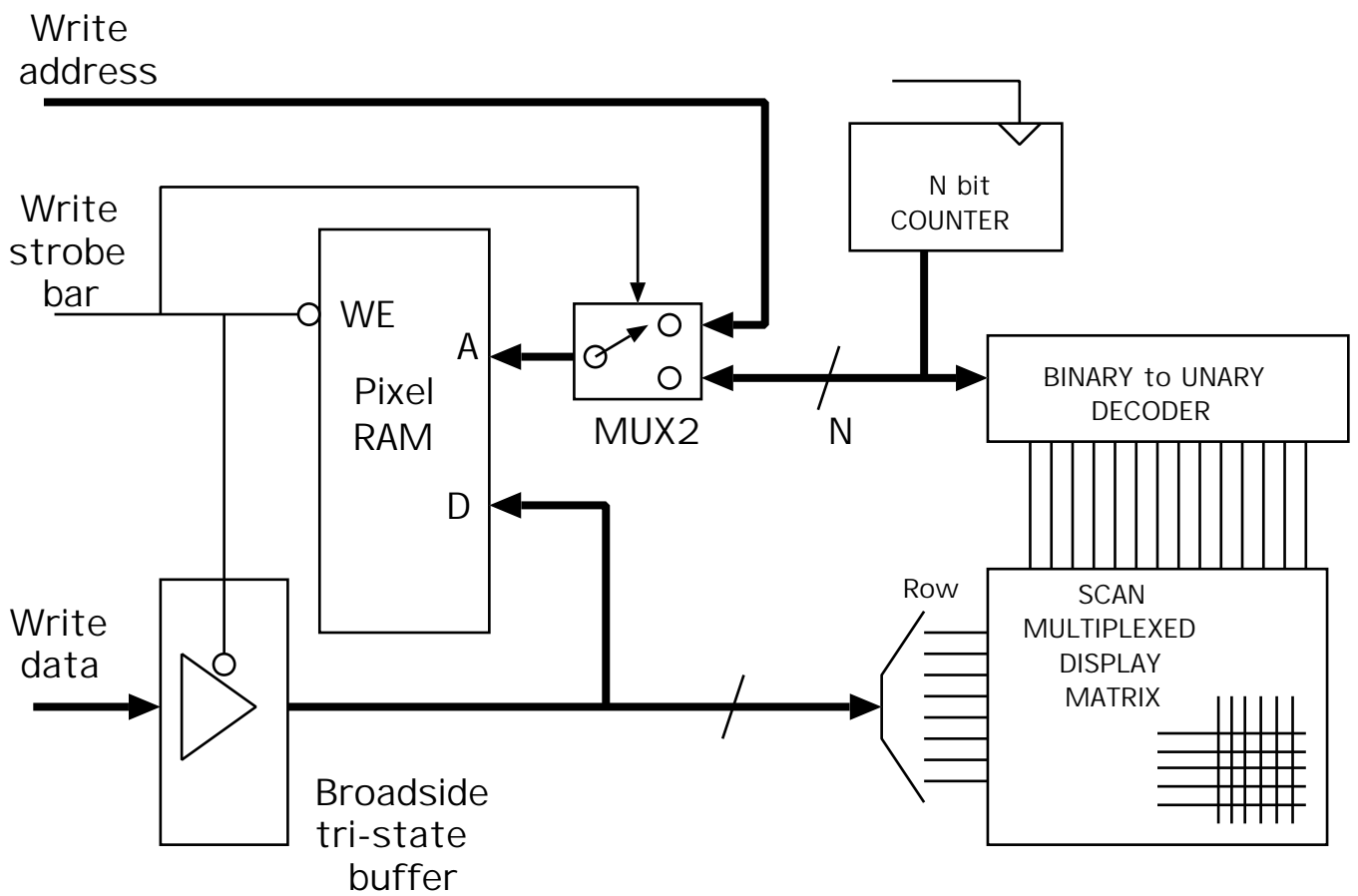



Use of a ROM as a function look-up table

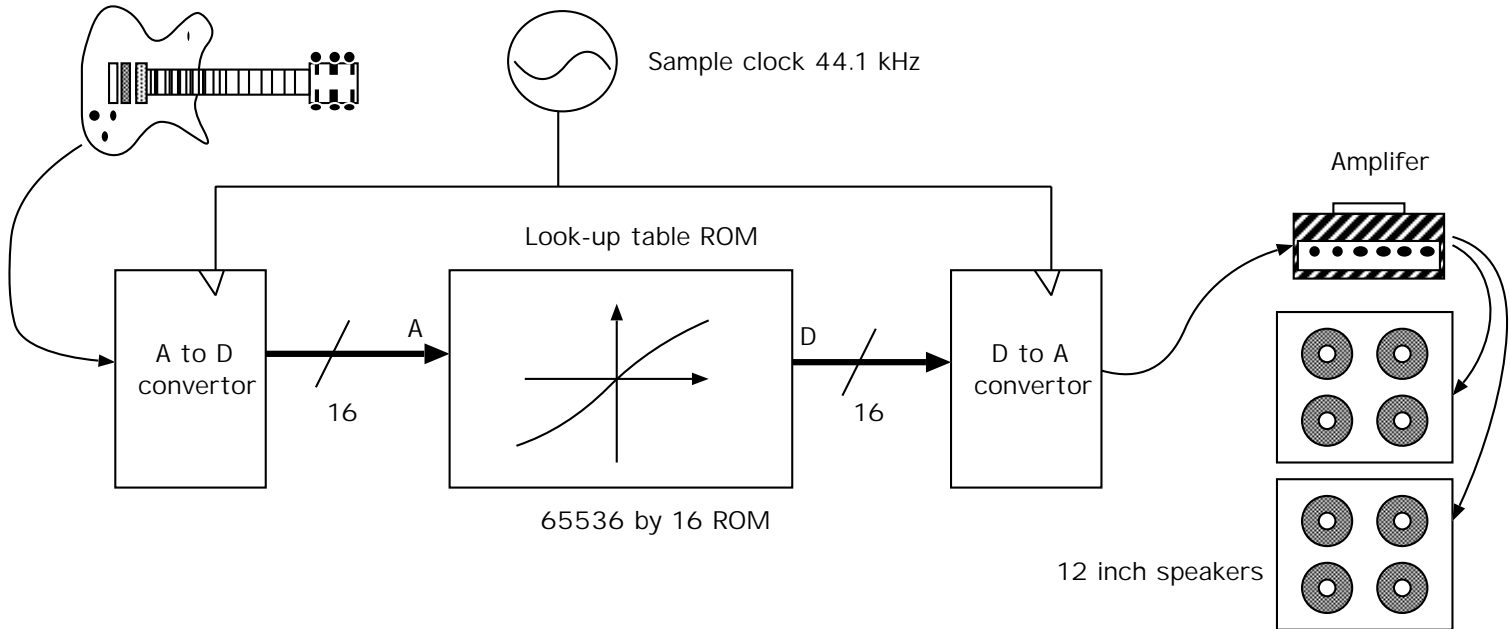

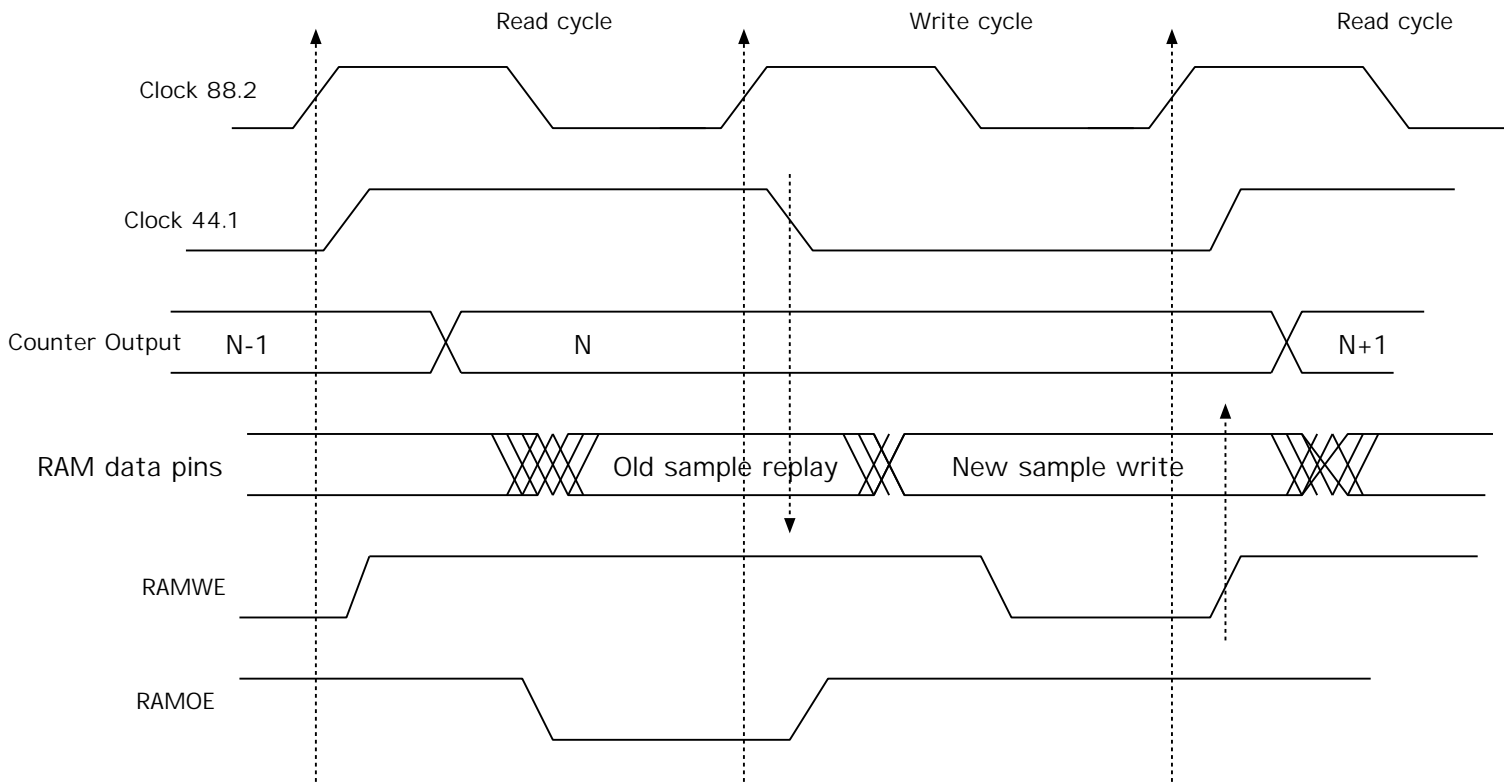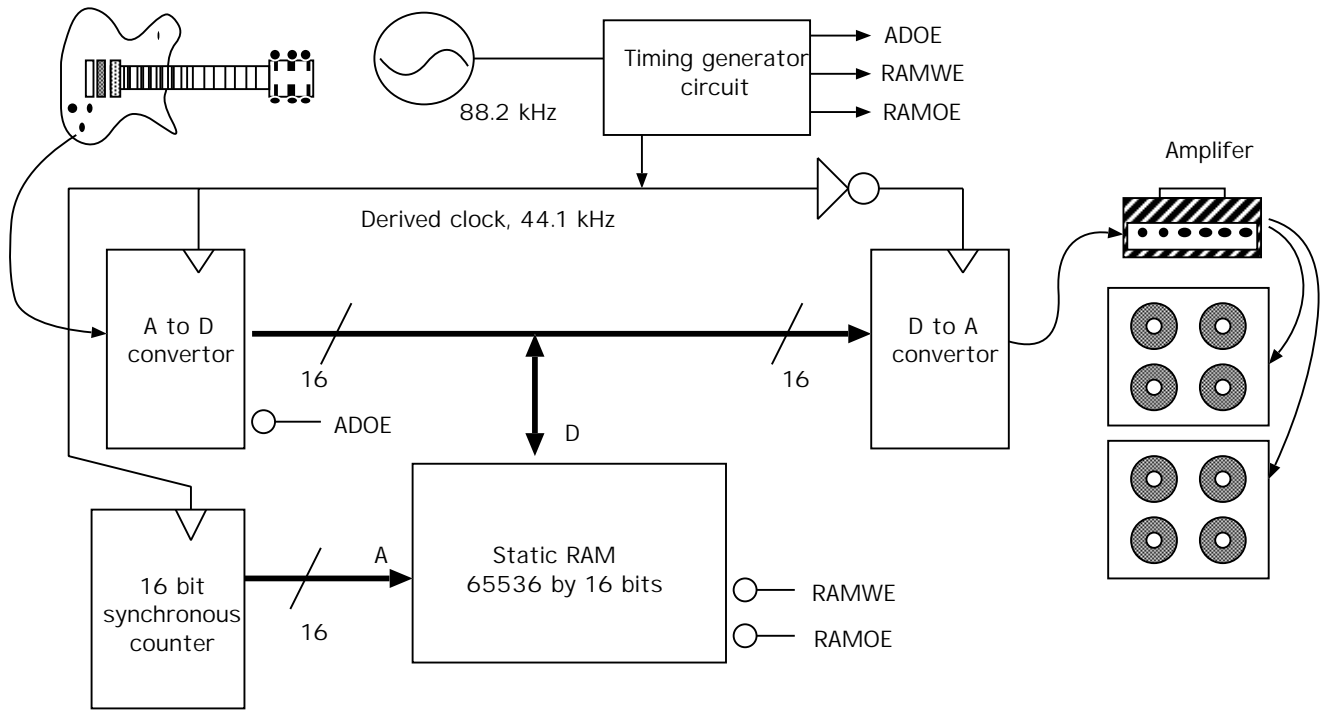Use of an SRAM to make the delay required for an echo unit




Merge unit block diagram

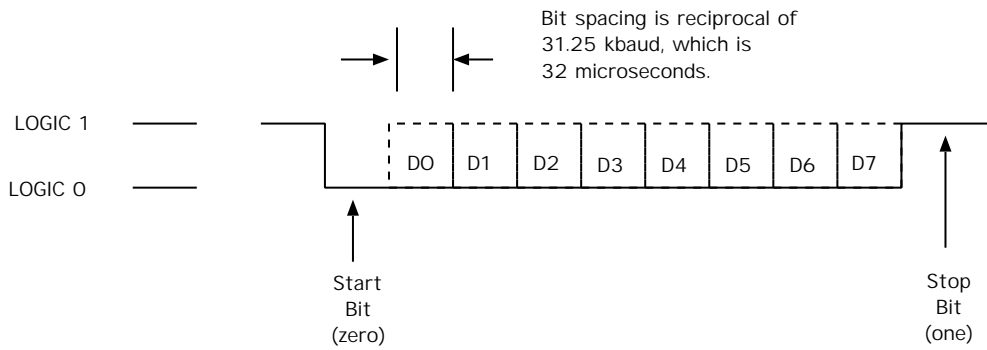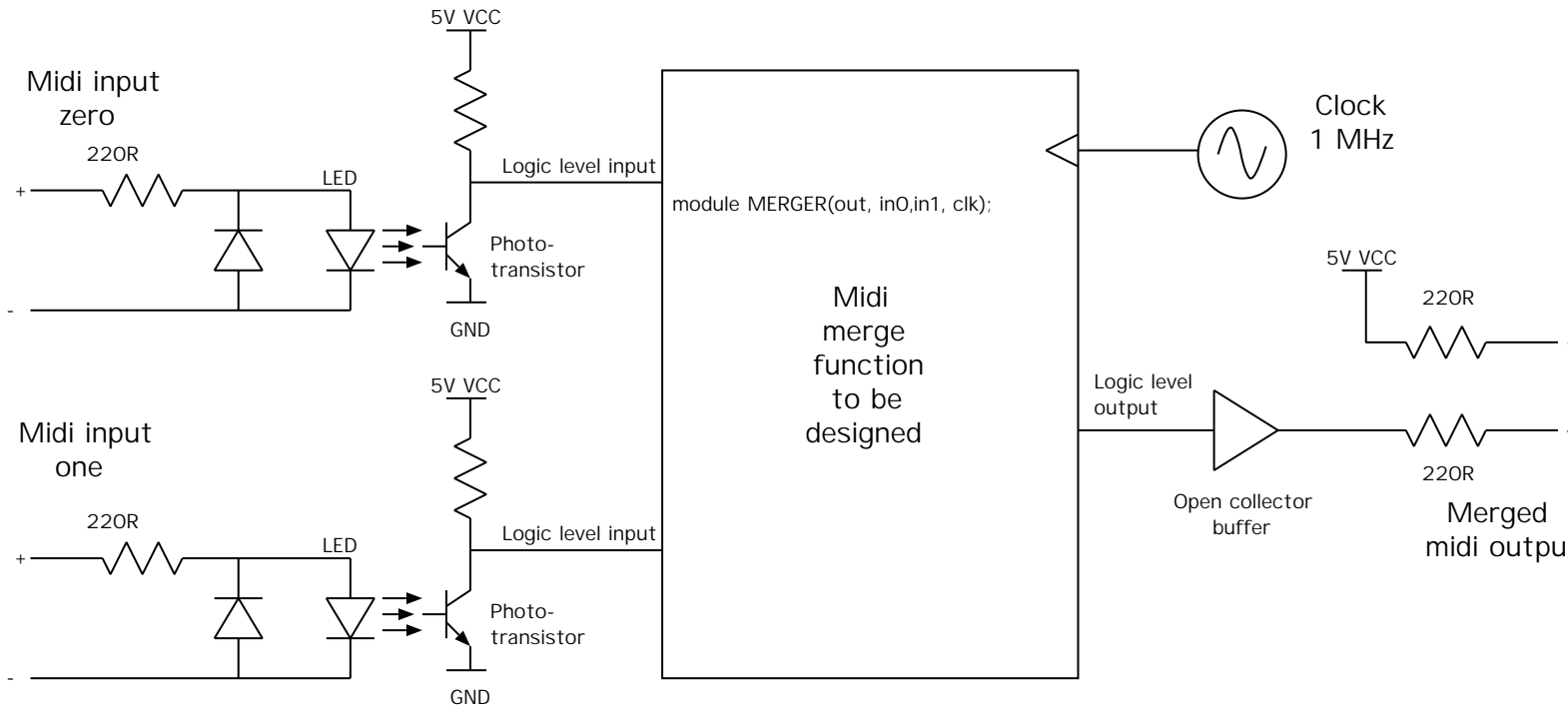

MIDI serial data format

- 9n kk vv (note on)
- 8n kk vv (note off)
- 9n kk 00 (note off with zero velocity)

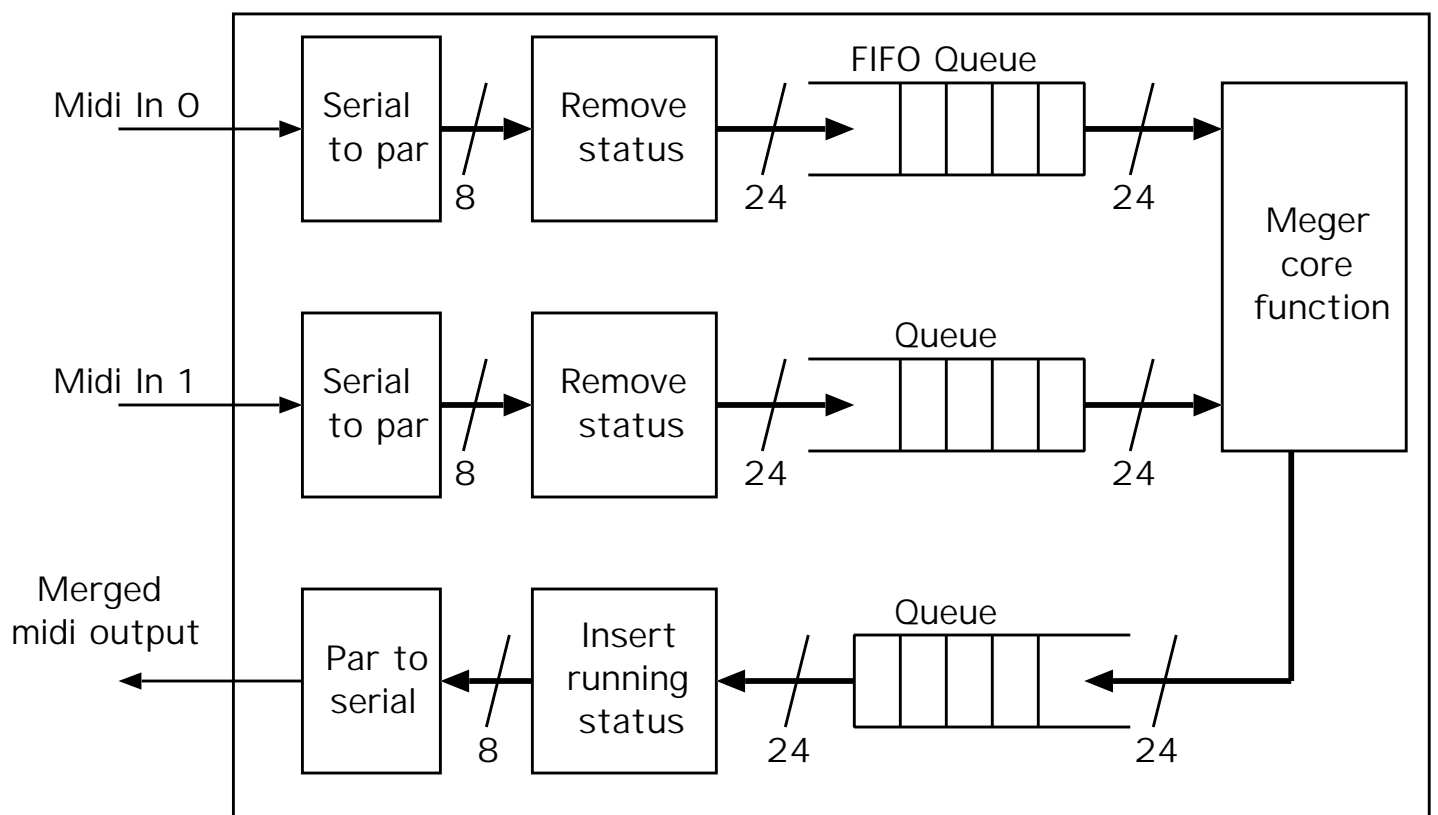MIDI merge unit internal functional units



The serial to parallel converter:

```
input clk;
output [7:0] pardata;    output guard;
```

The running status remover:

```
input clk;
input guard_in;    input [7:0] pardata_in;
output guard_out; output [23:0] pardata_out
```

For the FIFOs:

```
input clk;
input guard_in; input [7:0] pardata_in;
input read; output guard_out;    output [23:0] pardata_out;
input read; output guard_out;    output [23:0] pardata_out;
```

For the merge core unit:

```
input clk;
input guard_in0; input [23:0] pardata_in0; output read0;
input guard_in1; input [23:0] pardata_in1; output read1;
output guard_out; output [23:0] pardata_out;
input read; output guard_out;    output [23:0] pardata_out;
```

Status inserter / parallel to serial converter are
reverse of reciprocal units

Network Camera Node

