

## Example: Successive approximation analog to digital converter (ADC)

### Description of operation

A successive approximation ADC works by using a digital to analog converter (DAC) and a comparator to perform a binary search to find the input voltage.

A sample and hold circuit (S&H) is used to sample the analog input voltage and hold (i.e. keep a non-changing copy) the sampled value whilst the binary search is performed.


The binary search starts with the most significant bit (MSB) and works towards the least significant bit (LSB). For a 8-bit output resolution, 8 comparisons are needed in the binary search, taking at least 8 clock cycles.

The sample and hold circuit samples the analog input on a rising edge of the `sample` signal. The comparator output `cmp` is a logic 1 if the sampled analog voltage is greater than the output of the DAC, 0 otherwise.


The circuit in this example has two control signals `go` and `done`. At any point if `go` is 0 the circuit is reset. When `go` becomes a 1 the process of sampling and converting takes place. When a conversion is finished `valid` is set to 1 and the result is available.

Of relevance to the ECAD course is the state machine controlling this process.

## Block diagram

 

## State diagram

 

## Verilog description

```
// ADC controller
module controller(clk,go,valid,result, sample,value,cmp);
    input      clk; // clock input
    input      go; // go=1 to perform conversion
    output     valid; // valid=1 when conversion finished
    output [7:0] result; // 8 bit result output
    output     sample; // to S&H circuit
    output [7:0] value; // to DAC
    input      cmp; // from comparitor

    reg      [1:0] state; // current state in state machine
    reg      [7:0] mask; // bit to test in binary search
    reg      [7:0] result; // hold partially converted result

    // state assignment
    parameter sWait=0, sSample=1, sConv=2, sDone=3;

    // synchronous design
    always @(posedge clk) begin

        if (!go) state <= sWait; // stop and reset if go=0
        else case (state)           // choose next state in state machine
            sWait   : state <= sSample;
            sSample :
                begin                  // start new conversion so
                    state <= sConv;       // enter convert state next
                    mask   <= 8'b10000000; // reset mask to MSB only
                    result <= 8'b0;        // clear result
                end
            sConv   :
                begin
                    // set bit if comparitor indicates input larger than
                    // value currently under consideration, else leave bit clear
                    if (cmp) result <= result | mask;
                    // shift mask to try next bit next time
                    mask <= mask>>1;
                    // finished once LSB has been done
                    if (mask[0]) state <= sDone;
                end
            sDone   :";
        endcase
    end

    assign sample = state==sSample; // drive sample and hold
    assign value  = result | mask; // (result so far) OR (bit to try)
    assign valid  = state==sDone; // indicate when finished
endmodule
```

## Example of Verilog simulation testbench

(Note: This simulation code requires a simulator which supports such features.)

```
module testbench();

// registers to hold inputs to circuit under test, wires for outputs
reg clk,go;
wire valid,sample,cmp;
wire [7:0] result;
wire [7:0] value;

// instance controller circuit
controller c(clk,go,valid,result, sample,value,cmp);

// generate a clock with period of 20 time units
always begin
    #10;
    clk=~clk;
end
initial clk=0;

// simulate analogue circuit with a digital model
reg [7:0] hold;
always @ (posedge sample) hold = 8'b01000110;
assign cmp = ( hold >= value);

// monitor some signals and provide input stimuli
initial begin
    $monitor($time, " go=%b valid=%b result=%b sample=%b value=%b cmp=%b
                      state=%b mask=%b",
              go,valid,result,sample,value,cmp,c.state,c.mask);
    #100; go=0;
    #100; go=1;
    #5000; go=0;
    #5000; go=1;
    #40;   go=0;
    #5000;
    $stop;
end

endmodule
```

## Verilog simulation output

Note the use of x for undefined values.

```
0 go=x valid=x result=xxxxxxxx sample=x value=xxxxxxxx
  cmp=x state=xx mask=xxxxxxxx
100 go=0 valid=x result=xxxxxxxx sample=x value=xxxxxxxx
  cmp=x state=xx mask=xxxxxxxx
110 go=0 valid=0 result=xxxxxxxx sample=0 value=xxxxxxxx
  cmp=x state=00 mask=xxxxxxxx
200 go=1 valid=0 result=xxxxxxxx sample=0 value=xxxxxxxx
  cmp=x state=00 mask=xxxxxxxx
210 go=1 valid=0 result=xxxxxxxx sample=1 value=xxxxxxxx
  cmp=x state=01 mask=xxxxxxxx
230 go=1 valid=0 result=00000000 sample=0 value=10000000
  cmp=0 state=10 mask=10000000
250 go=1 valid=0 result=00000000 sample=0 value=01000000
  cmp=1 state=10 mask=01000000
270 go=1 valid=0 result=01000000 sample=0 value=01100000
  cmp=0 state=10 mask=00100000
290 go=1 valid=0 result=01000000 sample=0 value=01010000
  cmp=0 state=10 mask=00010000
310 go=1 valid=0 result=01000000 sample=0 value=01001000
  cmp=0 state=10 mask=00001000
330 go=1 valid=0 result=01000000 sample=0 value=01000100
  cmp=1 state=10 mask=00000100
350 go=1 valid=0 result=01000100 sample=0 value=01000110
  cmp=1 state=10 mask=00000010
370 go=1 valid=0 result=01000110 sample=0 value=01000111
  cmp=0 state=10 mask=00000001
390 go=1 valid=1 result=01000110 sample=0 value=01000110
  cmp=1 state=11 mask=00000000
5200 go=0 valid=1 result=01000110 sample=0 value=01000110
  cmp=1 state=11 mask=00000000
5210 go=0 valid=0 result=01000110 sample=0 value=01000110
  cmp=1 state=00 mask=00000000
10200 go=1 valid=0 result=01000110 sample=0 value=01000110
  cmp=1 state=00 mask=00000000
10210 go=1 valid=0 result=01000110 sample=1 value=01000110
  cmp=1 state=01 mask=00000000
10230 go=1 valid=0 result=00000000 sample=0 value=10000000
  cmp=0 state=10 mask=10000000
10240 go=0 valid=0 result=00000000 sample=0 value=10000000
  cmp=0 state=10 mask=10000000
10250 go=0 valid=0 result=00000000 sample=0 value=10000000
  cmp=0 state=00 mask=10000000
```

Note that at time 390 the result output is the same as the value loaded into the sample and hold model in the test bench circuit.