

## 1995 Paper 8 Question 12

### Specification and Verification II

Describe the technique of exhaustive enumeration and discuss its rôle in formal proofs of correctness. [5 marks]

The non-equality of two boolean streams, **a** and **b**, is defined as follows:

$$\begin{aligned} \text{NotEqual } 0 \text{ (a,b) = F) } \wedge \\ \text{NotEqual(t+1) (a,b) = } (\neg(\text{a t} = \text{b t}) \rightarrow \text{T} \mid \text{NotEqual t (a,b)}) \end{aligned}$$

Using basic gates and a register with the following behaviour

$$\text{REG(in,out) = } (\forall \text{t. out t = } ((\text{t} = 0) \rightarrow \text{F} \mid \text{in}(\text{t} - 1)))$$

devise and verify a circuit with inputs **a** and **b** and an output, **out**, which satisfies the following behaviour:  $\forall \text{t. out t = NotEqual t (a,b)}$  [15 marks]