

## 2000 Paper 4 Question 5

### ECAD

A naïve Verilog programmer has made two attempts at implementing a `RandomBits` module. The module is supposed to generate a pseudo-random sequence of bits.

```
module RandomBitsA( rand_bits );
    output rand_bits;
    wire [3:0] shift_reg;
    wire newbit = ~(shift_reg[3] ^ shift_reg[1] ^ shift_reg[0]);
    assign shift_reg[3] = shift_reg[2];
    assign shift_reg[2] = shift_reg[1];
    assign shift_reg[1] = shift_reg[0];
    assign shift_reg[0] = newbit;
    assign rand_bits = newbit;
endmodule
```

```
module RandomBitsB( clk, rand_bits );
    input clk;
    output rand_bits;
    reg [3:0] shift_reg;
    wire newbit = ~(shift_reg[3] ^ shift_reg[1] ^ shift_reg[0]);
    always @(posedge clk) begin
        shift_reg[3] <= shift_reg[2];
        shift_reg[2] <= shift_reg[1];
        shift_reg[1] <= shift_reg[0];
        shift_reg[0] <= newbit;
    end
    assign rand_bits = newbit;
endmodule
```

```
// TestRandom is the top level module
module TestRandom( clk, tstA, tstB );
    input clk; // input clock
    output tstA, tstB; // output test bits
    RandomBitsA randa( tstA );
    RandomBitsB randb( clk, tstB );
endmodule
```

- (a) In Verilog, what is the difference between continuous assignment and non-blocking assignment? [4 marks]
- (b) What are the circuit diagrams corresponding to `RandomBitsA` and `RandomBitsB`? [8 marks]
- (c) What is the output from `RandomBitsA` and `RandomBitsB`? [8 marks]