

## 2003 Paper 9 Question 2

### VLSI Design

Explain the operation of ripple carry and carry-skip in a binary adder. [4 marks]

Assuming a delay of  $\tau$  for each stage of combinational logic (consisting of negation, product and sum), estimate the delays involved in calculating the most significant bit of the sum and the final carry-out of an  $n$ -bit adder using

(a) ripple carry

(b) carry-skip arranged in  $b$  blocks of  $k$  bits. [4 marks]

What block size minimises the overall delay for a carry-skip adder? [2 marks]

Explain how a variable block size can reduce the overall delay. Compare the delays for a 64-bit adder using fixed and variable block sizes. [4 marks]

An alternative approach is to build a hierarchy of skip units in the style of a carry-lookahead tree. Derive equations for the skip units and estimate the delay in a 64-bit adder arranged as two 4-bit blocks, three groups of four 4-bit blocks (where each group has a higher level skip), and a further two 4-bit blocks. [6 marks]