

2006 Paper 3 Question 1

ECAD

- (a) In the Verilog hardware description language, what is the difference between *continuous*, *blocking* and *non-blocking* assignments? [6 marks]
- (b) What is the labelled circuit diagram which corresponds to the following snippet of Verilog? [3 marks]

```
reg [1:0] s;
wire t;
always @(posedge clk) s <= {s[0],t};
```

- (c) A naïve programmer has written the following Verilog module to sort two 4-bit values *a* and *b* such that $a < b$.

```
module sort2(clk,a,b);
  input clk;
  input [4:0] a;
  input [4:0] b;
  wire [4:0] t;
  always @(clk) begin
    if(a>b) begin
      t <= a;
      a <= b;
      b <= t;
    end
  end
endmodule
```

- (i) What is wrong with the code above? [6 marks]
- (ii) How would you correct this module so that it takes two values as input and outputs the sorted values one clock cycle later? [5 marks]