

COMPUTER SCIENCE TRIPOS Part IB – 2017 – Paper 3


7 Prolog (ARB)

- (a) Define `and/3` to model an AND gate, using 0 and 1 to mean “false” and “true” respectively. [2 marks]
- (b) A definition of `or/3` is shown on the left, and a query’s result on the right:

<pre>or(0,0,0). or(_,_,1).</pre>	<pre>?- or(0,0,Result). Result = 0 ; Result = 1.</pre>
----------------------------------	--

Explain this output, and correct `or/3` without increasing the number of clauses. [3 marks]

 - (c) Define `xor/3` using two rules. [2 marks]
- (d) Define `full_adder(A, B, CIn, COut, S)` to implement the following circuit. [5 marks]



- (e) Define `zip(InList1, InList2, OutList)` such that if `InList1` is `[1,3,...]` and `InList2` is `[2,4,...]` then `OutList` must be `[[1,2],[3,4],...]`. [2 marks]
- (f) Define `ripple_carry_adder(N, Inputs, CIn, COut, Result)` to cascade `N` calls to `full_adder/5`. Assume that we obtain parameter `Inputs` through `zip(X, Y, Inputs)` to add two `N`-bit values `X` and `Y`. In your answer take the most significant bit to be on the *right*. Thus you should expect to see:

```
?- ripple_carry_adder(2, [[1,1], [0,0]], 0, Cout, S).
Cout = 0, S = [0, 1].
?- ripple_carry_adder(2, [[0,0], [1,0]], 0, Cout, S).
Cout = 0, S = [0, 1].
?- ripple_carry_adder(2, [[0,0], [1,1]], 0, Cout, S).
Cout = 1, S = [0, 0]. [2 marks]
```

- (g) Define the predicate `test(X,Y,N)` which tests `ripple_carry_adder/5` against Prolog’s built-in addition function for up to `N` bits of precision, that is, fixed width `test(X,Y,N)` fails if overflow occurs (i.e., the carry bit is set). You may assume you are given predicates `dec2bin(Dec,BinList)` and `bin2dec(BinList,Dec)` for converting between integers and lists of bits, and `length(List,N)` which relates lists with their lengths. [4 marks]