

# Simulation semantics (a.k.a. event semantics)

- ▶ HDLs use *discrete event simulation*
  - ▶ changes to variables  $\Rightarrow$  threads enabled
  - ▶ enabled threads executed non-deterministically
  - ▶ execution of threads  $\Rightarrow$  more events

- ▶ Combinational thread:

```
always @(v1 or ... or vn) v := E
```

- ▶ enabled by any change to  $v_1, \dots, v_n$

- ▶ Positive edge triggered sequential threads:

```
always @(posedge clk) v := E
```

- ▶ enabled by  $clk$  changing to  $\mathbb{T}$


- ▶ Negative edge triggered sequential threads:

```
always @(negedge clk) v := E
```

- ▶ enabled by  $clk$  changing to  $\mathbb{F}$
 
# Simulation

- ▶ Given
  - ▶ a set of threads
  - ▶ initial values for variables read or written by threads
  - ▶ a sequence of input values  
(inputs are variables not in LHS of assignments)
- ▶ *simulation algorithm*  $\Rightarrow$  a sequence of states



- ▶ Simulation is non-deterministic

## Combinational threads in series



- ▶ HDL-like specification:

`always @ (in) l1 := f(in) ..... thread T1`


`always @ (l1) l2 := g(l1) ..... thread T2`

`always @ (l2) out := h(l2) ..... thread T3`


- ▶ Suppose `in` changes to `x` at simulation time `t`
  - ▶ T1 will become enabled and assign `f(x)` to `l1`
  - ▶ if `l1`'s value changes then T2 will become enabled (still simulation time `t`)
  - ▶ T2 will assign `g(f(x))` to `l2`
  - ▶ if `l2`'s value changes then T3 will become enabled (still simulation time `t`)
  - ▶ T3 will assign `h(g(f(x)))` to `out`
  - ▶ simulation quiesces (still simulation time `t`)
- ▶ Steps at same simulation time happen in “ $\delta$ -time” (VHDL jargon)
 
# Semantic gap

- ▶ Designers use HDLs and verify via simulation
  - ▶ event semantics
- ▶ Formal verifiers use logic and verify via proof
  - ▶ path semantics
- ▶ **Problem:** do path and simulation semantics agree?
- ▶ Would like:  
**paths = sequences of quiescent simulation states**


 
# Sequential threads: alternative simulation semantics




- ▶ Consider two Dtypes in series:

```
always @(posedge clk) l := in  
always @(posedge clk) out := l
```

- ▶ If `posedge clk`:
  - ▶ both threads become enabled
  - ▶ race condition
- ▶ Right thread executed first:
  - ▶ `out` gets previous value of `l`
  - ▶ then left thread executed
  - ▶ so `l` gets value input at `in`
- ▶ Left thread executed first:
  - ▶ `l` gets input value at `in`
  - ▶ then right thread executed
  - ▶ so `out` gets input value at `in`
 
## Sequential threads: aligning semantics



- ▶ If right thread executed first get formal model semantics  
 $R(in, l, out)(in', l', out') = (l' = in) \wedge (out' = l)$
- ▶ If left thread executed first get weird semantics  
 $R(in, l, out)(in', l', out') = (l' = in) \wedge (out' = in)$
- ▶ How to ensure formal model semantics?
- ▶ **Method 1:** use non-blocking assignments:  


```
always @(posedge clk) l <= in;  
always @(posedge clk) out <= l;
```

  - ▶ non-blocking assignments (<=) in Verilog
  - ▶ RHS of all non-blocking assignments first computed
  - ▶ assignments done at end of simulation cycle
- ▶ **Method 2:** make simulation cycle VHDL-like
 
# Verilog versus VHDL simulation cycles


- ▶ Verilog-like simulation cycle:

*Execute  
until  
quiescent  
then  
advance  
simulation  
time*




- ▶ VHDL-like simulation cycle:

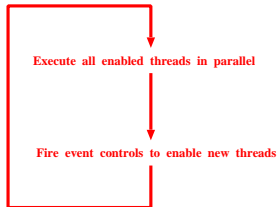*Execute  
until  
quiescent  
then  
advance  
simulation  
time*



# VHDL event semantics

 

- ▶ Recall HDL:

```
always @(posedge clk) l := in  
always @(posedge clk) out := l
```

- ▶ If *posedge clk*:

- ▶ both threads become enabled

- ▶ VHDL semantics:


- ▶ both threads executed in parallel
- ▶ *out* gets previous value of *l*
- ▶ in parallel *l* gets value input at *in*

- ▶ Now no race


- ▶ Event semantics matches path semantics


 
## Another example: combinational + sequential



 - ▶ Exercise: Do VHDL and Verilog event semantics agree?
- ▶ Ignoring race if input does change at clock edge
  - ▶ in real world might get meta-stability problems
  - ▶ also in previous example
  - ▶ need analogue simulation (e.g. using SPICE)



# Summary of dynamic versus static semantics

- ▶ Simulation (event) semantics different from path semantics
- ▶ No standard event semantics (Verilog versus VHDL)
- ▶ Verilog: need non-blocking assignments
- ▶ VHDL semantics closer path semantics
- ▶ Simulation runs generate finite sequences
  - ▶ better fit with LTL than CTL