

Digital Electronics (Part 2)



UNIVERSITY OF
CAMBRIDGE

Computer Laboratory

Part Ia, Part II (General) and Diploma in Computer Science

Copyright © Simon Moore, University of Cambridge, Computer Laboratory, 2003

Contents

Lecture notes:

- 9 LSI components and memories
- 10 Programmable logic devices
- 11 Asynchronous state machines

Datasheets:

- HCMOS family characteristics
- 74HC193 (counter)
- HT6166-70 (SRAM)
- GAL16V8 (PAL)

Lecture 9 — LSI components and memories

Contents:

- 74HC series chips
- SRAM
- address, data and control signals
- tristate



Example: 74HC193 counter chip

- referring to 74HC193 datasheet, note:
 - ◆ general description
 - ◆ pin out & pin definitions
 - ◆ function table
 - ◆ timing information
 - ◆ parallel load function




HCMOS family characteristics

- referring to HCMOS family datasheet pages 2 & 4:
 - ◆ power supply tolerances
 - ◆ valid input/output voltages and noise margins



Noise Margins

 


Memories

- store data in a volatile way (e.g. SRAM) or non volatile (e.g. FLASH, EEPROM, ROM)
- signals:
 - ◆ address bus — n bits which specify which location in memory is being referred to
 - ◆ data bus — m bits of bidirectional tristate bus transmitting data to be read/written
 - ◆ \overline{WE} — not write enable — determines whether data is to be read (1) or written (0)
 - ◆ \overline{OE} — not output enable — determines if data is to be output (0) or not (1)
 - ◆ \overline{CS} — not chip select — determines if the chip is to be activated (0) or not (1).



Tristate drivers

 

- when OE (output enable) is low the output is tristate



Datasheet: HT6116 SRAM

- referring to the HT6116 datasheet:
 - ◆ address and data buses
 - ◆ control signals
 - ◆ timing



Supervision Work

- design a 3-of-8 address decoder (i.e. 3 bits of address which decode to 8 word lines)
- design the state machine for workshop 4



Lecture 10 – Programmable Logic Devices

Contents:

- ROMs
- PALs
- FPGAs




ROMs – Overview

- ROM = Read Only Memory
- implements a table lookup where an *address* specifies a row in the table which holds the *data*
- for n bits of address we need 2^n rows in our table
- the n bits of address are decoded to 2^n *word lines*
- for m bit wide data the, size of a ROM = $O(m \times 2^n)$




ROMs – array structure

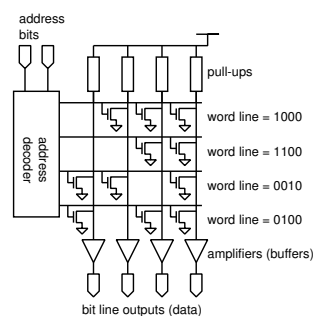

Notes:
2 address bits
4 data bits
so $2^2 \times 4 = 16$ bits



PALs – basic structure

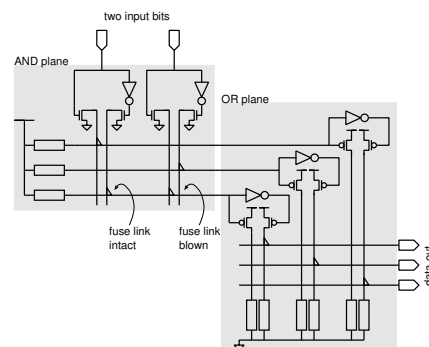

PALs – notes on datasheet

- page 1 shows the top level functionality and chip pin layout
- page 3 describes the Output Logic Macrocell which can emulate a wide range of old PAL devices
- page 4 shows the fixed OR plane, with or without DFF
- page 5 shows the extensive AND array structure which means that the fixed OR structure does not limit functionality
- pages 6–9 describe other modes (removed from handout)
- pages 11–13 contain the timing information (removed from handout)



PALs vs ROMs

- scaling issues:
 - ◆ ROM size is proportional to $O(2^{\text{address-bits}})$
 - ◆ PALs size is proportional to the number of terms that can be defined



FPGAs

- FPGA = Field Programmable Gate Array
- contains a sea of programmable wiring and function units controlled by memory bits which hold the program
- function units are typically 4 input, 1 output lookup tables with an optional DFF on the output
- more in Structured Hardware Design and ECAD



Supervision Work

- design determine the PAL equations for the state machines in workshops 2 & 3



Lecture 11 — Asynchronous Logic

Contents:

- asynchronous FIFO buffer design
- signal transition graphs
- C-elements




Synchronous vs asynchronous circuits

- Synchronous (clocked) circuits
 - ◆ discrete time provided by the clock
 - ◆ state is usually held in clocked flip-flops
 - ◆ typically no loops in combinational logic (no feedback)
 - ◆ easy to design in the small but can be problematic in the large
- Asynchronous circuits
 - ◆ continuous time
 - ◆ state is held in none clocked flip-flops
 - ◆ state holding elements often formed from combinational logic with loops (logic with feedback)
 - ◆ complex to design in the small but composes simply in the large



Fairbanks Scale: timing assumptions

 


Data signalling

- communication often required between a producer and a consumer which may be run from the same clock but produce/consume data at different rates
- signalling required for flow control to avoid data loss
- *delay insensitive* signalling guarantees that the consumer has consumed data before the producer produces more data
 - ◆ i.e. the producer waits until it has been acknowledged by the consumer
 - ◆ useful for synchronous design
 - ◆ vital for asynchronous design since there is no other mechanism (e.g. a clock) to ensure data ordering



 Example problem: Synchronous FIFO

- FIFO (First In First Out) buffers are often used to provide decoupled communication
- assume we have the following basic one place buffer arrangement:




Sync. FIFO: Environment rules

- we will use 4-phase level signalling on the input:
 - ◆ if $A_{in}=0$ then at some point R_{in} may go high
 - ◆ when $R_{in}=1$ then we expect A_{in} to go high eventually
 - ◆ if $A_{in}=1$ then at some point R_{in} may go low
 - ◆ when $R_{in}=0$ then we expect A_{in} to go low eventually
- storage assumption: when $A_{in}=1$ we assume that the data has been latched
- similarly on the output side




Signal Transition Graph Snippets

 - STGs specify the signal ordering rather than particular states
- STG snippets can specify requirements



Sync. FIFO: State transition graph

 

- note that $A_{in}=R_{out}=f$ in this example



Sync. FIFO: State table

current state			next state
f	Rin	Aout	f'=Ain=Rout
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



Sync. FIFO: K-map for f

f'		Rin=1		Aout=1	
		0	1	0	1
f=1	0	0	1	0	0
	1	1	1	1	0

$$f' = \text{Rin} \cdot \overline{\text{Aout}} + f \cdot \text{Rin} + f \cdot \overline{\text{Rout}}$$


note:

- ♦ glitch free function of f' if just one input changes at a time
- ♦ the environment rules specify that just one input changes at a time
- ♦ so do we need a DFF between f' and f?




Sync to Async

 - the signal transition graph for our f asynchronous state machine is below
- this satisfies the STG snippets



Gate level implementation

 

Muller C-element

- the function f we've just created is actually a Muller C-element with one input inverted
- the C-element is a little known latch designed by Muller in the 1950s
- truth table:

inputs		output
a	b	c'
0	0	0
0	1	c
1	0	c
1	1	1




RS latch implementations

- we could have implemented f using an RS latch with the following input functions:
 $S = \text{Rin} \cdot \overline{\text{Aout}}$
 $R = \text{Rin} \cdot \text{Aout}$
- the S input function determines the input combinations in the on-set
- the R input function determines the input combinations in the off-set
- for a valid asynchronous state machine:
 - ♦ the input transitions must only respond when the state is appropriate
 - ♦ the on-set and off-set should be disjoint and be implemented with glitch free functions



Timing assumptions for async. FIFO

 - the data must arrive before the request
- delay-lines (e.g. chains of inverters) are typically added in the request (Rout to Rin)



Supervision Work

- if n asynchronous FIFO storage elements from this lecture were connected together, how many data items could we store?
- hard problem: how could we improve the FIFO storage?
- suggested exam. questions useful for a revision supervision:
 - 2001 Paper 2 Questions 2 and 3
 - 2001 Paper 10 Question 1 parts a to e
 - 2002 Paper 2 Question 2
 - 2002 Paper 10 Question 1
 - 2003 Paper 2 Questions 2 and 3
 - 2003 Paper 10 Question 1

