

# 2006 Paper 2 Question 1

## Digital Electronics

Four pairs of circuits (a0, a1), (b0, b1), (c0, c1) and (d0, d1) are presented below. What is the operation of each circuit and how does it compare with its pair?

[5 marks each]

