 


COMPUTER SCIENCE TRIPOS Part IA – 2012 – Paper 2

2 Digital Electronics (IJW)

- (a) With the aid of appropriate diagrams, show how the Source–Drain current that flows in a p-channel MOSFET is controlled by the applied Gate–Source voltage. [4 marks]
- (b) (i) Draw the circuit diagram of a NOT gate that comprises an n-channel MOSFET and a resistor  $R$ . [2 marks]
- (ii) For the NOT gate in (b)(i), plot the relationship between the input voltage,  $V_{in}$  and the output voltage,  $V_{out}$ . Assume that the power supply voltage  $V_{DD} = 12\text{ V}$ ,  $R = 1\text{ k}\Omega$ , and that the MOSFET has the characteristics given in the following figure. [4 marks]



- (c) For the NOT gate in (b), calculate the power dissipated by the entire gate and that by resistor  $R$  alone, when  $V_{in} = 12\text{ V}$ . [4 marks]
- (d) The stray capacitance present at the output of the NOT gate in (b) can be represented by a capacitor,  $C = 100\text{ nF}$  connected between the gate output and  $0\text{ V}$ . Also assume that the MOSFET has an ON resistance  $R_{on} = 100\ \Omega$ . The input signal,  $V_{in}$ , is a  $1\text{ kHz}$  square wave with minimum and maximum amplitudes of  $0\text{ V}$  and  $12\text{ V}$  respectively.
- (i) Sketch the output signal waveform,  $V_{out}$ , of the NOT gate being sure to include indicative rise and fall times and voltage levels. [4 marks]
- (ii) How could the rise-time of  $V_{out}$  be reduced and what would be the impact of your proposed solution on the power dissipation of the circuit?

[2 marks]