

COMPUTER SCIENCE TRIPOS Part IA – 2013 – Paper 2

2 Digital Electronics (IJW)

- (a) With the use of appropriate diagrams, briefly explain the operation of Moore and Mealy finite state machines, paying particular regard to their differences.

[6 marks]

- (b) A serial data line carries binary data to a system with input  $X$ . The system is required to detect a sequence 010 in the data and give an output  $Y = 1$  at the end of the sequence. Only non-overlapping sequences should be detected in the data. For example, the output  $Y$  should only be 1 for the 0 underlined in the input sequence ... 1010101 ... .

Draw the state diagram for the system and state the minimum number of D-type bistables that are required to implement this finite state machine.

[6 marks]

- (c) A finite state machine (FSM) has the following sequence of states at the outputs of its D-type state registers,  $Q_A$ ,  $Q_B$  and  $Q_C$  :

$Q_A$	$Q_B$	$Q_C$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
0	0	0
$\vdots$	$\vdots$	$\vdots$

if the state registers are initialised to state 000, or

$Q_A$	$Q_B$	$Q_C$
1	1	1
1	1	0
1	0	1
1	1	1
$\vdots$	$\vdots$	$\vdots$

if the state registers are initialised to state 111.

Determine the next state combinational logic required to implement this FSM.

[8 marks]