

1998 Paper 7 Question 1

VLSI

Give the circuit for a CMOS inverter. [4 marks]

Give layouts for CMOS inverters of the following types:

- (a) basic design using one layer of metal
- (b) basic design using two layers of metal
- (c) an advanced design for driving large loads

[4 marks each]

What is the purpose of a buffer chain when distributing the clock? [4 marks]