

# Design of the Raspberry Spy NFC amplifier circuit

Alex Lee

August 31, 2012

## Summary

This Document details the calculations necessary to design the Near-Field radio receiver on the Raspberry Spy Robot PCB, in order that the operating frequency can be adjusted.

## 1 License



This work is licensed under a Creative Commons Attribution-ShareAlike 3.0 Unported License.

## Contents

<b>1 License</b>	<b>1</b>
<b>2 Introduction</b>	<b>2</b>
<b>3 Input Decoupling</b>	<b>2</b>
<b>4 Input Amplification</b>	<b>3</b>
4.1 Mid-band Gain . . . . .	3
4.2 Choice of Op-Amp . . . . .	3
4.3 High frequency cutoff . . . . .	4
<b>5 High Pass Filter</b>	<b>4</b>
<b>6 Rectifier</b>	<b>4</b>
<b>7 Envelope Detector</b>	<b>6</b>
<b>8 Envelope Amplifier</b>	<b>7</b>
<b>9 Potential Divider</b>	<b>7</b>
<b>10 <math>C_{12}</math></b>	<b>7</b>
<b>11 Coil and range</b>	<b>7</b>

## 2 Introduction

The Near Field Amplifier circuit was designed to be as easy to understand as possible, and its operation can be broken down into a series of stages. The overall circuit is shown in Figure 9 in the Appendix.

## 3 Input Decoupling

The input signal from the coil is roughly sinusoidal and oscillates about 0V. In order to amplify this directly, we would need to power the Op-Amp with both positive and negative supply voltages which are inconvenient to produce. It is much easier to power the Op-Amp between +5V and 0V and shift the input signal such that it is never negative. This is achieved by the circuit in Figure 1

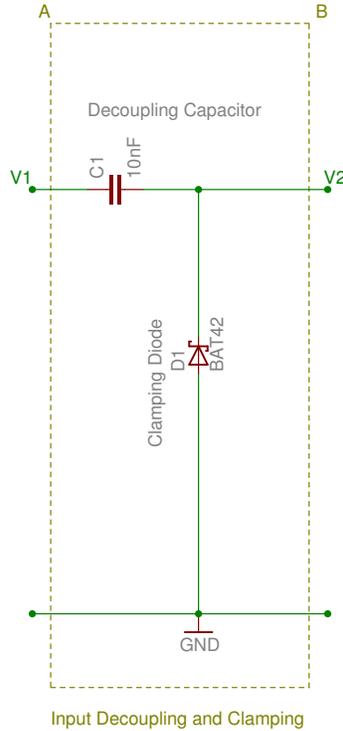


Figure 1: Input Decoupling and Clamping Stage

Assuming an input  $V_1$  varying between  $\pm v$  :

- The decoupling capacitor  $C_1$  blocks any DC component (impedance  $\frac{1}{j\omega C} \rightarrow \infty$  as  $\omega \rightarrow 0$ )
- When  $V_1$  is negative ( $V_1 = -v$ ), the diode  $D_1$  holds  $V_2$  at 0 V by conducting from GND. The current from GND charges  $C_1$  to  $V_{C_1} = -v$ .
- When  $V_1 = +v$ , diode  $D_1$  does not conduct. Assuming the current drawn from the output terminals is small enough compared to the period of oscillation,  $C_1$  will not discharge significantly and  $V_2 = V_1 - V_{C_1} = 2v$  while  $V_1$  is high.

## 4 Input Amplification

The next step is to amplify the input signal with the circuit in Figure 2

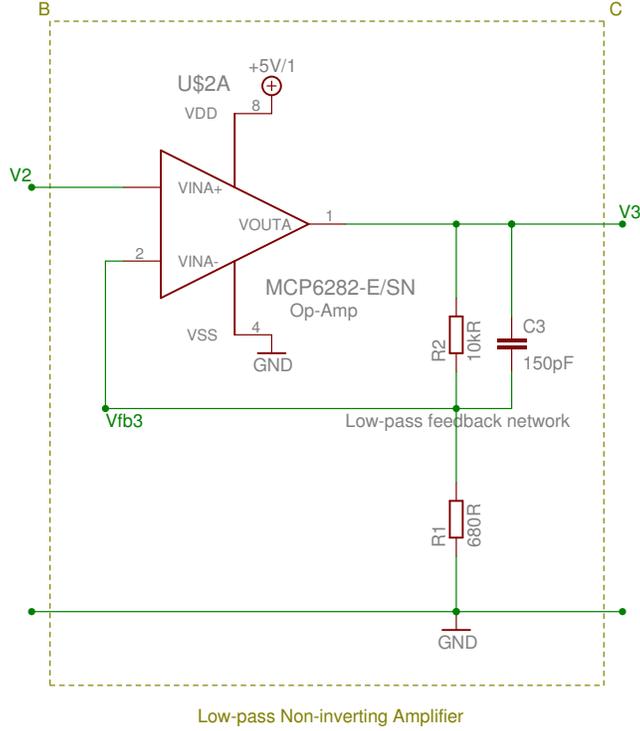


Figure 2: Input Amplifier

### 4.1 Mid-band Gain

At Mid-band (i.e the frequency we are interested in),  $C_6$  behaves as an open circuit and may be neglected.

$$\begin{aligned} \text{For an ideal Op-Amp: } V_{fb3} &= V_2 \\ V_{fb3} &= \frac{V_3 R_1}{R_2 + R_1} \\ \text{so Gain } G &= \frac{V_3}{V_2} = 1 + \frac{R_2}{R_1} \end{aligned}$$

Tests show that the voltage input from the coil is around 300 mV so to get output up to the 5V rail we need a gain of around 15. Therefore choose  $R_2 = 10\text{k}\Omega$ ,  $R_1 = 680\Omega$ .

### 4.2 Choice of Op-Amp

To achieve a gain of 15 at 64 kHz with the output varying between 0 V and +5 V the minimum properties in Table 1 are required. Rail-to-rail operation is also desirable given the low voltage supply. The MCP628x series fits this specification.

Property	Minimum Value
Gain-Bandwidth Product (also known as Unity gain bandwidth)	1 MHz
Slew rate	2 V/ $\mu$ s

Table 1: Op Amp Properties

### 4.3 High frequency cutoff

The capacitor  $C_3$  acts to bypass  $R_2$  at high frequencies and thus reduce the high frequency gain to unity. The impedance of  $R_2//C_3$  is

$$Z_{fb3} = \frac{R_2}{1 + j\omega R_2 C_3}$$

It is approximately true ( $G \approx \frac{Z_{fb3}}{R_1}$ ) that for the gain to be reduced by 3 dB from its mid-band value (half-power), the magnitude of the denominator must be equal to  $\sqrt{2}$ , thus

$$\omega_{-3dB} R_2 C_3 = 1$$

Choosing the cutoff frequency  $f_{-3dB} = 84\text{kHz}$  we find

$$C_3 = \frac{1}{2\pi f_{-3dB} R_2} = 190\text{pF} \approx 150\text{pF}$$

## 5 High Pass Filter

The signal has now been amplified and low-pass filtered but there may still remain low frequency interference. This is removed in stage CD (Figure 3).

The effective resistance  $R_{eff}$  is taken as being equal to  $R_3$  on the grounds that  $D_9$  has negligible effect on positive signals (see Figure 9). The output voltage  $V_4$  of this stage is thus given by the potential divider equation:

$$V_4 = V_3 \frac{R_{effective}}{R_{eff} + \frac{1}{j\omega C_2}} = V_3 \frac{1}{1 + \frac{1}{j\omega R_{eff} C_2}}$$

So for a lower -3dB frequency  $f_{-3dB} = 44\text{kHz}$ :

$$2\pi f_{-3dB} C_2 R_{eff} = 1$$

$$\text{so } C_2 = \frac{1}{2\pi f_{-3dB} R_{eff}} \approx 3.3\text{nF}$$

N.B. this needs to be recalculated if  $R_8$  is altered.

## 6 Rectifier

Circuit DE in Figure 4 is used to re-clip the output of the amplifier to have a minimum value of 0 V (the output otherwise does not quite reach the 0 V rail due to imperfect clamping on the input).  $D_3$  in combination with  $C_2$  performs the clamping. The rectifier diode  $D_9$  may not seem necessary at first but it prevents current from flowing backwards into the amplifier feedback network when the envelope detector circuit is holding  $V_5$  greater than  $V_4$ .

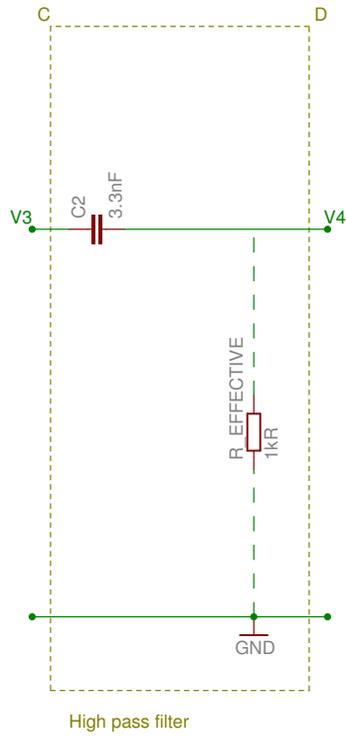


Figure 3: High Pass Filter

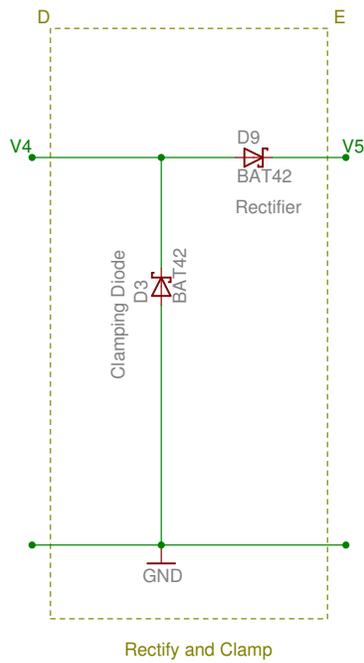


Figure 4: Rectifier and Clamping

## 7 Envelope Detector

The envelope detector EF shown in Figure 5 relies on the transient behaviour of a parallel RC circuit rather than the steady-state frequency response used in the filters.

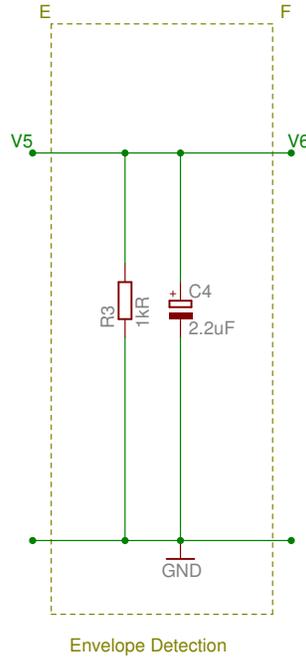


Figure 5: Envelope Detector

When the amplifier output at  $V_4$  is high (+5 V), the capacitor  $C_4$  will charge up almost instantaneously. When  $V_4$  is low, diode  $D_9$  prevents the flow of current back into the amplifier so  $C_4$  must discharge through the parallel resistor  $R_3$ .

We must choose the time constant  $RC$  such that the carrier wave ripple is smoothed out but the envelope is still sufficiently sharp to detect the rising edge reliably. The circuit was designed for a 64 kHz carrier wave and a modulating signal of the order of 10 Hz (to allow for imprecise timing when bit-banging the GPIO pins from python).

Thus we need:

$$\begin{aligned} \tau_{carrier} &<< RC < \tau_{envelope} \\ \text{or } \frac{1}{64 \times 10^3} &<< RC < \frac{1}{10} \end{aligned} \quad (1)$$

For minimum ripple,  $RC \approx 0.002$  s was chosen (only just over one order of magnitude smaller than  $\tau_{envelope}$ ). The maximum sustained output current of the MCP628x range of Op-Amps is 30 mA so  $R_3$  must be greater than  $\approx 180 \Omega$ . To fit both criteria we choose  $R_3 = 1 \text{ k}\Omega$  and  $C_4 = 2.2 \mu\text{F}$

The speed of transmission can be increased by around an order of magnitude by reducing  $C_4$  to 22 nF and  $C_{12}$  to 2.2 nF ( see Section 10 ). This increases the ripple on the output slightly but the main limiting factor is the speed of the receiving python code on the Raspberry

Pi. Re-writing the code in C may allow higher transmission speeds but the inherent timing inaccuracies in non-real-time Linux make this more difficult than on a micro-controller.

## 8 Envelope Amplifier

The envelope detector increases significant attenuation so the output must be amplified again with the non-inverting amplifier stage FG in Figure 6.

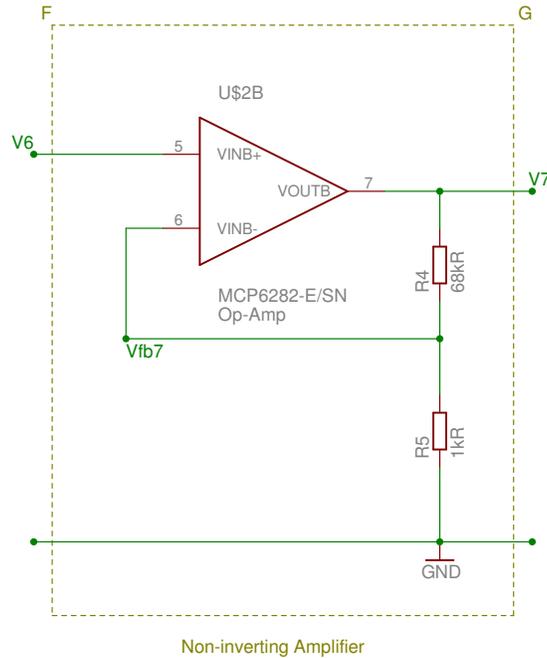


Figure 6: Envelope Amplifier

Resistors  $R_4 = 68 \text{ k}\Omega$  and  $R_5 = 1 \text{ k}\Omega$  are selected to give a gain of 70, ensuring the output clips to the +5 V rail. Almost any Op-Amp capable of running from a +5 V/0 V supply would be suitable here as the frequency of the signal to be amplified is so low. However the spare pins on the MCP6282 are used for convenience.

## 9 Potential Divider

The GPIO pins of the Raspberry Pi are not 5 V tolerant so the potential divider GH in Figure 7 is used to reduce the "high" voltage from 5 V to 3.3 V.

## 10 $C_{12}$

$C_{12}$  was added to remove noise spikes when the circuit was built on solderless breadboard. It may not be necessary at all on the PCB.

## 11 Coil and range

Experiments show that a 60-70mm diameter coil of around 30 turns of 0.2mm enamelled wire works well (the coil may be circular or square as in Figure 8 ).

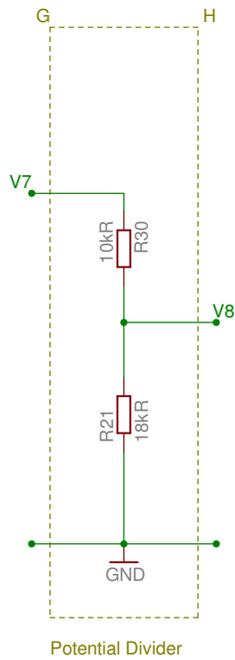


Figure 7: Potential Divider

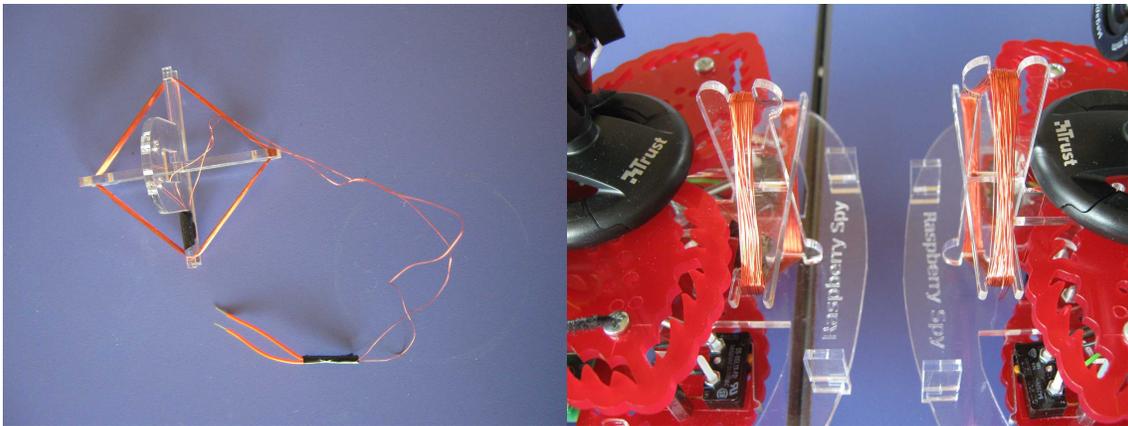


Figure 8: Example of Coil and mounting

The maximum distance between coils is around 70mm and a minimum distance is also sometimes observed.

## A Circuit Diagrams

Figure 9 shows the whole schematic for the near-field receiver.

Figure 11 shows the prototype circuit on solderless breadboard using two MCP6283 single Op-Amp 8-pin DIPs.

Figure 10 shows the receiver circuit on the PCB (top half of picture) using a single dual Op-Amp MCP6282 SOIC package. The second (lower) chip is used as a buffer in the transmitter. In future board versions an MCP6284 quad Op-Amp could be used to reduce the part count.

# RECEIVER

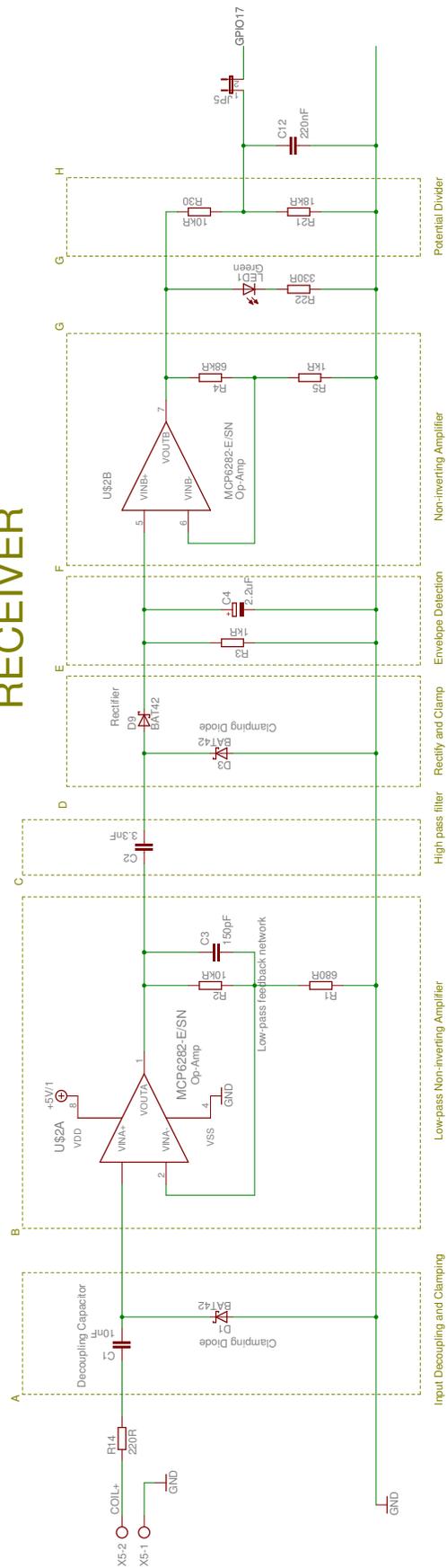


Figure 9: Whole Receiver Circuit

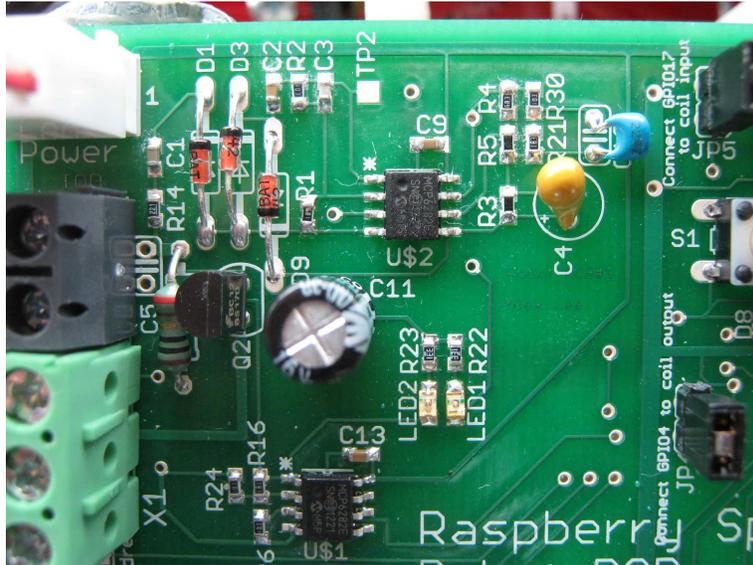


Figure 10: Receiving and Transmitting Circuits on PCB

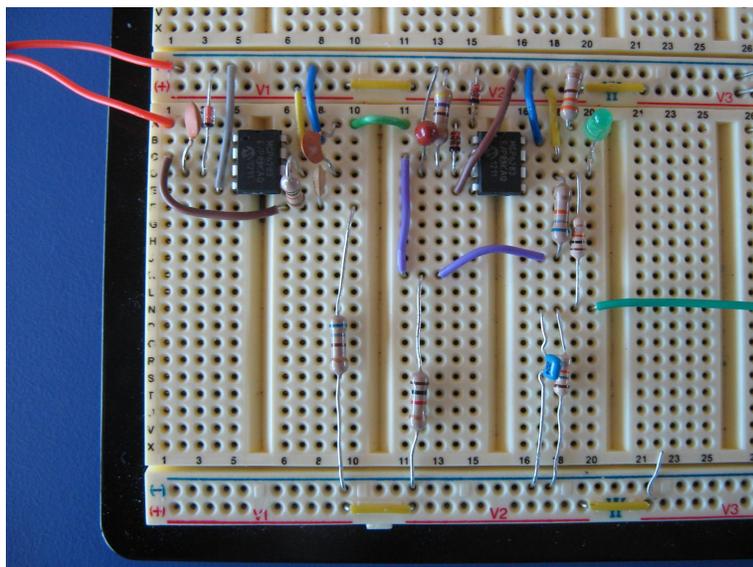


Figure 11: Receiving Circuit on Solderless Breadboard