
System On Chip Design And Modelling

CST Part II, 12 lectures

Lent Term 2009

Dr. David Greaves

`David.Greaves@cl.cam.ac.uk`

Reading material


- These slides plus the ADDITIONAL MATERIAL
- * OSCI. *SystemC tutorials and whitepapers*. Download from OSCI www.systemc.org and examples from course web site.
- *Transaction-Level Modeling with SystemC: TLM Concepts and Applications for Embedded Systems*. Frank Ghenassia. Springer (2006).
- *A Practical Introduction to PSL*. Cindy Eisner, Dana Fisman. Springer 2006. (Series on Integrated Circuits and Systems).

- *Creating Assertion-Based IP*. Harry D. Foster and Adam C. Krolnik. Springer (Series on Integrated Circuits and Systems).
- *System Design with SystemC* Springer. Grotket, Liao, Martin and Swan.
- *Modern VLSI Design (SoC Design)* W Wolf. Pearson Education.
- The Web: <http://www.flylogic.com/>
<http://www.systemc.org/> <http://www.spiritconsortium.org/>
<http://www.design-reuse.com/articles/>
http://www.esperan.com/tutorial/psl_simple.html

Course Pre-requisites

- Computer Design (Ib)
 - Some Assembler (e.g. MIPS/ARM/ARC/x86)
 - Verilog ECAD & Architecture
 - Preferably C/C++
 - Operating Systems & Computer Architecture

Increasing abstraction

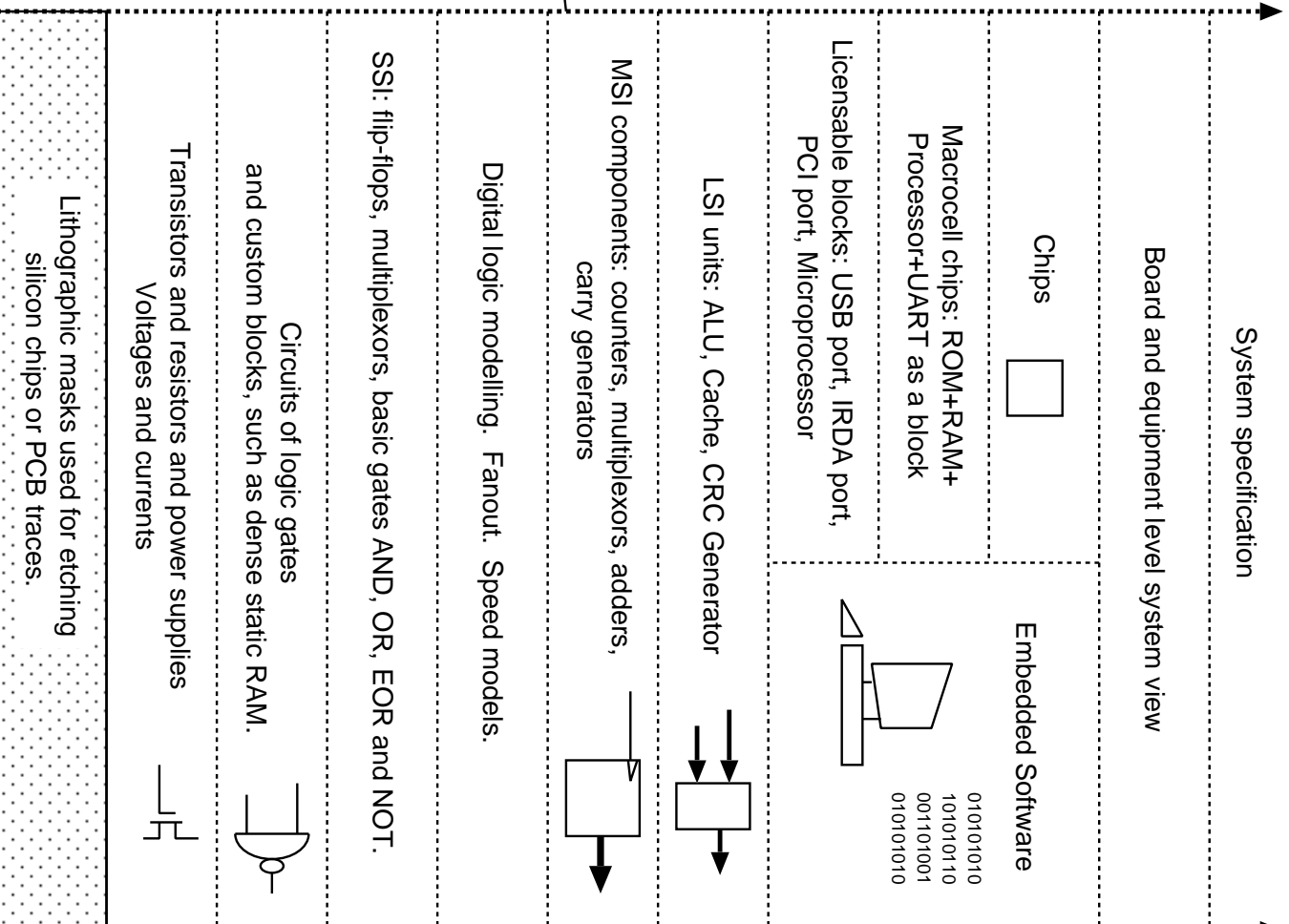

Program files for field programmable hardware devices.

Software for embedded processor

L1: Verilog RTL Design: Simulation and Synthesis.


Topic: L1 Basic RTL to logic gates: styles, simulation and synthesis.

- LG1.1 - Basic RTL
- LG1.2 - Structural, Combinational, Behavioural
- LG1.3 - RTL abstract syntax
- LG1.4 - Compute/Commit Cycle
- LG1.5 - Event Driven Simulation Kernel
- LG1.6 - RTL internal forms
- LG1.7 - Basic Synthesis Algorithm
- LG1.8 - Adder Synthesis
- LG1.9 - RAM Memories
- LG1.10 - Structural Hazards
- LG1.11 - Retiming
- LG1.12 - RTL Compared with Software
- LG1.13 - Long Multiplication

LG1.1 - Basic RTL 1/3, Structural

Level 1/3: Structural Verilog : Structural, Heirarchic, Netlist
 
```
BEGIN subcircuit(clk, rst, q2);  
  INPUT clk, rst;  
  OUTPUT q2;  
  Ff1   : DFFR(clk, rst, a, q1, qb1);  
  Ff2   : DFFR(clk, rst, q1, q2, qb2);  
  Ff3   : DFFR(clk, rst, q2, q3, qb3);  
  Nor   : NOR2(a, q2, q3);  
END subcircuit;
```



Just a netlist.

No registers are transferred by assignment!

LG1.1c - RTL Flattening

Heirarchic Netlist

```

module MOD1(b, a);
  input a; output b;
  wire c;
  INV inv1(c, a);
  MODX modx1(b, c);
endmodule

module MOD2(q, s, r);
  input r, s; output q;
  wire c;
  INV inv2(c, s);
  MODY mody1(q, c, r);
endmodule

module MODTOP(r, aa, bb);
  output rr;
  input aa, bb;

  wire l, m;

  MOD1 m(l, aa);
  MOD1 n(m, bb);
  MOD2 o(rr, l, m);
endmodule

```

Equivalent Flattened Netlist


```

module MODTOP (rr, aa, bb);
  input aa, bb; output rr;
  wire l, m;
  wire m_c, n_c, o_c;

  INV m_inv1(m_c, aa);
  INV n_inv1(n_c, bb);
  INV o_inv2(o_c, l);
  MODX m_modx1(m_c, l);
  MODX n_modx1(n_c, m);
  MODY o_mody1(rr, o_c, m);
endmodule


```

For many designs the flattened netlist is often bigger than the hierarchic netlist owing to multiple instances of the same component. Here it was smaller.

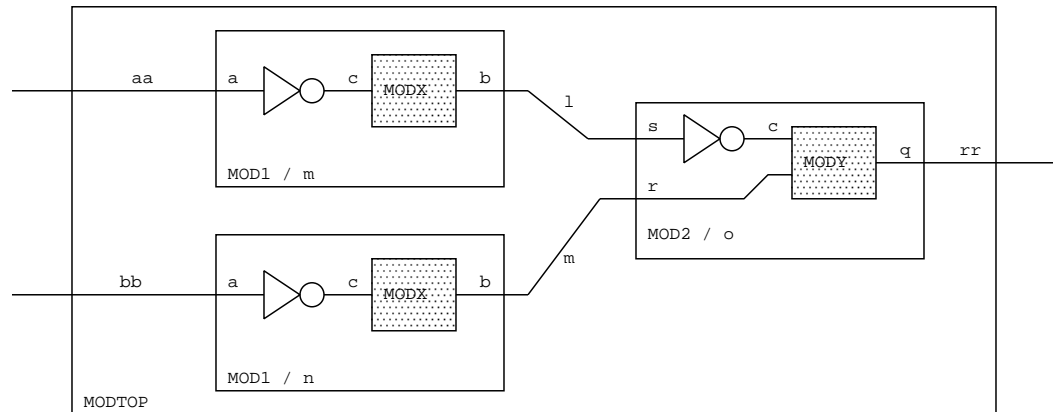


LG1.1c - Elementary Constructs

Nand Gate

 


```
assign y = ~(a & b);
```

2 input Mux

 

```
if (cond) y = e1;
else y = e0;
y = (cond) ? e1 : e0;
```


D-type FF

 

"On the positive edge of the clock the value on the d input is copied to the q output"

```
always @(posedge clk) q <= d;
```

Accumulator

 


```
reg [15..0] qp;
input [15..0] data;
always @(posedge clk) qp <= qp+data;
```

Little Circuit (pulse generator).

```
module CCT(d, clk, op);
input d, clk;
output op;
reg op;
reg v1, v2;

always @(posedge clk)
begin
v1 <= d;
v2 <= v1;
op <= v1 & ~v2;
end
endmodule
```

 

LG1.1c Basic RTL 2/3, RTL with register transfers!

```
module CTR16(ck, din, o);

    input ck, din;
    output o;

    reg [3:0] count, oldcount;

    // Add a four bit decimal value of one to count
    always @(posedge ck) begin
        count <= count + 1;
        if (din) oldcount <= count;
    end

    // Note ^ is exclusive or operator
    assign o = count[3] ^ count[1];

endmodule
```

Registers are assigned in clock domains.

Combinational logic (continuous assign) has no explicit clock domain.

If we do not assign a register, it retains its old value:

```
oldcount <= (din) ? count : oldcount;
```

L1.1c - Basic RTL 3/3, Behavioural

Behavioural RTL resembles software.

A behavioural thread references variables already updated.

The order of the statements has an effect!

The following behavioural code

```
if (k) x = y;  
z = !x;
```

can be compiled down to the following unordered RTL

```
x <= (k) ? y: x;  
z <= !((k) ? y: x);
```

Not all RTL is classed as '*synthesisable*'.

L1.1c - Behavioural - 'Non-Synthesisable' RTL

RTL with event control in the body of a thread defines a statemachine.

The statemachine requires a PC register at runtime (implied).

```
input clk, din;
output req [3:0] q;

always begin
    q <= 1;
    @(posedge clk) q <= 2;
    if (din) @(posedge clk) q <= 3;
    q <= 4;
end
```


How many bits of PC are needed ?

Is conditional event control synthesisable ?

Does the output q ever take on the value 4 ?

L1.1c - Behavioural - 'Non-Synthesisable' RTL continued

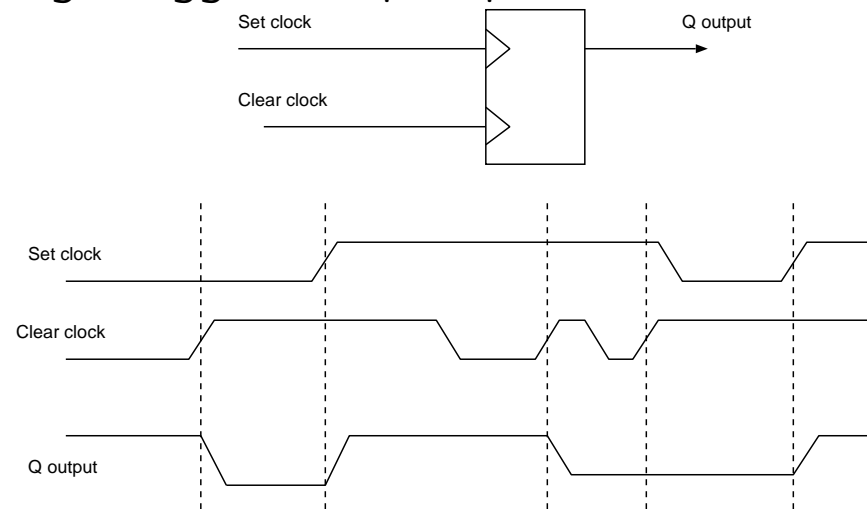Consider the dual-edge-triggered flip-flop.



```
reg q;  
input set, clear;  
  
always @(posedge set) q = 1;  
always @(posedge clear) q = 0;
```

Here a variable is updated by more than one thread.

This component is commonly used in phase-locked loops.

Can be modelled in Verilog, but not part of Verilog synthesis.

LG1.1c - Non-synth continued.

Test bench commonly uses delays:

```
reg clk, reset;
```

```
initial begin clk=0; forever #50 clk = !clk; end
```

```
initial begin reset = 1; # 1025 reset = 0; end
```

Other non-synthesisable constructs:

- fork/join
- Variable update by more than one thread

Finite state is all that should matter!

LG1.2 - RTL Forms, Summary.

Summary:

Verilog RTL allows these levels to be mixed within one module.

1. Structural - a hierarchial net list form
2. Un-ordered RTL - complex RHS expressions.
3. Behavioural - follows flow of program counter.

Simulation uses a top-level test bench module with no inputs.

Synthesis starts from a root lower in the hierarchy.

Synthesisable code uses synthesisable subset!

Later topics: SystemC, Bluespec and C-to-RTL flows.

LG1.3 - SRTL abstract syntax

Synthesisable RTL - Zero Delay.

Expressions

```
datatype ex_t =  
  Num of int  
  | Net of string  
  | Inv of ex_t  
  | Query of ex_t * ex_t * ex_t  
  | Diadic of diop_t * ex_t * ex_t  
  | Subscript of ex_t * ex_t
```

Imperative commands (might also include a case statement) but no loops.

```
datatype cmd_t =  
  Assign of ex_t * ex_t  
  | If1 of ex_t * cmd_t  
  | If2 of ex_t * cmd_t * cmd_t  
  | Block of cmd_t list
```

Our top level will be an unordered list of the following sentences:

```
datatype s_t =  
  Sequential of edge_t * ex_t * cmd_t  
  | Combinational of ex_t * ex_t
```


LG1.5 - Event Driven Simulation Kernel

Datastructure for the model and netlist.

```
(* A net has a string name and a width.
 * A net may be high z, dont know or contain an integer from 0 up to 2**width - 1.
 * A net has a list of driving and reading models.
 * A model has a unique instance name, a delay, a form and a list of nets it contacts.
 * It also may have some internal state, held in the last field.
*)
datatype value_t = V_n of int | V_z | V_x;


datatype m_t = M_AND | M_OR | M_INV | M_XOR | M_DFF | M_BUFIF | M_TLATCH | M_CLOCK;

datatype internal_state_t =
  IS_NONE
| IS_DFF of value_t ref
| IS_CLOCK of int ref
;

datatype
  net_t = NET of value_t ref * string * int * model_t list ref * model_t list ref

and
  model_t = MODEL of string * int * m_t * net_t list * internal_state_t
;
```

LG1.5c - Event Driven Simulation Kernel

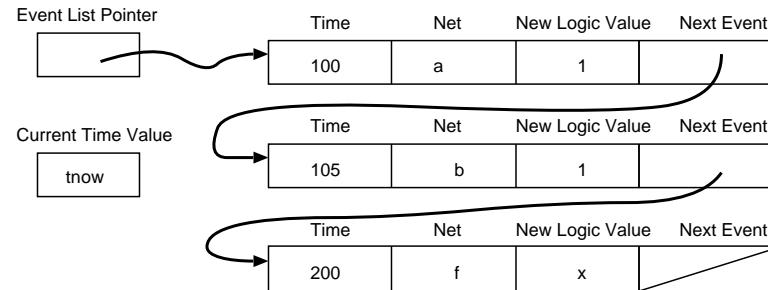

Constructor for a new event: insert at correct point in the sorted event list:

```

fun event(time, net, value) =
  let fun a e = case !e of
        (A as EMPTY) => e := EVENT(time, net, value, ref A)
      | (A as EVENT(t, n, v, e')) => if (t > time)
        then e := EVENT(time, net, value, ref A)
        else a e'
    in a eventlist
  end
  
```

Main simulation: keep dispatching until event list empty:


```

fun dispatch_one_event() =
  if (!eventlist = EMPTY) then print("simulation finished - no more events\n")
  else let val EVENT(time, net, value, e') = !eventlist in
    ( eventlist := !e';
      tnow := time;
      app example_models (net_setvalue(net, value))
    ) end
  
```

LG1.4 - Compute/Commit Cycle

Hardware simulators support compute/commit signal paradigm.
 
```
reg A, B;  
always @(posedge ck) begin  
    A <= B;  
    B <= A;  
end
```



```
reg zz;  
reg [2:0] q;  
always @(posedge ck) begin  
    zz <= ~zz;  
    if (zz) q <= q + 3'd1;  
    // Prev line sees old zz  
end
```

- All of the right-hand side expressions are evaluated
- All the results are stored into the left-hand sides.
- Repeat

Commit may create further events for current simulation time.

Delta cycle: a compute/commit cycle without advancing global time.

A VHDL 'signal' has a current and a next value. A SystemC 'sc_signal' likewise has a current and a next value. In Verilog, it's a matter of the assignment operator rather than the net declaration.

LG1.4c - Compute/Commit Cycle

Compute/commit extension: either we need

- a next value field in signal nets (arrays may have multiple), or
- a separate list of pending values to be committed.

Modified EDS kernel:

Repeat:

1. S = all events that have identical time taken from the event list head.
2. Dispatch all of S (this is the compute phase).
3. Commit pending values to current values.

When we repeat the above loop, if there are any zero-delay models, the value of t_{now} may not advance: hence a delta cycle.

LG1.6 - RTL Synthesis: Internal forms

Ignore all timing information (hash delays.)

For synthesis to gates, generate a list of assignments for each clock domain, that can be done in parallel.

A final list represents combinational logic, not associated with a clock domain.

Code generation phase: match operations needed against library of gates.

(Similar to a software compiler: match operations needed against instruction set.)

Need to keep additional information for asynchronous reset and presets.

Transparent latches also need additional handling.

```
module TLATCH(q, g, d);  
    input d, q;  
    output q;  
    assign q = (g) ? d: q;  
endmodule
```

LG1.7 - Basic Synthesis Algorithm

Input

```
module TC(clk, cen);
  input clk, cen;
  reg [1:0] count;
  always @(posedge clk) if (cen) count<=count+1;
endmodule// User=djg11
```

Output

```
module TC(clk, cen);
  wire u10022, u10021, u10020, u10019;
  wire [1:0] count;
  input cen;   input clk;
  CVINV  i10021(u10021, count[0]);
  CVMUX2 i10022(u10022, cen, u10021, count[0]);
  CVDFE  u10023(count[0], u10022, clk, 1'b1, 1'b0, 1'b0);
  CVXOR2 i10019(u10019, count[0], count[1]);
  CVMUX2 i10020(u10020, cen, u10019, count[1]);
  CVDFE  u10024(count[1], u10020, clk, 1'b1, 1'b0, 1'b0);
endmodule
```

Phase ONE - Generate guard/value lists for each lhs/clock domain.

Phase TWO - Convert to binary gate (bit lane) form with one expression for each bit lane.

LG1.7 Phase ONE - Generate guard/value lists for each clock domain.

Generate a list of variables assigned under the clock.

For each variable, collate the assignments into (guard, value) pairs.

For array assigns, we need a (guard, subscript, value) tuple for each update.

Generate an assignment for each variable where the rhs is a query tree from each list.

If blocking assigns are present, then an environment must be passed in for re-writing the rhs expressions as though the assigns had taken place.

Non-determinism arises if array subscripts cannot be compared at compile time (pointer alias problem).

A final list is needed for the unclocked, combinational logic.

LG1.7 Phase TWO - Convert to binary (bit lane) form

Sign extend an arg to width n:

```
fun sex n nil = if n<=0 then nil else raise "cannot do sex on an empty list"
| sex n [item] = if n<=1 then [item] else item :: sex (n-1) [item]
| sex n (h::t) = h :: (sex (n-1) t);
```

Example: integer constant:

```
| pandex w (Num n) = if n = 0 then [ xi_false ] else
  let fun k 0 = nil (* lsb first *)
      k n = (if (n mod 2)=1 then xi_true else xi_false) :: k (n div 2)
          fun q 0 = [xi_true] (* final negative sign bit *)
          q n = (if (n mod 2)=0 then xi_true else xi_false) :: q (n div 2)
  in if (n >= 0) then k n else sex w (q (0-1-n)) end
```

Example: -4 in a 6 bit field is 111100.

Example: conditional expression: a broadside multiplexor:

```
| pandex w (Query(g, t, f)) =
  let val t' = pandex w t
      val f' = pandex w f
  fun k([], []) = []
    k(a, nil) = k(a, [ false ])
    k(nil, b) = k([ false ], b)
    k(a::at, b::bt) = gen_mux2(g, a, b) :: k(at, bt)
  in k(t', f') end
```


LG1.7 Further Synthesis Issues

This basic algorithm does not consider any guiding metrics:

- Power consumption
- Area use
- Performance
- Testability

Gate libraries have high and low drive power forms of most gates.

Use Quine/McCluskey Espresso Algorithm for logic minimisation.

Can re-compute expressions locally.

Retiming for structural hazard and timing closure avoidance is now becoming more common (BlueSpec)

LG1.8 - Adder Build (Synthesis)

Adding a pair of bit lists, lsb first.



Ripple carry adder:

```
fun add c (nil, nil) = [c]
| add c (a::at, b::bt) =
  let val s = gen_xor(a, b)
      val c1 = gen_and(a, b)
      val c2 = gen_and(s, c)
  in (gen_xor(s, c))::(add (gen_or(c2, c1)) (at, bt))
  end
```

Faster adder: use wide gates: use functions like `gen_add1`

Carry argument is replaced with a list of generate and propagate pairs from the earlier stages.

LG1.8 continued - Kogge Stone adder

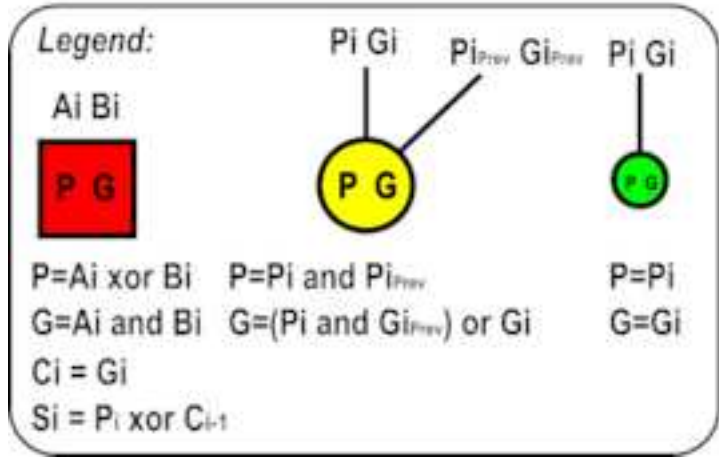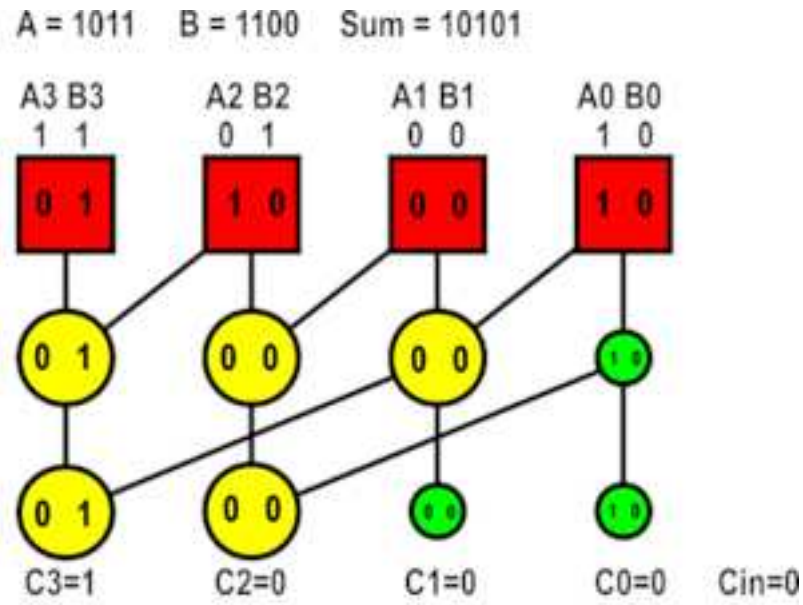

Kogge-Stone is very fast and the area is not too bad, but the wiring is not regular.

Synthesises well. Hard to understand!

For FPGA: Just use RTL '+' and FPGA tools instantiate special paths.

Ex (long): Write a Kogge-Stone generator.

LG1.8c continued - Subtractor, Equality, Inequality, Shifts

- < > ?= <= != == << >>

Subtractor: instead pass in a one as the leading borrow-bar and complement each bit from the second operand.

A subtractor will generate a borrow output. If $a < b$ then $a - b$ will need a borrow, hence the raw subtractor implements less-than.

Greater than or equal is just the complement of less than.

Other two inequalities: just swap the operands.

Equality test: check subtractor output is zero: requires an additional NOR gate.

Constant shifts: trivial in bit lane form.

Dynamic shifts: ML code to synthesise barrel shifter is easy.

LG1.9 - RAM Memories

RTL supports arrays: arrays can be synthesised to RAM memories or register files.

```
reg [31:0] myram [32767:0]; // 32K words of 32 bits each.  
// To execute the following in one clock cycle needs two RAM ports  
always @(posedge clk) myram[a] <= myram[b] + 2;
```

Today: RAM inference from array only done by FPGA tools and high-level synthesis tools. Everyone else defines busses and makes structural instances.

Example dual-ported (one read, one write), SRAM behavioural model:

```
module R1W1RAM(din, waddr, clk, wen, raddr, dout);  
    input clk, wen;  
    input [14:0] waddr, raddr;  
    input [31:0] din;  
    output [31:0] dout;  
  
    reg [31:0] myram [32767:0]; // 32K words of 32 bits each.  
    always @(posedge clk) begin  
        dout <= myram[raddr];  
        if (wen) myram[waddr] <= din;  
    end
```

The behavioural model will be replaced with a RAM macrocell for silicon implementation.

LG1.9c Memories continued

On-chip SRAM needs test mechanism:

- Can test with software running on embedded processor.
- Can have a special test mode, where address and data lines become directly controllable (JTAG or otherwise).
- Can use a built-in self test (BIST) wrapper that implements 0/F/5/A and walking ones typical tests.

Off-chip RAMS, such as DRAM and ZBT SRAM commonly used:

- Large area: would not be cost-effective on-chip.
- Specialised, proprietary or dense VLSI technology
- Non-volatile process (FLASH)
- Commodity part (DRAM, FLASH)

Again, these are instantiated by hand.

LG1.10 - Structural Hazards

Structural Hazard: an interruption to a computation or flow of data owing to a physical resource that has insufficient capacity.

Operations that could potentially be done in parallel have to be done serially.

Example: insufficient number ALUs.

Example: insufficient number of ports on a RAM/register file.

Holding registers typically needed.

Non-fully pipelined component: is unable to start a new operation on every clock cycle.

Start input and a busy/ready output.




Busy for a constant or variable number of cycles.

Example: fixed point multipliers and dividers.


Example: all floating point operators.

LG1.11 - Retiming & Recoding

Timing closure : Making the design meet its target clock rate.

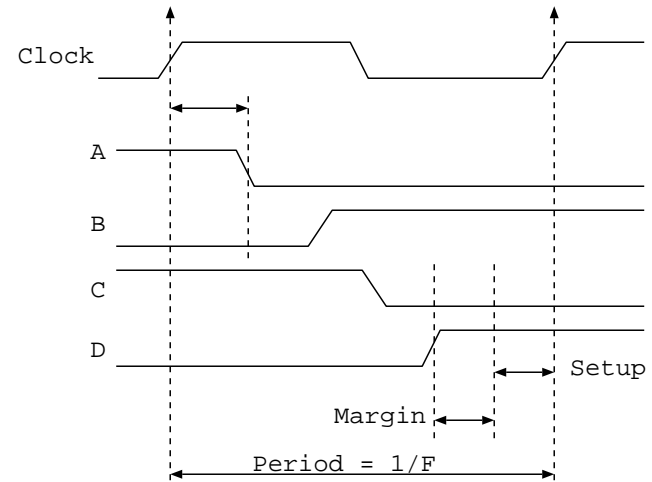 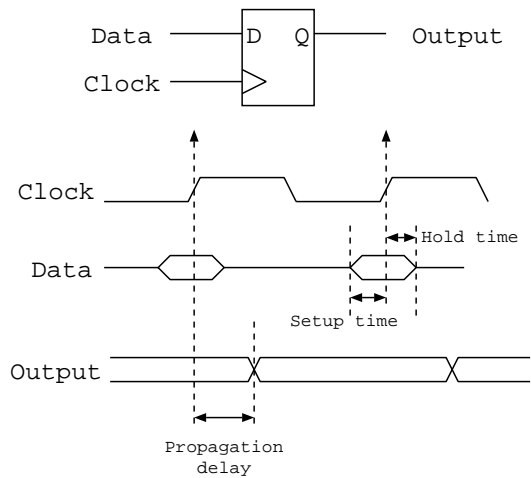

LG1.11 - Retiming continued

 

Flip-flop migration:

```
a <= b + c;          b1 <=c; c1 <= c;  
q <= (d) ? a:0;      q <= (d) ? b1+c1:0;
```

Alternatively, pushing the multiplexor back will require an earlier version of d which might not be available.

Problems with internal loops.

Problems with external handshakes that are non-transactional.

Retiming can overcome structural hazard (e.g. write back cycle in RISC pipeline).

Other rewrites: Automatically introduce one-hot and gray encoding, or invert for reset as preset.

LG1.12 - RTL Compared with Software

Synthesisable RTL (SRTL) looks a lot like software at first glance, but we soon see many differences.

SRTL is statically allocated and defines a finite-state machine.

Threads do not leave their starting context and all communication is through shared variables that denote wires.

There are no thread synchronisation primitives, except to wait on a clock edge.

Each variable must be updated by at most one thread.


Software on the other hand uses far fewer threads: just where needed. The threads may pass from one module to another and thread blocking is used for flow control of the data.

SRTL requires the programmer to think in a massively parallel way and leaves no freedom for the execution platform to reschedule the design.

In the future, we expect/hope to see more convergence between these styles: Retimed Parallel Expression or Parallelism Inference.

LG1.13 - Long Multiplication


 
Flash multiplier - combinatorial implementation (e.g. a Wallace Tree).



Sequential Long Multiplication

```
RA=A
RB=B
RC=0
while(RA>0)
{
    if odd(RA) RC=RC+RB;
    RA = RA >> 1;
    RB = RB << 1;
}
```

Micro-Architecture for a Long Multiplier

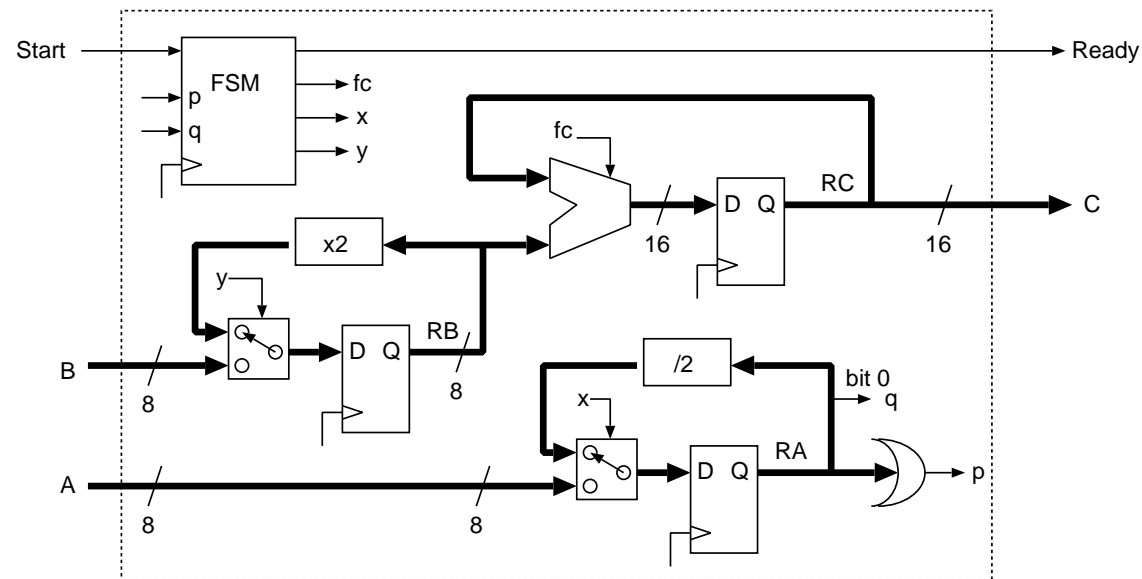 

Implements conventional long multiplication.

Certainly not fully-pipelined.

Exercise: Write out complete design, including sequencer in RTL or SystemC.

Booth's Multiplier

Booth does two bits per clock cycle:

(* Call this function with $c=0$ and $carry=0$ to multiply x by y . *)

```
fun booth(x, y, c, carry) =
  if(x=0 andalso carry=0) then c else
let val x' = x div 4
    val y' = y * 4
    val n = (x mod 4) + carry
    val (carry', c') = case (n) of
      (0) => (0, c)
    | (1) => (0, c+y)
    | (2) => (0, c+2*y)
    | (3) => (1, c-y)
    | (4) => (1, c)
    in booth(x', y', c', carry')
end
```

Exercise: Design a micro-architecture consisting of an ALU and register file to implement Booth. Design the sequencer too.