

# Digital Electronics

## Part II – Electronics, Devices and Circuits

Dr. I. J. Wassell

### Introduction


- In the coming lectures we will consider how logic gates can be built using electronic circuits
- First, basic concepts concerning electrical circuits and components will be introduced
- This will enable the analysis of linear circuits, i.e., one where superposition applies:
  - If an input  $x_1(t)$  gives an output  $y_1(t)$ , and input  $x_2(t)$  gives an output  $y_2(t)$ , then input  $[x_1(t)+x_2(t)]$  gives an output  $[y_1(t)+y_2(t)]$

## Introduction

- However, logic circuits are non-linear, consequently we will introduce a graphical technique for analysing such circuits
- Semiconductor materials, junction diodes and field effect transistors (FET) will be introduced
- The construction of an NMOS inverter from an n-channel (FET) will then be described
- Finally, CMOS logic built using FETs will then be presented
 
## Basic Electricity

- An electric current is produced when charged particles e.g., electrons in metals, move in a definite direction
- A battery acts as an 'electron pump' and forces the free electrons in the metal to drift through the metal wire in the direction from its -ve terminal toward its +ve terminal



## Basic Electricity

- Actually, before electrons were discovered it was imagined that the flow of current was due to positively charged particles flowing out of +ve toward -ve battery terminal
- Indeed, the positive direction of current flow is still defined in this way!
- The unit of charge is the *Coulomb (C)*. One Coulomb is equivalent to the charge carried by  $6.25 \cdot 10^{18}$  electrons (since one electron has a charge of  $1.6 \cdot 10^{-19}$  Coulombs).

## Basic Electricity


- Current is defined as the rate of flow of charge, i.e., a flow of 1 *Coulomb (C)* in 1 second is defined as 1 *Ampere (A)*.
- In the circuit shown in the earlier slide, it is the battery that supplies the electrical force and energy that drives the electrons round the circuit.
- In doing so, the electrons give up most of their energy as heat as the temperature of the metal wire rises.

## Basic Electricity

- It can be *imagined* that each Coulomb of charge that leaves the battery receives a fixed amount of electrical energy that depends upon the battery.
- So the electromotive force (emf)  $E$  of a battery is defined to be 1 *Volt* (V) if it gives 1 *Joule* (J) of electrical energy to each Coulomb passing through it.
 
## Basic Electricity

- A closely related concept is potential difference (pd). For example, the lamp in the following circuit changes most of the electrical energy carried by the electrons into heat and light.



- So the pd across a device, e.g., the lamp, in a circuit is 1V if it changes 1 J of electrical energy into other forms of energy when 1 C of charge passes through it.

## Basic Electricity


- Note that pd and emf are usually called *voltages* since both are measured in V.
- Electrical engineers have an alternative (but essentially equivalent) view concerning pd.
- That is, conductors, to a greater or lesser extent, oppose the flow of current. This 'opposition' is quantified in terms of *resistance* ( $R$ ). Thus the greater is the resistance, the larger is the potential difference measured across the conductor.

## Basic Electricity

- The *resistance* ( $R$ ) of a conductor is defined as  $R=V/I$ , where  $V$  is the pd across the conductor and  $I$  is the current through the conductor.
- This is known as *Ohms Law* and is usually expressed as  $V=IR$ , where resistance is defined to be in Ohms ( $\Omega$ ).
- So for an *ohmic* (i.e., linear) conductor, plotting  $I$  against  $V$  yields a straight line through the origin
 
## Basic Electricity


- Conductors made to have a specific value of resistance are known as *resistors*.
- They have the following symbol in an electrical circuit:



- Analogy:
  - The flow of electric charges can be compared with the flow of water in a pipe.
  - A pressure (voltage) difference is needed to make water (charges) flow in a pipe (conductor).
 
## Basic Circuits


- Kirchhoff's Current Law – The sum of currents entering a junction (or node) is zero, e.g.,



- That is, what goes into the junction is equal to what comes out of the junction – Think water pipe analogy again!
 
## Basic Circuits


- Kirchhoff's Voltage Law – In any closed loop of an electric circuit the sum of all the voltages in that loop is zero, e.g.,



- We will now analyse a simple 2 resistor circuit known as a *potential divider*
 
## Potential Divider

- What is the voltage at point  $x$  relative to the 0V point?



$$V = V_1 + V_2$$

$$V_1 = IR_1 \quad V_2 = IR_2$$

$$V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$I = \frac{V}{(R_1 + R_2)}$$

$$V_x = V_2 = \frac{V}{(R_1 + R_2)} R_2 = V \left( \frac{R_2}{R_1 + R_2} \right)$$


Note: circle represents an ideal voltage source, i.e., a perfect battery

## Solving Non-linear circuits

- As mentioned previously, not all electronic devices have linear I-V characteristics, importantly in our case this includes the FETs used to build logic circuits
- Consequently we cannot easily use the algebraic approach applied previously to the potential divider. Instead, we will use a graphical approach
- Firstly though, we will apply the graphical approach to the potential divider example


## Potential Divider

- How can we do this graphically?

 

So if  $V = 10V$ ,  $R_1 = 1\Omega$  and  $R_2 = 2\Omega$
 
$$V_x = V \left( \frac{R_2}{R_1 + R_2} \right) = 10 \left( \frac{2}{1 + 2} \right) = 6.7V$$






## Graphical Approach


- Clearly approach works for a linear circuit.
- How could we apply this if we have a non-linear device, e.g., a transistor in place of  $R_2$ ?
- What we do is substitute the  $V$ - $I$  characteristic of the non-linear device in place of the linear characteristic (a straight line due to Ohm's Law) used previously for  $R_2$

## Graphical Approach

 


So if  $V = 10V$  and  $R_1 = 1\Omega$

 The voltage at  $x$  is  $aV$  as shown in the graph


 
## Devices that store energy

- Some common circuit components store energy, e.g., capacitors and inductors.
- We will now consider capacitors in detail.
- The physical construction of a capacitor is effectively 2 conductors separated by a non-conductor (or dielectric as it is known).



Symbol of a Capacitor

Unit of capacitance: Farads (F)

- Electrical charge can be stored in such a device.

## Capacitors

- So, parallel conductors brought sufficiently close (but not touching) will form a capacitor
- Parallel conductors often occur on circuit boards (and on integrated circuits), thus creating unwanted (or parasitic) capacitors.
- We will see that parasitic capacitors can have a significant negative impact on the switching characteristics of digital logic circuits.


## Capacitors

- The relationship between the charge  $Q$  stored in a capacitor  $C$  and the voltage  $V$  across its terminals is  $Q = VC$ .
- As mentioned previously, current is the rate of flow of charge, i.e.,  $dQ/dt = I$ , or alternatively,  $Q = \int Idt$ .
- So we can write,


$$V = \frac{1}{C} \int Idt$$
 
## Capacitors

- We now wish to investigate what happens when sudden changes in configuration occur in a simple resistor-capacitor (RC) circuit.




## RC circuits

 

- Initially,  $C$  is discharged, i.e.,  $V_{out}=0$  and the switch moves from position  $b$  to position  $a$
- $C$  charges through  $R_1$  and current  $I$  flows in  $R_1$  and  $C$

## RC circuits

 

$$V_{DD} - V_1 - V_{out} = 0$$

$$V_{DD} = V_1 + V_{out}$$

Sub for  $V_{out}$  in terms of  $I$  and  $C$  (from earlier eqn.)

$$V_{DD} = IR_1 + \frac{1}{C} \int Idt$$

Differentiate wrt  $t$  gives

$$0 = R_1 \frac{dI}{dt} + \frac{I}{C} \quad \text{Then rearranging gives} \quad -\frac{dt}{CR_1} = \frac{dI}{I}$$

## RC circuits

Integrating both sides of the previous equation gives

$$-\frac{t}{CR_1} + a = \ln I$$

We now need to find the integration constant  $a$ .

To do this we look at the initial conditions at  $t = 0$ , i.e.,  $V_{out} = 0$ . This gives an initial current  $I_0 = V_{DD}/R_1$

$$a = \ln I_0 = \ln\left(\frac{V_{DD}}{R_1}\right)$$

So,

$$-\frac{t}{CR_1} + \ln I_0 = \ln I$$

$$-\frac{t}{CR_1} = \ln \frac{I}{I_0}$$

Antilog both sides,

$$e^{-t/CR_1} = \frac{I}{I_0}$$

$$I = I_0 e^{-t/CR_1}$$

## RC circuits

Now,

$$V_{out} = V_{DD} - V_1$$

and,

$$V_1 = IR_1$$

Substituting for  $V_1$  gives,

$$V_{out} = V_{DD} - IR_1$$


$$V_{out} = V_{DD} - R_1 I_0 e^{-t/CR_1}$$

Substituting for  $I_0$  gives,

$$V_{out} = V_{DD} - R_1 \frac{V_{DD}}{R_1} e^{-t/CR_1}$$


$$V_{out} = V_{DD} \left(1 - e^{-t/CR_1}\right)$$

Plotting yields,

 


$CR_1$  is known as the time constant – has units of seconds

## RC circuits

 


- Initially assume  $C$  is fully charged, i.e.,  $V_{out} = V_{DD}$  and the switch moves from position  $a$  to position  $c$
- $C$  discharges through  $R_2$  and current flows in  $R_2$  and  $C$

## RC circuits

 

The expression for  $V_{out}$  is,

$$V_{out} = V_{DD} e^{-t/CR_2}$$

 


## Basic Materials

- The electrical properties of materials are central to understanding the operation of electronic devices
- Their functionality depends upon our ability to control properties such as their resistance or current-voltage characteristics
- Whether a material is a conductor or insulator depends upon how strongly bound the outer valence electrons are to their atomic cores

 
## Insulators

- Consider a crystalline insulator, e.g., diamond
- Electrons are strongly bound and unable to move
- When a voltage difference is applied, the crystal will distort a bit, but no charge (i.e., electrons) will flow until breakdown occurs


 
## Conductors

- Consider a metal conductor, e.g., copper
- Electrons are weakly bound and free to move
- When a voltage difference is applied, the crystal will distort a bit, but charge (i.e., electrons) will flow




## Semiconductors

- Since there are many free electrons in a metal, it is difficult to control its properties
- Consequently, what we need is a material with a low electron density, i.e., a semiconductor
- By carefully controlling the electron density we can create a whole range of electronic devices


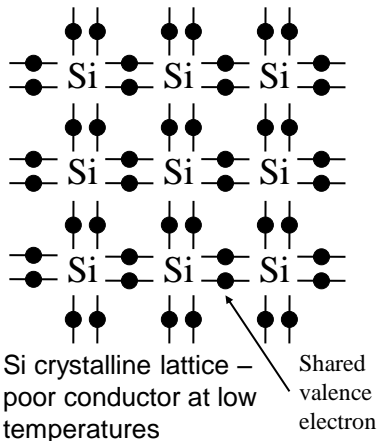
# Semiconductors

- Silicon (Si, Group IV) is a poor conductor of electricity, i.e., a 'semiconductor'




Si is *tetravalent*, i.e., it has 4 electrons in its *valance* band

Si crystals held together by '*covalent*' bonding

Recall that 8 valence electrons yield a stable state – each Si atom now appears to have 8 electrons, though in fact each atom only has a half share in them. Note this is a much more stable state than is the exclusive possession of 4 valence electrons
 
# Semiconductors

- As temperature rises conductivity rises



As temperature rises, thermal vibration of the atoms causes bonds to break: electrons are free to wander around the crystal.


When an electron breaks free (i.e., moves into the '*conduction band*' it leaves behind a '*hole*' or absence of negative charge in the lattice

The hole can appear to move if it is filled by an electron from an adjacent atom

The availability of free electrons makes Si a conductor (a poor one)
 
## n-type Si

- n-type silicon (Group IV) is doped with arsenic (Group V) that has an additional electron that is not involved in the bonds to the neighbouring Si atoms



The additional electron needs only a little energy to move into the conduction band.


This electron is free to move around the lattice

Owing to its negative charge, the resulting semiconductor is known as *n-type*

Arsenic is known as a *donor* since it donates an electron
 
## p-type Si

- p-type silicon (Group IV) is doped with boron (B, Group III)



The B atom has only 3 valence electrons, it accepts an extra electron from one of the adjacent Si atoms to complete its covalent bonds

This leaves a *hole* (i.e., absence of a valence electron) in the lattice


This hole is free to move in the lattice – actually it is the electrons that do the shifting, but the result is that the hole is shuffled from atom to atom.

The free hole has a positive charge, hence this semiconductor is *p-type*

B is known as an *acceptor*
 
# p-n Junction


- The key to building useful devices is combining p and n type semiconductors to form a p-n junction



- Electrons and holes diffuse across junction due to large concentration gradient
- On n-side, diffusion out of electrons leaves +ve charged donor atoms
- On p-side, diffusion out of holes leaves -ve charged acceptor atoms
- Leaves a space-charge (depletion) region with no free charges
- Space charge gives rise to electric field that opposes diffusion

- Equilibrium is reached where no more charges move across junction
- The pd associated with field is known as 'contact potential'




# Biased p-n Junction

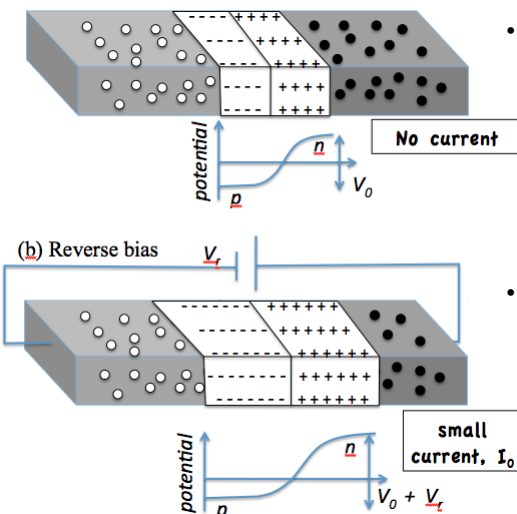


- With no external voltage some current flows due to diffusion of charges against junc electric field. Balanced by thermally generated electrons in p-type and holes in n-type. These are swept across junc by the field and this 'drift' current exactly balances diffusion current
- Reverse bias:** By making n-type +ve, electrons are removed from it increasing size of space charge region. Similarly holes are removed from p-type region. Thus space charge region and its associated field are increased.

- This reduces diffusion current but drift current is not significantly changed
- The net current is known as the reverse saturation current – order of nA

# Biased p-n Junction

   



Diode current-voltage characteristics

 

- With **forward bias**, on the p-side holes are pushed toward junction where they neutralise some of the -ve space charge.
- Similarly on the n-side, electrons are pushed toward the junction and neutralise some of the +ve space charge.
- So depletion region and associated field are reduced.
- This allows diffusion current to increase significantly. Reverse 'drift' current is virtually unchanged. Net current is now predominantly due to diffusion current and has the order of mA


- Thus the p-n junction allows significant current flow in only one direction
- This device is known as a **diode**

# Diode – Ideal Characteristic

  
 
## n-Channel MOSFET


- We will now introduce a more complex semiconductor device known as an n-channel Metal Oxide Semiconductor Field Effect Transistor (MOSFET) and see how it can be used to build logic circuits



The current flow from D to S ( $I_{DS}$ ) is controlled by the voltage applied between G and S ( $V_{GS}$ )


We will be describing enhancement mode devices in which no current flows ( $I_{DS}=0$ , i.e., the transistor is Off) when  $V_{GS}=0V$

## n-Channel MOSFET

 

Drain (and Source) diode reverse biased, so no path for current to flow from S to D, i.e., the transistor is **off**

# n-Channel MOSFET

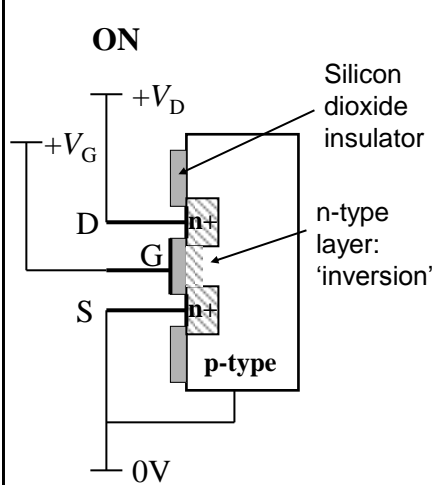

Consider the situation when the Gate (G) voltage ( $V_G$ ) is raised to a positive voltage, say  $V_D$



Electrons attracted to underside of the G, so this region is 'inverted' and becomes n-type. This region is known as the *channel*

There is now a continuous path from n-type S to n-type D, so electrons can flow from S to D, i.e., the transistor is **on**


The G voltage ( $V_G$ ) needed for this to occur is known as the *threshold voltage* ( $V_t$ ). Typically 0.3 to 0.7 V.
  
# p-Channel MOSFET


- Two varieties, namely p and n channel
- p-channel have the opposite construction, i.e., n-type substrate and p-type S and D regions



# n-MOSFET Characteristics

 

 
Plots V-I characteristics of the device for various Gate voltages ( $V_{GS}$ )





At a constant value of  $V_{DS}$ , we can also see that  $I_{DS}$  is a function of the Gate voltage,  $V_{GS}$

The transistor begins to conduct when the Gate voltage,  $V_{GS}$ , reaches the Threshold voltage:  $V_T$

# n-MOS Inverter

 

  We can use the graphical approach to determine the relationship between  $V_{in}$  and  $V_{out}$




Note  $V_{in} = V_{GS}$  and  $V_{out} = V_{DS}$


## n-MOS Inverter

- Note it does not have the 'ideal' characteristic that we would like from an 'inverter' function

Actual

 


Ideal

 

However if we specify suitable voltage thresholds, we can achieve a 'binary' action.

## n-MOS Inverter

Actual

 

So if we say:

voltage  $> 9V$  is logic 1

voltage  $< 2V$  is logic 0

The gate will work as follows:

$V_{in} > 9V$  then  $V_{out} < 2V$  and if

$V_{in} < 2V$  then  $V_{out} > 9V$




## n-MOS Logic

- It is possible (and was done in the early days) to build other logic functions, e.g., NOR and NAND using n-MOS transistors
- However, n-MOS logic has fundamental problems:
  - Speed of operation
  - Power consumption
 
## n-MOS Logic


- One of the main speed limitations is due to stray capacitance owing to the metal track used to connect gate inputs and outputs. This has a finite capacitance to ground, i.e., the 0V connection.
  - We modify the circuit model to include this 'stray' capacitance  $C$



## n-MOS Logic

- To see the effect of this stray capacitance we will consider what happens when the transistor is ON (so that  $V_{out}=0V$  at beginning), then turned OFF and then turned ON again
- When the transistor is OFF it is effectively an open circuit, i.e., we can eliminate it from the circuit diagram

Transistor turned OFF

 

The problem with capacitors is that the voltage across them cannot change instantaneously.


The 'stray' capacitor  $C$  charges through  $R_1$ . Note  $C$  is initially discharged, i.e.,  $V_{out}=0V$

## n-MOS Logic

- Using the previous result for a capacitor charging via a resistor we can write:

$$V_{out} = V_{DD} \left( 1 - e^{-t/CR_1} \right)$$

Plotting yields,

 


Where  $CR_1$  is known as the time constant – has units of seconds

## n-MOS Logic

- When the transistor is ON it is effectively a low value resistor,  $R_{ON}$ . (say  $< 100\Omega$ )
- We will assume capacitor is charged to a voltage  $V_{DD}$  just before the transistor is turned ON

Transistor turned ON again

 


'Stray' capacitor  $C$  discharges through  $R_{ON}$

The expression for  $V_{out}$  is,


$$V_{out} = V_{DD}e^{-t/CR_{ON}}$$

Plotting yields,

 

 
## n-MOS Logic

- When the transistor turns OFF,  $C$  charges through  $R_1$ . This means the rising edge is slow since it is defined by the large time constant  $R_1C$  (since  $R_1$  is high).
- When the transistor turns ON,  $C$  discharges through it, i.e., effectively resistance  $R_{ON}$ . The speed of the falling edge is faster since the transistor ON resistance ( $R_{ON}$ ) is low.



## n-MOS Logic

- Power consumption is also a problem

 

Transistor OFF

No problem since no current is flowing through  $R_1$ , i.e.,  $V_{out} = 10\text{V}$

Transistor ON


This is a problem since current is flowing through  $R_1$ . For example, if  $V_{out} = 1\text{V}$  (corresponds with  $V_{in} = 10\text{V}$  and  $I_D = I = 9\text{mA}$ ), the power dissipated in the resistor is the product of voltage across it and the current through it, i.e.,

$$P_{disp} = I \times V_1 = 9 \times 10^{-3} \times 9 = 81 \text{ mW}$$

## CMOS Logic


- To overcome these problems, complementary MOS (CMOS) logic was developed
- As the name implies it uses p-channel as well as n-channel MOS transistors
- Essentially, p-MOS transistors are n-MOS transistors but with all the polarities reversed!

# CMOS Inverter

 


Using the graphical approach we can show that the switching characteristics are now much better than for the n-MOS inverter

$V_{in}$	N-MOS	P-MOS	$V_{out}$
low	off	on	high
high	on	off	low

 
 
# CMOS Inverter

- It can be shown that the transistors only dissipate power while they are switching.




This is when both transistors are on. When one or the other is off, the power dissipation is zero

CMOS is also better at driving capacitive loads since it has active transistors on both rising and falling edges

## CMOS Gates

- CMOS can also be used to build NAND and NOR gates
- They have similar electrical properties to the CMOS inverter

## CMOS NAND Gate

 

$V_A$	$V_B$	T1	T2	T3	T4	$V_Y$
low	low	on	on	off	off	high
low	high	on	off	on	off	high
high	low	off	on	off	on	high
high	high	off	off	on	on	low

## Logic Families

- **NMOS** – compact, slow, cheap, obsolete
- **CMOS** – Older families slow (4000 series about 60ns), but new ones (74AC) much faster (3ns). 74HC series popular
- **TTL** – Uses bipolar transistors. Known as 74 series. Note that most 74 series devices are now available in CMOS. Older versions slow (LS about 16ns), newer ones faster (AS about 2ns)
- **ECL** – High speed, but high power consumption

## Logic Families


- Best to stick with the particular family which has the best performance, power consumption cost trade-off for the required purpose
- It is possible to mix logic families and sub-families, but care is required regarding the acceptable logic voltage levels and gate current handling capabilities

## Meaning of Voltage Levels

- As we have seen, the relationship between the input voltage to a gate and the output voltage depends upon the particular implementation technology
- Essentially, the signals between outputs and inputs are 'analogue' and so are susceptible to corruption by additive noise, e.g., due to cross talk from signals in adjacent wires
- What we need is a method for quantifying the tolerance of a particular logic to noise
 
## Noise Margin

- Tolerance to noise is quantified in terms of the noise margin



$$\text{Logic 0 noise margin} = V_{IL}(max) - V_{OL}(max)$$

$$\text{Logic 1 noise margin} = V_{OH}(min) - V_{IH}(min)$$



## Noise Margin

- For the 74 series High Speed CMOS (HCMOS) used in the hardware labs (using the values from the data sheet):

$$\text{Logic 0 noise margin} = V_{IL(\text{max})} - V_{OL(\text{max})}$$

$$\text{Logic 0 noise margin} = 1.35 - 0.1 = 1.25 \text{ V}$$

$$\text{Logic 1 noise margin} = V_{OH(\text{min})} - V_{IH(\text{min})}$$

$$\text{Logic 1 noise margin} = 4.4 - 3.15 = 1.25 \text{ V}$$

See the worst case noise margin = 1.25V, which is much greater than the 0.4 V typical of TTL series devices. Consequently HCMOS devices can tolerate more noise pick-up before performance becomes compromised