

# Digital Electronics – Electronics, Devices and Circuits

Dr. I. J. Wassell

## Introduction

- In the coming lectures we will consider how logic gates can be built using electronic circuits
- First, basic concepts concerning electrical circuits and components will be introduced
- This will enable the analysis of linear circuits, i.e., one where superposition applies:
  - If an input  $x_1(t)$  gives an output  $y_1(t)$ , and input  $x_2(t)$  gives an output  $y_2(t)$ , then input  $[x_1(t)+x_2(t)]$  gives an output  $[y_1(t)+y_2(t)]$

## Introduction

- However, logic circuits are non-linear, consequently we will introduce a graphical technique for analysing such circuits
- Semiconductor materials, metal oxide field effect transistors (MOSFET) will be introduced
- Building an NMOS inverter from an n-channel (MOSFET) will be described
- CMOS logic built using MOSFETs will be presented
- Finally, we will look at interfacing to the analogue world

## Basic Electricity


- An electric current is produced when charged particles (e.g., electrons in metals, or electrons and ions in a gas or liquid) move in a definite direction
- In metals, the outer electrons are held loosely by their atoms and are free to move around the fixed positive metal ions
- This free electron motion is random, and so there is no net flow of charge in any direction, i.e., no current flow

## Basic Electricity

- If a metal wire is connected across the terminals of a battery, the battery acts as an 'electron pump' and forces the free electrons to drift toward the +ve terminal and in effect flow through the battery
- The drift speed of the free electrons is low, e.g., < 1 mm per second owing to frequent collisions with the metal ions.
- However, they all start drifting together as soon as the battery is applied
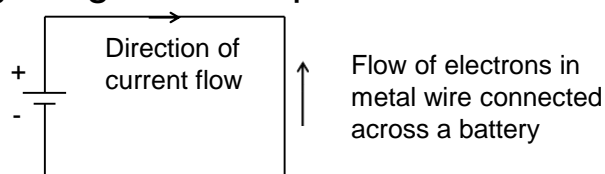
## Basic Electricity

- The flow of electrons in one direction is known as an electric current and reveals itself by making the metal warmer and by deflecting a nearby magnetic compass



- Before electrons were discovered it was imagined that the flow of current was due to positively charged particles flowing out of +ve toward -ve battery terminal

## Basic Electricity


- Note that 'conventional' current flow is still defined as flowing from the +ve toward the –ve battery terminal (i.e., the opposite way to the flow of the electrons in the metal)!
- A huge number of charged particles (electrons in the case of metals) drift past each point in a circuit per second.
- The unit of charge is the *Coulomb (C)* and one electron has a charge of  $1.6 \cdot 10^{-19} \text{ C}$

## Basic Electricity

- Thus one C of charge is equivalent to  $6.25 \cdot 10^{18}$  electrons
- When one C of charge passes a point in a circuit per second, this is defined as a current ( $I$ ) of 1 *Ampere (A)*, i.e.,  $I = Q/t$ , where  $Q$  is the charge (C) and  $t$  is time in seconds (s), i.e., current is the rate of flow of charge.
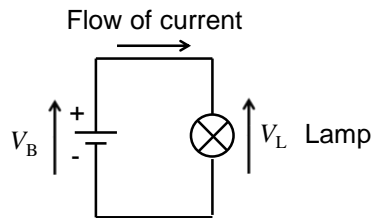
## Basic Electricity

- In the circuit shown below, it is the battery that supplies the electrical force and energy that drives the electrons around the circuit.



- The electromotive force (emf)  $V_B$  of a battery is defined to be 1 *Volt* (V) if it gives 1 *Joule* (J) of electrical energy to each C of charge passing through it.

## Basic Electricity

- The lamp in the previous circuit changes most of the electrical energy carried by the free electrons into heat and light
- The potential difference (pd)  $V_L$  across the lamp is defined to be 1 *Volt* (V) if it changes 1 *Joule* (J) of electrical energy into other forms of energy (e.g., heat and light) when 1 C of charge passes through it, i.e.,  $V_L = E/Q$ , where  $E$  is the energy dissipated (J) and  $Q$  is the charge (C)

## Basic Electricity

- Note that pd and emf are usually called *voltages* since both are measured in V
- The flow of electric charge in a circuit is analogous to the flow of water in a pipe. Thus a pressure difference is required to make water flow – To move electric charge we consider that a pd is needed, i.e., whenever there is a current flowing between 2 points in a circuit there must be a pd between them

## Basic Electricity

- What is the power dissipated ( $P_L$ ) in the lamp in the previous circuit?
- $P_L = E/t$  (J/s). Previously we have,  $E = QV_L$ , and so,  $P_L = QV_L/t$  (W) .
- Now substitute  $Q = It$  from before to give,  $P_L = It V_L /t = IV_L$  (W) , an expression that hopefully is familiar

## Basic Electricity


- So far, we have only considered metallic conductors where the charge is carried by 'free' electrons in the metal lattice.
- We will now consider the electrical properties of some other materials, specifically, *insulators* and *semiconductors*

## Basic Materials

- The electrical properties of materials are central to understanding the operation of electronic devices
- Their functionality depends upon our ability to control properties such as their current-voltage characteristics
- Whether a material is a conductor or insulator depends upon how strongly bound the outer valence electrons are to their atomic cores

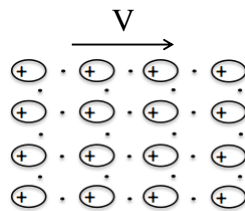
## Insulators

- Consider a crystalline insulator, e.g., diamond
- Electrons are strongly bound and unable to move
- When a voltage difference is applied, the crystal will distort a bit, but no charge (i.e., electrons) will flow until breakdown occurs


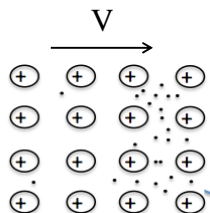
## Conductors

- Consider a metal conductor, e.g., copper
- Electrons are weakly bound and free to move
- When a voltage difference is applied, the crystal will distort a bit, but charge (i.e., electrons) will flow





## Semiconductors

- Since there are many free electrons in a metal, it is difficult to control its electrical properties
- Consequently, what we need is a material with a low electron density, i.e., a semiconductor, e.g., Silicon
- By carefully controlling the electron density we can create a whole range of electronic devices

## Semiconductors

- We can create *n*-type silicon (Group 4) by doping with arsenic (Group V) that donates an additional electron
- This electron is free to move around the silicon lattice
- Owing to its negative charge, the resulting semiconductor is known as *n*-type

## Semiconductors

- Similarly we can create *p*-type silicon (Group 4) by doping with Boron (Group 3) that accepts an additional electron
- This leaves a *hole* (i.e., absence of a valence electron) in the lattice
- This hole is free to move in the lattice – actually it is the electrons in the lattice that do the shifting, but the net result is that the hole is shuffled from atom to atom.
- The free hole has a positive charge, hence this semiconductor is *p*-type

## Semiconductors

- The Metal Oxide Semiconductor Field Effect Transistor (MOSFET) devices that are used to implement virtually all digital logic circuits are fabricated from *n* and *p* type silicon
- Later on, we will see how MOSFETs can be used to implement digital logic circuits

## Circuit Theory

- Electrical engineers have an alternative (but essentially equivalent) view concerning pd.
- That is, conductors, to a greater or lesser extent, oppose the flow of current. This 'opposition' is quantified in terms of *resistance* ( $R$ ). Thus the greater is the resistance, the larger is the potential difference measured across the conductor (for a given current).


## Circuit Theory

- The *resistance* ( $R$ ) of a conductor is defined as  $R=V/I$ , where  $V$  is the pd across the conductor and  $I$  is the current through the conductor.
- This is known as *Ohms Law* and is usually expressed as  $V=IR$ , where resistance is defined to be in Ohms ( $\Omega$ ).
- So for an *ohmic* (i.e., linear) conductor, plotting  $I$  against  $V$  yields a straight line through the origin
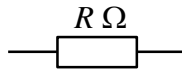
## Circuit Theory

- Conductors made to have a specific value of resistance are known as *resistors*.

- They have the following symbol in an electrical circuit:




- Analogy:

- The flow of electric charges can be compared with the flow of water in a pipe.
- A pressure (voltage) difference is needed to make water (charges) flow in a pipe (conductor).
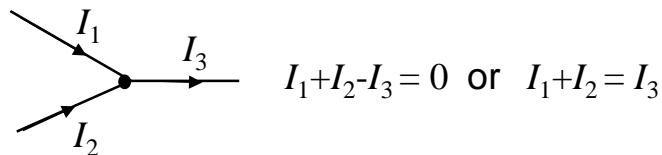
## Circuit Theory


- Kirchhoff's Current Law – The sum of currents entering a junction (or node) is zero, e.g.,



- That is, what goes into the junction is equal to what comes out of the junction – Think water pipe analogy again!
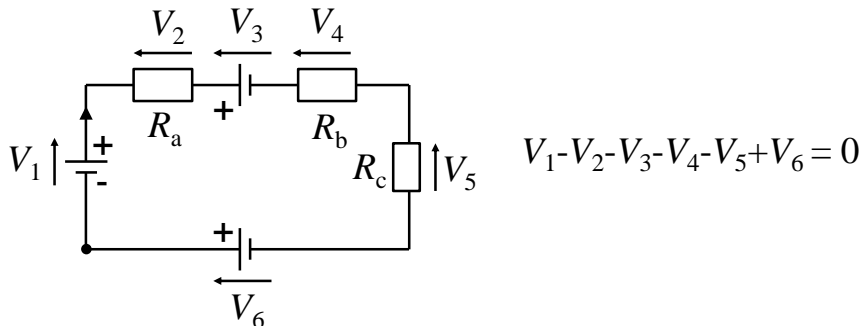
## Circuit Theory


- Kirchhoff's Voltage Law – In any closed loop of an electric circuit the sum of all the voltages in that loop is zero, e.g.,



- We will now analyse a simple 2 resistor circuit known as a *potential divider*
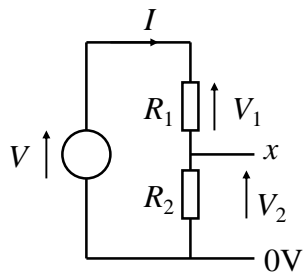
## Potential Divider

- What is the voltage at point  $x$  relative to the 0V point?



$$V = V_1 + V_2$$

$$V_1 = IR_1 \quad V_2 = IR_2$$

$$V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$I = \frac{V}{(R_1 + R_2)}$$

$$V_x = V_2 = \frac{V}{(R_1 + R_2)} R_2 = V \left( \frac{R_2}{R_1 + R_2} \right)$$


Note: circle represents an ideal voltage source, i.e., a perfect battery

## Solving Non-linear circuits

- As mentioned previously, not all electronic devices have linear I-V characteristics, importantly in our case this includes the FETs used to build logic circuits
- Consequently we cannot easily use the algebraic approach applied previously to the potential divider. Instead, we will use a graphical approach
- Firstly though, we will apply the graphical approach to the potential divider example


## Potential Divider

- How can we do this graphically?

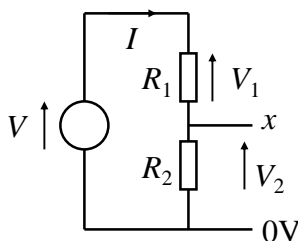

So if  $V = 10\text{V}$ ,  $R_1 = 1\Omega$  and  $R_2 = 2\Omega$

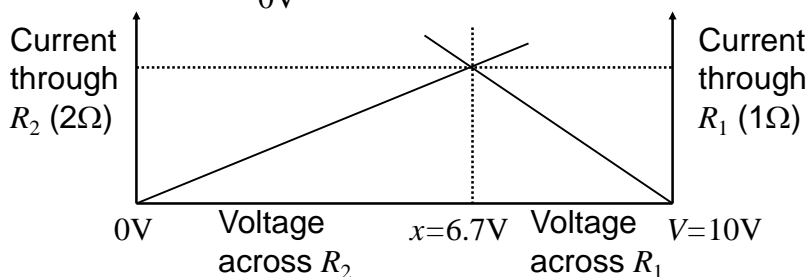
$$V_x = V \left( \frac{R_2}{R_1 + R_2} \right) = 10 \left( \frac{2}{1 + 2} \right) = 6.7\text{V}$$



## Graphical Approach


- Clearly approach works for a linear circuit.
- How could we apply this if we have a non-linear device, e.g., a transistor in place of  $R_2$ ?
- What we do is substitute the  $V$ - $I$  characteristic of the non-linear device in place of the linear characteristic (a straight line due to Ohm's Law) used previously for  $R_2$

## Graphical Approach

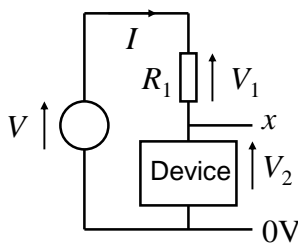


So if  $V = 10V$  and  $R_1 = 1\Omega$

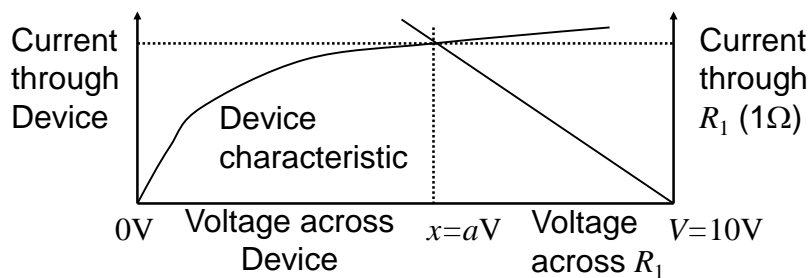The voltage at  $x$  is  $aV$  as shown in the graph


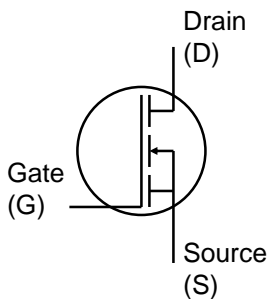
## n-Channel MOSFET

- We will now briefly introduce the n-channel MOSFET
- The charge carriers in this device are electrons




The current flow from D to S ( $I_{DS}$ ) is controlled by the voltage applied between G and S ( $V_{GS}$ ), i.e., G has to be +ve wrt S for current  $I_{DS}$  to flow (transistor **On**)

We will consider enhancement mode devices in which no current flows ( $I_{DS}=0$ , i.e., the transistor is **Off**) when  $V_{GS}=0V$
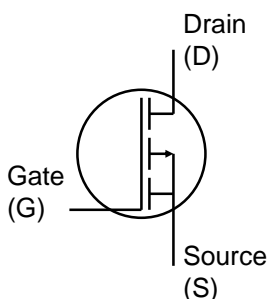
## p-Channel MOSFET

- Similarly we have p-channel MOSFETs where the charge carriers are holes




The current flow from S to D ( $I_{DS}$ ) is controlled by the voltage applied between G and S ( $V_{GS}$ ), i.e., G has to be -ve wrt S for current  $I_{DS}$  to flow (transistor **On**)


We will be consider enhancement mode devices in which no current flows ( $I_{DS}=0$ , i.e., the transistor is **Off**) when  $V_{GS}=0V$



# n-MOSFET Characteristics

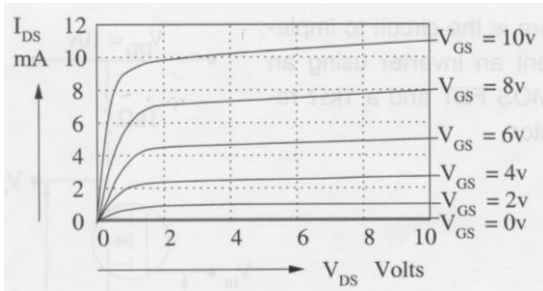

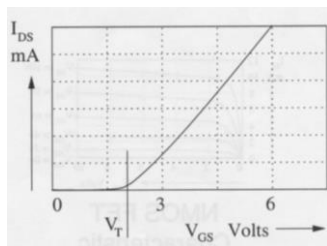
Plots V-I characteristics of the device for various Gate voltages ( $V_{GS}$ )





At a constant value of  $V_{DS}$ , we can also see that  $I_{DS}$  is a function of the Gate voltage,  $V_{GS}$

The transistor begins to conduct when the Gate voltage,  $V_{GS}$ , reaches the Threshold voltage:  $V_T$

# n-MOS Inverter

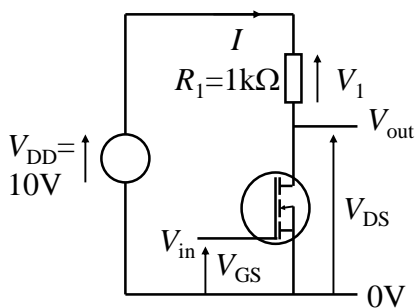

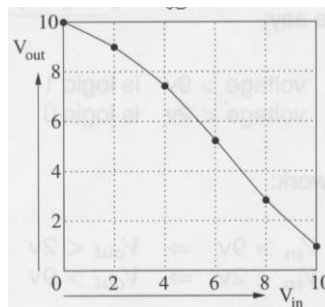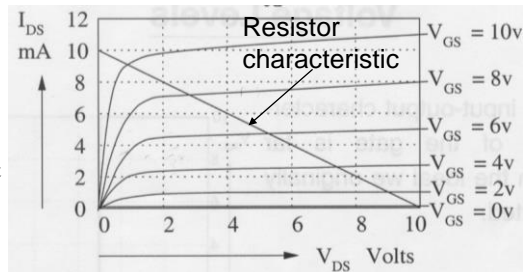We can use the graphical approach to determine the relationship between  $V_{in}$  and  $V_{out}$




Note  $V_{in} = V_{GS}$  and  $V_{out} = V_{DS}$


## n-MOS Inverter

- Note it does not have the 'ideal' characteristic that we would like from an 'inverter' function

Actual

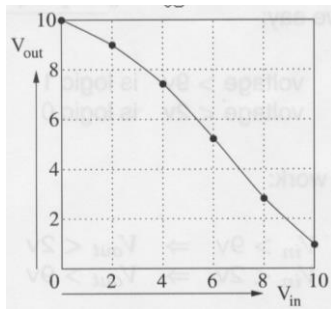


Ideal

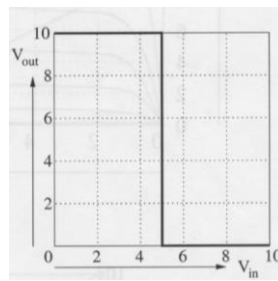

However if we specify suitable voltage thresholds, we can achieve a 'binary' action.

## n-MOS Inverter

Actual

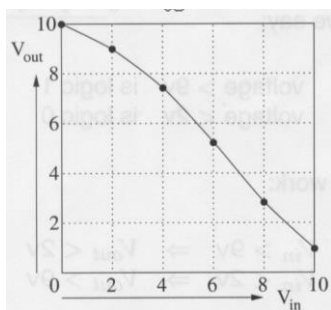

So if we say:

voltage  $> 9V$  is logic 1

voltage  $< 2V$  is logic 0

The gate will work as follows:

$V_{in} > 9V$  then  $V_{out} < 2V$  and if


$V_{in} < 2V$  then  $V_{out} > 9V$

## n-MOS Logic

- It is possible (and was done in the early days) to build other logic functions, e.g., NOR and NAND using n-MOS transistors
- However, n-MOS logic has fundamental problems:
  - Speed of operation
  - Power consumption
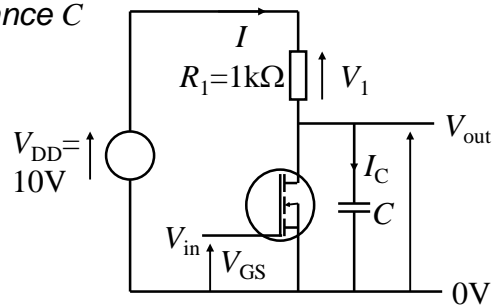
## n-MOS Logic


- One of the main speed limitations is due to stray capacitance owing to the metal track used to connect gate inputs and outputs. This has a finite capacitance to ground, i.e., the 0V connection.
  - We modify the circuit model to include this *stray capacitance*  $C$



- To see the effect of stray capacitance, we first consider the electrical properties of capacitors.
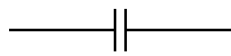
## Devices that store energy

- Some common circuit components store energy, e.g., capacitors and inductors.
- We will now consider capacitors in detail.
- The physical construction of a capacitor is effectively 2 conductors separated by a non-conductor (or dielectric as it is known).



Symbol of a Capacitor

Unit of capacitance: Farads (F)

- Electrical charge can be stored in such a device.

## Capacitors

- So, parallel conductors brought sufficiently close (but not touching) will form a capacitor
- Parallel conductors often occur on circuit boards (and on integrated circuits), thus creating unwanted (or parasitic) capacitors.
- We will see that parasitic capacitors can have a significant negative impact on the switching characteristics of digital logic circuits.


## Capacitors

- The relationship between the charge  $Q$  stored in a capacitor  $C$  and the voltage  $V$  across its terminals is  $Q = VC$ .
- As mentioned previously, current is the rate of flow of charge, i.e.,  $dQ/dt = I$ , or alternatively,  $Q = \int Idt$ .
- So we can write,


$$V = \frac{1}{C} \int Idt$$
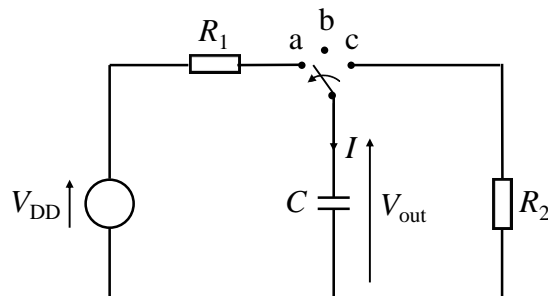
## Capacitors

- We now wish to investigate what happens when sudden changes in configuration occur in a simple resistor-capacitor (RC) circuit.




## RC circuits

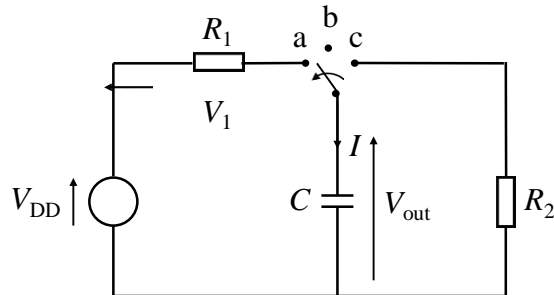

- Initially,  $C$  is discharged, i.e.,  $V_{out}=0$  and the switch moves from position  $b$  to position  $a$
- $C$  charges through  $R_1$  and current  $I$  flows in  $R_1$  and  $C$

## RC circuits

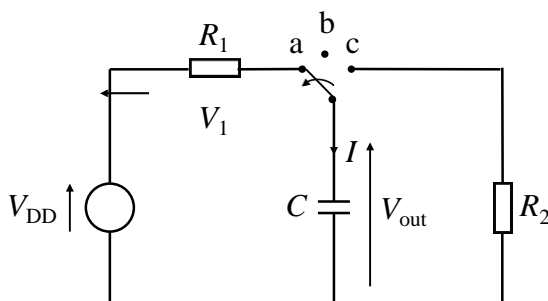

$$V_{DD} - V_1 - V_{out} = 0$$

$$V_{DD} = V_1 + V_{out}$$

Sub for  $V_{out}$  in terms of  $I$  and  $C$  (from earlier eqn.)

$$V_{DD} = IR_1 + \frac{1}{C} \int Idt$$

Differentiate wrt  $t$  gives

$$0 = R_1 \frac{dI}{dt} + \frac{I}{C} \quad \text{Then rearranging gives} \quad -\frac{dt}{CR_1} = \frac{dI}{I}$$

## RC circuits

Integrating both sides of the previous equation gives

$$-\frac{t}{CR_1} + a = \ln I$$

We now need to find the integration constant  $a$ .

To do this we look at the initial conditions at  $t = 0$ , i.e.,  $V_{out} = 0$ . This gives an initial current  $I_0 = V_{DD}/R_1$

$$a = \ln I_0 = \ln\left(\frac{V_{DD}}{R_1}\right)$$

So,

$$-\frac{t}{CR_1} + \ln I_0 = \ln I$$

$$-\frac{t}{CR_1} = \ln \frac{I}{I_0}$$

Antilog both sides,

$$e^{-t/CR_1} = \frac{I}{I_0}$$

$$I = I_0 e^{-t/CR_1}$$

## RC circuits

Now,

$$V_{out} = V_{DD} - V_1$$

and,

$$V_1 = IR_1$$

Substituting for  $V_1$  gives,

$$V_{out} = V_{DD} - IR_1$$


$$V_{out} = V_{DD} - R_1 I_0 e^{-t/CR_1}$$

Substituting for  $I_0$  gives,

$$V_{out} = V_{DD} - R_1 \frac{V_{DD}}{R_1} e^{-t/CR_1}$$


$$V_{out} = V_{DD} \left(1 - e^{-t/CR_1}\right)$$

Plotting yields,

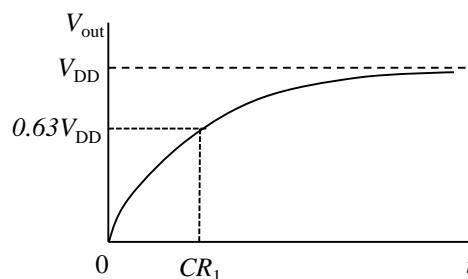


$CR_1$  is known as the time constant – has units of seconds

## RC circuits

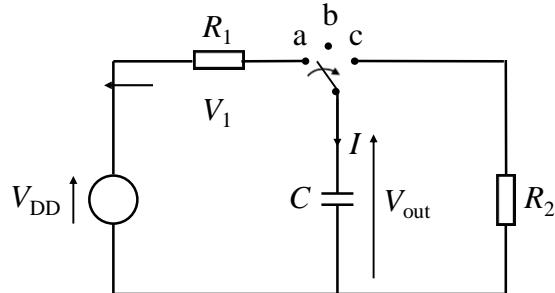


- Initially assume  $C$  is fully charged, i.e.,  $V_{out} = V_{DD}$  and the switch moves from position  $a$  to position  $c$
- $C$  discharges through  $R_2$  and current flows in  $R_2$  and  $C$

## RC circuits

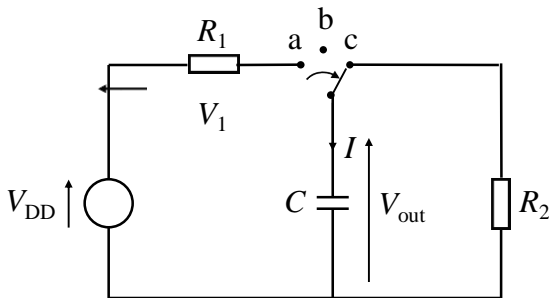

The expression for  $V_{out}$  is,

$$V_{out} = V_{DD} e^{-t/CR_2}$$

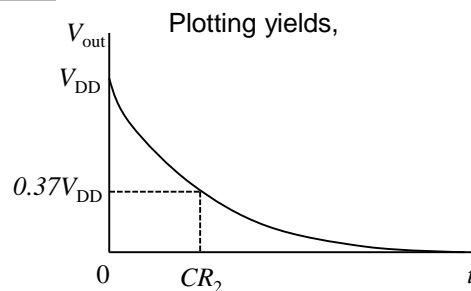




## n-MOS Logic

- To see the effect of this stray capacitance we will consider what happens when the transistor is ON (so that  $V_{out}=0V$  at beginning), then turned OFF and then turned ON again
- When the transistor is OFF it is effectively an open circuit, i.e., we can eliminate it from the circuit diagram

Transistor turned OFF

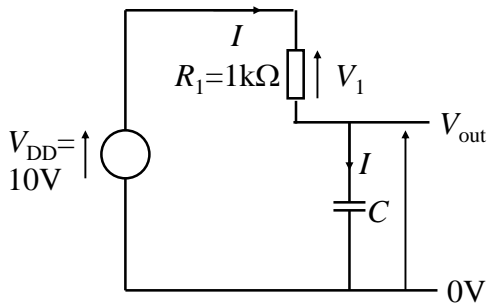

The problem with capacitors is that the voltage across them cannot change instantaneously.


The 'stray' capacitor  $C$  charges through  $R_1$ . Note  $C$  is initially discharged, i.e.,  $V_{out}=0V$

## n-MOS Logic

- Using the previous result for a capacitor charging via a resistor we can write:

$$V_{out} = V_{DD} \left( 1 - e^{-t/CR_1} \right)$$

Plotting yields,

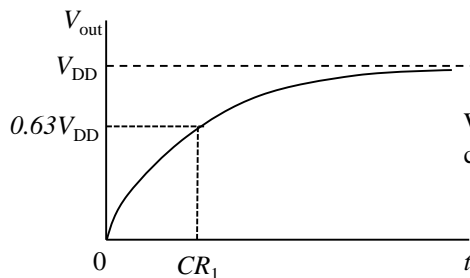


Where  $CR_1$  is known as the time constant – has units of seconds

## n-MOS Logic

- When the transistor is ON it is effectively a low value resistor,  $R_{ON}$ . (say  $< 100\Omega$ )
- We will assume capacitor is charged to a voltage  $V_{DD}$  just before the transistor is turned ON

Transistor turned ON again

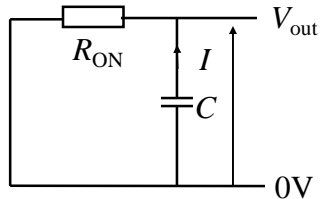


'Stray' capacitor  $C$  discharges through  $R_{ON}$

The expression for  $V_{out}$  is,


$$V_{out} = V_{DD} e^{-t/CR_{ON}}$$

Plotting yields,

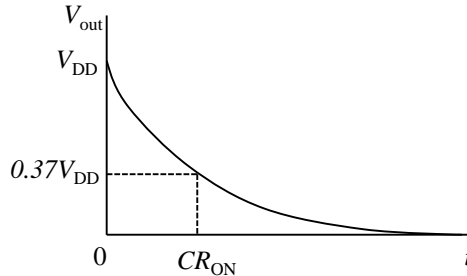

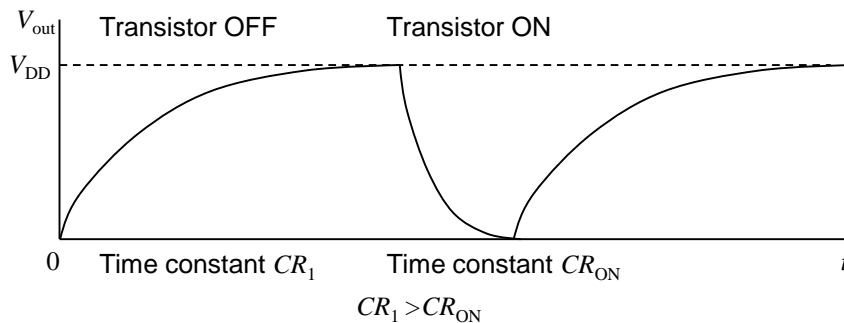
## n-MOS Logic

- When the transistor turns OFF,  $C$  charges through  $R_1$ . This means the rising edge is slow since it is defined by the large time constant  $R_1C$  (since  $R_1$  is high).
- When the transistor turns ON,  $C$  discharges through it, i.e., effectively resistance  $R_{ON}$ . The speed of the falling edge is faster since the transistor ON resistance ( $R_{ON}$ ) is low.



## n-MOS Logic

- Power consumption is also a problem

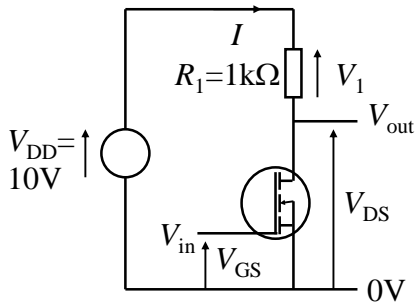

Transistor OFF

No problem since no current is flowing through  $R_1$ , i.e.,  $V_{out} = 10\text{V}$

Transistor ON


This is a problem since current is flowing through  $R_1$ . For example, if  $V_{out} = 1\text{V}$  (corresponds with  $V_{in} = 10\text{V}$  and  $I_D = I = 9\text{mA}$ ), the power dissipated in the resistor is the product of voltage across it and the current through it, i.e.,

$$P_{disp} = I \times V_1 = 9 \times 10^{-3} \times 9 = 81 \text{ mW}$$

## CMOS Logic


- To overcome these problems, complementary MOS (CMOS) logic was developed
- As the name implies it uses p-channel as well as n-channel MOS transistors
- Essentially, p-MOS transistors are n-MOS transistors but with all the polarities reversed!

## CMOS Inverter

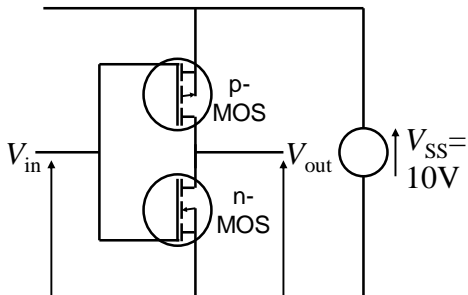


Using the graphical approach we can show that the switching characteristics are now much better than for the n-MOS inverter

$V_{in}$	N-MOS	P-MOS	$V_{out}$
low	off	on	high
high	on	off	low

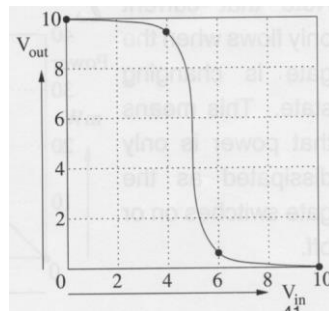
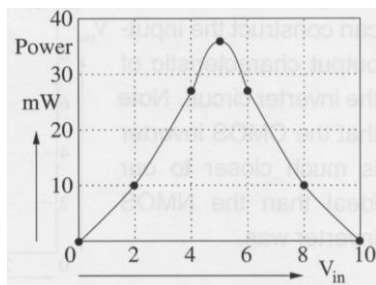
## CMOS Inverter

- It can be shown that the transistors only dissipate power while they are switching.




This is when both transistors are on. When one or the other is off, the power dissipation is zero

CMOS is also better at driving capacitive loads since it has active transistors on both rising and falling edges

## CMOS Gates

- CMOS can also be used to build NAND and NOR gates
- They have similar electrical properties to the CMOS inverter

## CMOS NAND Gate

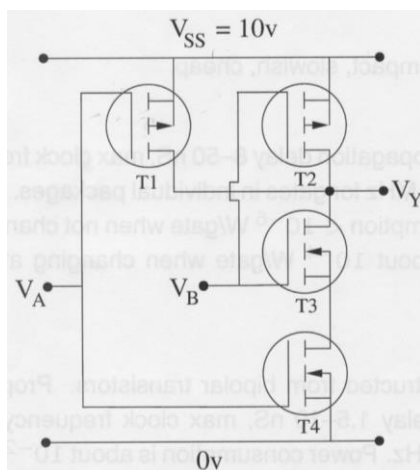

$V_A$	$V_B$	T1	T2	T3	T4	$V_Y$
low	low	on	on	off	off	high
low	high	on	off	on	off	high
high	low	off	on	off	on	high
high	high	off	off	on	on	low

## Logic Families

- **NMOS** – compact, slow, cheap, obsolete
- **CMOS** – Older families slow (4000 series about 60ns), but new ones (74AC) much faster (3ns). 74HC series popular
- **TTL** – Uses bipolar transistors. Known as 74 series. Note that most 74 series devices are now available in CMOS. Older versions slow (LS about 16ns), newer ones faster (AS about 2ns)
- **ECL** – High speed, but high power consumption

## Logic Families


- Best to stick with the particular family which has the best performance, power consumption cost trade-off for the required purpose
- It is possible to mix logic families and sub-families, but care is required regarding the acceptable logic voltage levels and gate current handling capabilities

## Meaning of Voltage Levels

- As we have seen, the relationship between the input voltage to a gate and the output voltage depends upon the particular implementation technology
- Essentially, the signals between outputs and inputs are 'analogue' and so are susceptible to corruption by additive noise, e.g., due to cross talk from signals in adjacent wires
- What we need is a method for quantifying the tolerance of a particular logic to noise
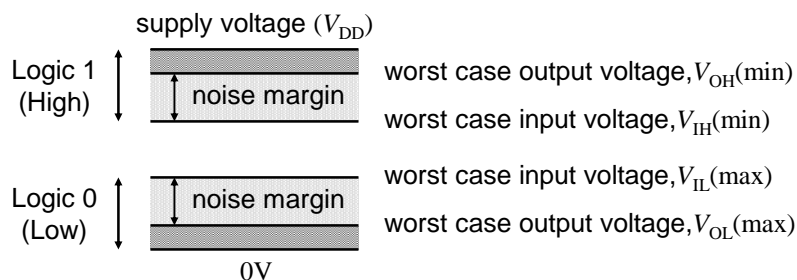
## Noise Margin

- Tolerance to noise is quantified in terms of the noise margin



$$\text{Logic 0 noise margin} = V_{IL}(\max) - V_{OL}(\max)$$

$$\text{Logic 1 noise margin} = V_{OH}(\min) - V_{IH}(\min)$$

## Noise Margin

- For the 74 series High Speed CMOS (HCMOS) used in the hardware labs (using the values from the data sheet):

$$\text{Logic 0 noise margin} = V_{IL(\text{max})} - V_{OL(\text{max})}$$

$$\text{Logic 0 noise margin} = 1.35 - 0.1 = 1.25 \text{ V}$$

$$\text{Logic 1 noise margin} = V_{OH(\text{min})} - V_{IH(\text{min})}$$

$$\text{Logic 1 noise margin} = 4.4 - 3.15 = 1.25 \text{ V}$$

See the worst case noise margin = 1.25V, which is much greater than the 0.4 V typical of TTL series devices.

Consequently HCMOS devices can tolerate more noise pick-up before performance becomes compromised

## Interfacing to the 'Analogue World'

- Digital electronic systems often need to interface to the 'analogue' real world. For example:
  - To convert an analogue audio signal to a digital format we need an analogue to digital converter (ADC)
  - Similarly to convert a digitally represented signal into an analogue signal we need to use a digital to analogue converter (DAC)
- ADCs and DACs are implemented in various ways depending upon factors such as conversion speed, resolution and power consumption




# Analogue to Digital Conversion

- ADC is a 2 stage process:
  - Regular sampling to convert the continuous time analogue signal into a signal that is discrete in time, i.e., it only exists at multiples of the sample time  $T$ . Thus  $x(t)$  can be represented as  $x(0)$ ,  $x(T)$ ,  $x(2T)$ ,  $x(3T)$ ....
  - These sample values can still take continuous amplitude values, hence the next step is to represent them using only discrete values in the amplitude domain. To do this the samples are quantised in amplitude, i.e., they are constrained to take one of only  $M$  possible amplitude values
  - Each of these discrete amplitude levels is represented by an  $n$ -bit binary code
  - Thus in an  $n$ -bit ADC, there are  $M=2^n$  quantisation levels
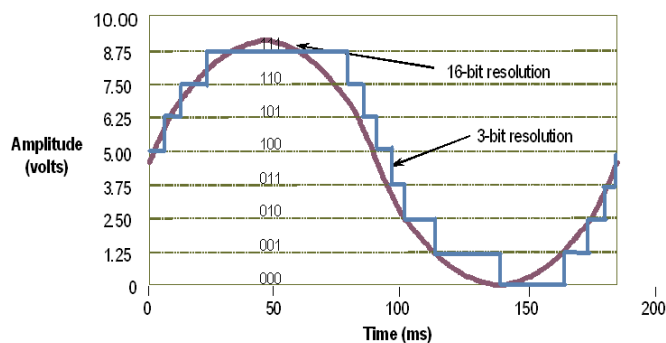
# Analogue to Digital Conversion

- Thus the ADC process introduces 'quantisation error' owing to the finite number of possible amplitude levels that can be represented
- The greater is the number of quantisation levels (i.e., 'bits' in the ADC), the lower will be the quantisation error, but at the cost of a higher bit rate



## Analogue to Digital Conversion

- In addition, the sample rate ( $1/T$ ) must be at least twice the highest frequency in the analogue signal being sampled – known as the Nyquist rate
- To ensure this happens, the analogue signal is often passed through a low pass filter that will remove frequencies above a specified maximum
- If the Nyquist rate is not satisfied, the sampled signal will be subject to ‘alias distortion’ that cannot be removed and will be present in the reconstructed analogue signal

## Analogue to Digital Conversion

- The ADC also requires that the input signal suits its specified amplitude range. Usually, the ADC has a range covering several Volts, while the signal from the transducer can be of the order of mV
- Consequently, amplification (a voltage gain  $>1$ ) of the analogue signal is usually required before being input to the ADC
- If not, the digitised signal will have poor quality (i.e., a low signal to quantisation noise ratio)
- Operational amplifier based ‘Gain blocks’ in front of the ADC are often used since they have predictable performance and are straightforward to use


## Digital to Analogue Conversion

- A DAC is used to convert the digitised sample values back to an analogue signal.
- A low pass filter (one that removes high frequencies) usually follows the DAC to yield a smooth continuous time signal
- Operational amplifier based buffer amplifiers are also often used following the DAC to prevent the load (e.g., transducers such as headphones) affecting the operation of the DAC

## Operational Amplifier Circuits

- Operational amplifiers (or 'Op-Amps) have 2 inputs (known as inverting (-) and non-inverting (+)) and a single output
- They can be configured to implement gain blocks (i.e., amplifiers) and many other functions, e.g., filters, summing blocks
- We will now look at several common op-amp based amplifier configurations, specifically inverting, non-inverting and unity gain buffer
- We will assume the use of 'ideal' op-amps, i.e., infinite input resistance (zero input current) and infinite gain.

## Inverting Amplifier

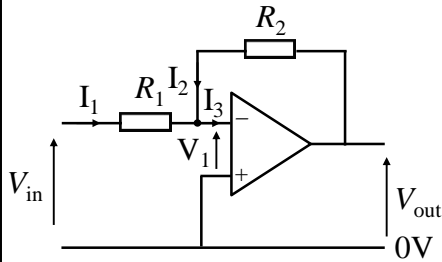

$$I_1 + I_2 - I_3 = 0$$

Now,  $I_3 = 0$  since the input resistance of the op amp is  $\infty$ , so

$$I_1 = -I_2$$

$$V_{in} - I_1 R_1 - V_1 = 0 \text{ and}$$

$$V_1 + I_2 R_2 - V_{out} = 0$$


Now,  $V_1 = 0$  since the op - amp has  $\infty$  gain (virtual earth assumption)

$$V_{in} = I_1 R_1 \text{ and } V_{out} = I_2 R_2 = -I_1 R_2$$

$$\text{So, } I_1 = -\frac{V_{out}}{R_2}$$

$$\text{Yielding, } V_{in} = -\frac{V_{out} R_1}{R_2} \quad \text{Voltage gain, } \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

## Non-Inverting Amplifier

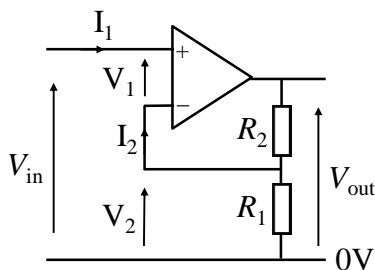

Now,  $I_1 = I_2 = 0$  since the input resistance of the op amp is  $\infty$ , so

$$V_2 = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{in} - V_1 - V_2 = 0$$


Now,  $V_1 = 0$  since the op - amp has  $\infty$  gain (virtual earth assumption)

$$V_2 = V_{in}$$

$$\text{So, } V_{in} = V_{out} \frac{R_1}{R_1 + R_2}$$

$$\text{Yielding, } \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} \quad \text{Voltage gain, } \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$


## Buffer Amplifier (Unity Gain)

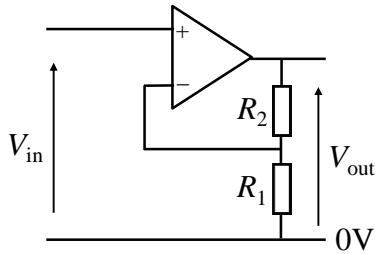

We know the voltage gain for the non-inverting amplifier is,



$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

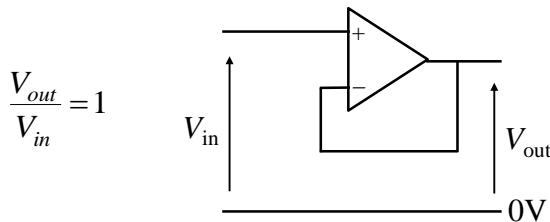Now, if we let  $R_2 = 0$  (a short circuit) and  $R_1 = \infty$  (open circuit) then


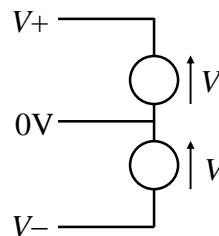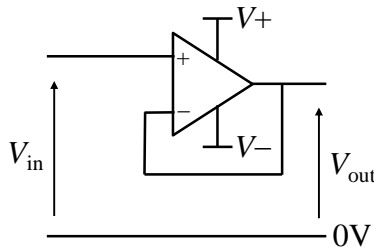
## Op-Amp Power Supplies

- Usually, op-amps use split power supplies, i.e., +ve and -ve power supply connections



- This permits input signals having both +ve and -ve excursions to be amplified
- This can be inconvenient for battery powered equipment. However, if the input signal is for e.g., always +ve, the  $V_-$  rail can be removed i.e., set to 0V

## Op-Amp Applications

- As mentioned, op-amps can be used in many other common analogue signal processing tasks, for example:
  - Filters: circuits that can manipulate the frequency content of signals
  - Mathematical functions, e.g., integrators and differentiators
  - Comparators and triggers, i.e., thresholding devices
- A 'cookbook' of useful such applications can be found in 'The Art of Electronics' by Horowitz and Hill