

# Digital Electronics: Sequential Logic

## Introduction, Latches and Flip-Flops

### Introduction


- The logic circuits discussed previously are known as *combinational*, in that the output depends only on the condition of the latest inputs
- However, we will now introduce a type of logic where the output depends not only on the latest inputs, but also on the condition of earlier inputs. These circuits are known as *sequential*, and implicitly they contain *memory* elements

## Memory Elements

- A memory stores data – usually one bit per element
- A snapshot of the memory is called the *state*
- A one bit memory is often called a *bistable*, i.e., it has 2 stable internal states
- *Flip-flops* and *latches* are particular implementations of bistables
 
## RS Latch


- An RS latch is a memory element with 2 inputs: Reset ( $R$ ) and Set ( $S$ ) and 2 outputs:  $Q$  and  $\bar{Q}$ .



$S$	$R$	$Q'$	$\bar{Q}'$	comment
0	0	$Q$	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	0	0	illegal

Where  $Q'$  is the next state and  $Q$  is the current state

## RS Latch - Operation

 

NOR truth table


$a$	$b$	$y$
0	0	1
0	1	0
1	0	0
1	1	0

$b$  complemented

always 0

- $R = 1$  and  $S = 0$ 
  - Gate 1 output in 'always 0' condition,  $Q = 0$
  - Gate 2 in 'complement' condition, so  $\bar{Q} = 1$
- This is the (R)eset condition

## RS Latch - Operation

 

NOR truth table


$a$	$b$	$y$
0	0	1
0	1	0
1	0	0
1	1	0

$b$  complemented

always 0

- $S = 0$  and  $R$  to 0
  - Gate 2 remains in 'complement' condition,  $\bar{Q} = 1$
  - Gate 1 into 'complement' condition,  $Q = 0$
- This is the hold condition

## RS Latch - Operation

 

NOR truth table


$a$	$b$	$y$
0	0	1
0	1	0
1	0	0
1	1	0

$b$  complemented

always 0

- $S = 1$  and  $R = 0$ 
  - Gate 1 into 'complement' condition,  $Q = 1$
  - Gate 2 in 'always 0' condition,  $\bar{Q} = 0$
- This is the (S)et condition

## RS Latch - Operation

 

NOR truth table

$a$	$b$	$y$
0	0	1
0	1	0
1	0	0
1	1	0

$b$  complemented

always 0

- $S = 1$  and  $R = 1$ 
  - Gate 1 in 'always 0' condition,  $Q = 0$
  - Gate 2 in 'always 0' condition,  $\bar{Q} = 0$
- This is the illegal condition

## RS Latch – State Transition Table

- A *state transition table* is an alternative way of viewing its operation

$Q$	$S$	$R$	$Q'$	comment
0	0	0	0	hold
0	0	1	0	reset
0	1	0	1	set
0	1	1	0	illegal
1	0	0	1	hold
1	0	1	0	reset
1	1	0	1	set
1	1	1	0	illegal

- A state transition table can also be expressed in the form of a *state diagram*

## RS Latch – State Diagram

- A *state diagram* in this case has 2 states, i.e.,  $Q=0$  and  $Q=1$
- The state diagram shows the input conditions required to transition between states. In this case we see that there are 4 possible transitions
- We will consider them in turn

## RS Latch – State Diagram

$Q$	$S$	$R$	$Q'$	comment
0	0	0	0	hold
0	0	1	0	reset
0	1	0	1	set
0	1	1	0	illegal
1	0	0	1	hold
1	0	1	0	reset
1	1	0	1	set
1	1	1	0	illegal

$$Q = 0 \quad Q' = 0$$

From the table we can see:

$$\bar{S}.\bar{R} + \bar{S}.R + S.R =$$

$$\bar{S}.\bar{R} + \bar{S}.R + S.R = \bar{S} + S.R =$$

$$(\bar{S} + S).\bar{R} + S.R = \bar{R} + S.R$$

$$Q = 1 \quad Q' = 1$$

From the table we can see:

$$\bar{S}.\bar{R} + S.\bar{R} = \bar{R}.\bar{S} + S.\bar{R} =$$

$$\bar{R}$$

## RS Latch – State Diagram

$Q$	$S$	$R$	$Q'$	comment
0	0	0	0	hold
0	0	1	0	reset
0	1	0	1	set
0	1	1	0	illegal
1	0	0	1	hold
1	0	1	0	reset
1	1	0	1	set
1	1	1	0	illegal

$$Q = 1 \quad Q' = 0$$

From the table we can see:

$$\bar{S}.R + S.R =$$

$$R.\bar{S} + S.R = R$$


$$Q = 0 \quad Q' = 1$$

From the table we can see:

$$S.\bar{R}$$
 
## RS Latch – State Diagram

- Which gives the following state diagram:



- A similar diagram can be constructed for the  $\bar{Q}$  output
- We will see later that state diagrams are a useful tool for designing sequential systems

## Clocks and Synchronous Circuits

- For the RS latch we have just described, we can see that the output state changes occur directly in response to changes in the inputs. This is called *asynchronous* operation
- However, virtually all sequential circuits currently employ the notion of *synchronous* operation, that is, the output of a sequential circuit is constrained to change only at a time specified by a global *enabling* signal. This signal is generally known as the system *clock*

## Clocks and Synchronous Circuits


- The Clock: What is it and what is it for?
  - Typically it is a square wave signal at a particular frequency
  - It imposes order on the state changes
  - Allows lots of states to appear to update simultaneously
- How can we modify an asynchronous circuit to act synchronously, i.e., in synchronism with a clock signal?

## Transparent D Latch

- We now modify the RS Latch such that its output state is only permitted to change when a valid enable signal (which could be the system clock) is present
- This is achieved by introducing a couple of AND gates in cascade with the R and S inputs that are controlled by an additional input known as the *enable* (EN) input.



## Transparent D Latch

 


- See from the AND truth table:
  - if one of the inputs, say  $a$  is 0, the output is always 0
  - Output follows  $b$  input if  $a$  is 1
- The complement function ensures that  $R$  and  $S$  can never be 1 at the same time, i.e., illegal avoided

AND truth table

$a$	$b$	$y$
0	0	0
0	1	0
1	0	0
1	1	1

## Transparent D Latch

 


$D$	$EN$	$Q'$	$\bar{Q}'$	comment
X	0	$Q$	$\bar{Q}$	RS hold
0	1	0	1	RS reset
1	1	1	0	RS set

- See  $Q$  follows  $D$  input provided  $EN=1$ .  
If  $EN=0$ ,  $Q$  maintains previous state

## Master-Slave Flip-Flops


- The transparent D latch is so called '*level*' triggered. We can see it exhibits transparent behaviour if  $EN=1$ . It is often more simple to design sequential circuits if the outputs change only on the either rising (positive going) or falling (negative going) '*edges*' of the clock (i.e., enable) signal
- We can achieve this kind of operation by combining 2 transparent D latches in a so called *Master-Slave* configuration

## Master-Slave D Flip-Flop

 

- To see how this works, we will use a timing diagram
- Note that both latch inputs are effectively connected to the clock signal (admittedly one is a complement of the other)

## Master-Slave D Flip-Flop

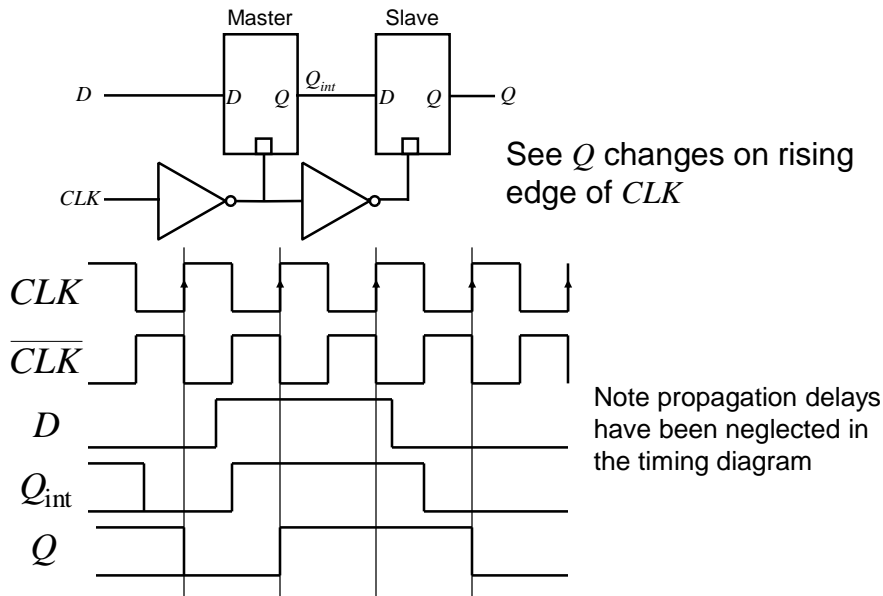

## D Flip-Flops

- The Master-Slave configuration has now been superseded by new F-F circuits which are easier to implement and have better performance
- When designing synchronous circuits it is best to use truly edge triggered F-F devices
- We will not consider the design of such F-Fs on this course

## Other Types of Flip-Flops

- Historically, other types of Flip-Flops have been important, e.g., J-K Flip-Flops and T-Flip-Flops
- However, J-K FFs are a lot more complex to build than D-types and so have fallen out of favour in modern designs, e.g., for field programmable gate arrays (FPGAs) and VLSI chips

## Other Types of Flip-Flops


- Consequently we will only consider synchronous circuit design using D-type FFs
- However for completeness we will briefly look at the truth table for J-K and T type FFs

## J-K Flip-Flop

- The J-K FF is similar in function to a clocked RS FF, but with the illegal state replaced with a new 'toggle' state

$J$	$K$	$Q'$	$\bar{Q}'$	comment
0	0	$Q$	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	$\bar{Q}$	$Q$	toggle

 Where  $Q'$  is the next state  
and  $Q$  is the current state




## T Flip-Flop

- This is essentially a J-K FF with its J and K inputs connected together and renamed as the T input

$T$	$Q'$	$\bar{Q}'$	comment
0	$Q$	$\bar{Q}$	hold
1	$\bar{Q}$	$Q$	toggle

 Where  $Q'$  is the next state  
and  $Q$  is the current state




## Asynchronous Inputs

- It is common for the FF types we have mentioned to also have additional so called 'asynchronous' inputs
- They are called asynchronous since they take effect independently of any clock or enable inputs
- Reset/Clear – force  $Q$  to 0
- Preset/Set – force  $Q$  to 1
- Often used to force a synchronous circuit into a known state, say at start-up.

## Timing

- Various timings must be satisfied if a FF is to operate properly:
  - *Setup time*: Is the minimum duration that the data must be stable at the input before the clock edge
  - *Hold time*: Is the minimum duration that the data must remain stable on the FF input after the clock edge

## Timing

 

$t_{su}$  Set-up time

$t_h$  Hold time

$t_p$  Propagation delay