

# 1994 Paper 13 Question 1

## Digital Electronics and Computer Design

Write about 300 words about the purpose of and prospects for asynchronous logic systems. [15 marks]

Distinguish speed-independent and self-timed circuits from conventional asynchronous circuits. [5 marks]