

1996 Paper 9 Question 1

VLSI

Give the transistor schematic and stick diagram for

- (a) a static CMOS 2-input NOR gate [4 marks]
- (b) a static CMOS 3-input NAND gate [6 marks]
- (c) a 3-bit barrel shifter [10 marks]