

1998 Paper 2 Question 3

Digital Electronics

You are to design a circuit with the following inputs:

- D – the data input
- R – a reset input (active high)
- CLK – a clock

and one output, ERR .

ERR should be high if an error is found. An error occurs if, since the last reset, in the sequence of D values which occur on the rising edge of the clock the number of zeros exceeds the number of ones by three, or *vice versa*. R should be sampled on the rising edge of the clock. When R is asserted, the D value is ignored.

(a) Give a state diagram for the circuit. [10 marks]

(b) Implement the circuit using J-K flip flops. [10 marks]