

## 2001 Paper 10 Question 1

### Digital Electronics

- (a) Give the truth table for the exclusive or (XOR) of two boolean variables. [2 marks]
- (b) Express XOR in disjunctive normal form. [3 marks]
- (c) XOR gates are sometimes called *half-adders*. Show how two XOR gates can be used to find the low-order bit of the sum of three one-bit numbers. [3 marks]
- (d) If the XOR gates in part (c) were composed of gates corresponding to the expression in part (b), what would the delay of the circuit be? (Assume that inverters, OR gates and AND gates have a delay  $\tau$ .) [4 marks]
- (e) Give the transistor level circuit diagram for a CMOS NOR gate and explain its operation. [4 marks]
- (f) Give a transistor level circuit diagram for a CMOS XOR gate. [4 marks]