

2002 Paper 9 Question 12

Specification and Verification II

The multiplexer MUX, register REG c (where c is the initial value) and combinational unit COM f (where f is the function computed) are defined to have the behaviour given below.

$$\begin{aligned}\text{MUX}(sw, i1, i2, o) &= \forall t. o\ t = \text{if } sw\ t \text{ then } i1\ t \text{ else } i2\ t \\ \text{REG } c\ (i, o) &= (o\ 0 = c) \wedge \forall t. o(t+1) = i\ t \\ \text{COM } f\ (i, o) &= \forall t. o\ t = f(i\ t)\end{aligned}$$

Using only instances of MUX, REG c and COM f design a device DEV(c, f) that satisfies

$$\begin{aligned}\text{DEV}(c, f)(\text{reset}, i, o) &= \\ (o\ 0 = c) \wedge \forall t. o(t+1) &= \text{if } \text{reset}(t+1) \text{ then } c \text{ else } f(o\ t)\end{aligned}$$

[8 marks]

Prove that your design meets this specification.

[12 marks]