

2002 Paper 9 Question 2

VLSI Design

Write brief notes (including circuit diagrams if appropriate) on the following schemes for carry propagation in binary addition:

- (a) ripple carry;
- (b) Manchester carry;
- (c) carry look-ahead tree;
- (d) carry skip;
- (e) carry select.

[4 marks each]