

2003 Paper 10 Question 1

Digital Electronics

- (a) An n -bit decoder is a combinational circuit with n inputs and 2^n outputs. For each possible assignment of values to inputs there is a corresponding output which is set to “1” when and only when that assignment is made to the inputs. Give a design for a 3-bit decoder. [4 marks]
- (b) Ignoring inverters, how many gates are required for your design? How many are required for an n -bit decoder? [2 marks]
- (c) An n -bit priority encoder has $2^n - 1$ inputs and n outputs. The inputs $x_1, x_2 \dots x_{2^n-1}$ are ordered in priority with x_j having higher priority than x_i if $j > i$. The outputs $a_{n-1}, a_{n-2} \dots a_0$, interpreted as an unsigned integer, denote the highest priority input asserted high. Give a design for a 3-bit priority encoder. [6 marks]
- (d) Give *two* designs for a combinational circuit which has K ordered inputs and K corresponding outputs where the only output asserted (if any) is the one corresponding to the asserted input with the highest priority. [6 marks]
- (e) Which design is better, and why? [2 marks]