

## 2005 Paper 10 Question 1

### Digital Electronics

- (a) What is a *minimum sum-of-products*? [3 marks]
- (b) A full adder has data inputs ( $A_0, B_0$ ) and a carry input ( $C_0$ ). The sum ( $S_0$ ) and carry ( $C_1$ ) are output. What are the minimum sum-of-products equations for  $S_0$  and  $C_1$ ? [6 marks]
- (c) How could the gate count for the implementation of output  $S_0$  be reduced using XOR gates? [2 marks]
- (d) For a 3-bit full adder (i.e. one which has three A inputs ( $A_0, A_1, A_2$ ), three B inputs ( $B_0, B_1, B_2$ ) and three sum outputs ( $S_0, S_1, S_2$ )), the final carry output is  $C_3$ . What is the sum-of-products equation for  $C_3$  in terms of the A and B inputs? [6 marks]
- (e) If we were to implement an 8-bit full adder, why would we look for a multi-level logic implementation for the carry output ( $C_8$ )? [3 marks]