

COMPUTER SCIENCE TRIPOS Part IA – 2017 – Paper 2

1 Digital Electronics (IJW)

(a) Briefly describe the main feature of a combinational logic block. [2 marks]

(b) Use Boolean algebra to simplify the following expression

$$W = A.\bar{B}.C.\bar{D}.E + A.C.D + A.C.\bar{F}.G.\bar{H} + A.B.C.\bar{D}.E + A.C.D.\bar{E} + \bar{E}.\bar{H}$$

in sum of products form.

Hint: $X.Y + \bar{X}.Z = X.Y + \bar{X}.Z + Y.Z$ [4 marks]

(c) A 2-bit binary adder sums two numbers, A_1A_0 and B_1B_0 to yield the unsigned result $Y_2Y_1Y_0$, where the zero subscript indicates the least significant bit (LSB).

(i) Write down the truth table for the required outputs Y_2 , Y_1 and Y_0 .

(ii) Using a Karnaugh map (K map) or otherwise, give the simplified sum of products expression for Y_2 .

(iii) Using a K map or otherwise, determine a simplified product of sums expression for Y_2 and show how the circuit can be implemented using only NOR gates (of any number of inputs).

[7 marks]

(d) Simplify the following four variable function $F(A, B, C, D)$ using the Quine-McCluskey (Q-M) method:

Minterms: $\bar{A}.\bar{B}.\bar{C}.\bar{D}$, $\bar{A}.\bar{B}.C.D$, $\bar{A}.B.\bar{C}.D$, $\bar{A}.B.C.D$, $A.\bar{B}.\bar{C}.\bar{D}$, $A.\bar{B}.C.\bar{D}$

Don't cares: $\bar{A}.\bar{B}.\bar{C}.D$, $A.\bar{B}.\bar{C}.D$, $A.B.C.D$ [7 marks]