

COMPUTER SCIENCE TRIPOS Part IA – 2023 – Paper 2

1 Digital Electronics (ijw24)

- (a) Simplify the following Boolean function into both sum of products and product of sums forms, taking into account the don't care terms $A.B$ and $A.C$

$$F(A, B, C, D) = \overline{A}.B.\overline{C} + A.\overline{B}.\overline{C} + \overline{A}.\overline{B}.D + \overline{A}.C.\overline{D}$$


[5 marks]

- (b) Using a Karnaugh Map, simplify the following Boolean function into sum of products form

$$G(A, B, C, D) = (\overline{A} + \overline{B} + C).(B + C + \overline{D}).(A + \overline{B} + D).(\overline{A} + B + \overline{D}).(\overline{B} + C + D)$$

[3 marks]

 - (c) For the following circuit, assume that all the logic gates have an equal value of *non-zero* propagation delay and that $X = 0$ and $Y = 0$



- (i) With the aid of a timing diagram, show that a static hazard is present at output P when input Z changes from 0 to 1.
- (ii) With the assistance of a Karnaugh Map, show how the static hazard identified in Part (c)(i) can be eliminated.

[7 marks]

- (d) (i) Show how the following Boolean function may be implemented using an 8:1 multiplexer. Use variable X as the most significant bit of the multiplexer selector inputs

$$M(X, Y, Z) = \overline{X}.\overline{Y}.Z + \overline{X}.Y.Z + X.\overline{Y}.\overline{Z} + X.\overline{Y}.Z$$

- (ii) Show how the function in Part (d)(i) may alternatively be implemented using a 2:1 multiplexer and a NOT gate. Assume that complemented input variables are *not* available.

[5 marks]