

Limitations of the Method


- Formal proof can't guarantee actual chips will work:
 - design models are not always accurate
 - there may be fabrication defects
- Specifications may not capture requirements:
 - large specifications may be unreadable
 - some input conditions may be ignored

Modelling Hardware in Higher Order Logic

Original slides by Tom Melham and Michael Norrish
(edited by Mike Gordon)

Why Formal Specification?

 Consider this device (J. Herbert's example):



This can be specified *informally* by


The input line *datain* accepts a stream of bits, and the output line *dataout* emits the same stream delayed by four cycles. The bus *out* is four bits wide. If the input *sample* is false then the 4-bit word at *out* is the last four bits input at *datain*. Otherwise, the output word is all zeros.

Hardware Verification Method

- Classical method of hardware verification:
 1. write a specification of intended behaviour
Spec
 2. write specifications of the design components
Part-1, ... Part-*n*
 3. define a formal model of the design
 $\vdash \text{Design} = \text{Part-1} + \dots + \text{Part-}n$
 4. formulate and prove correctness
 $\vdash \text{Design satisfies Spec}$
- This general verification approach
 - underlies various specific formal methods
 - requires mechanized support for large designs
 - is usually applied hierarchically


Specification Examples

- Simple combinational behaviour:

 

$$\vdash \text{Xor}(i_1, i_2, o) = (o = \neg(i_1 = i_2))$$

- Bidirectional wires:

 

$$\vdash \text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$


Why Formal Specification?

The informal specification is

- vague: does ‘the last four bits input’ include the current bit?
- incomplete: what is the value at *dataout* during the first three cycles?
- unusable: a natural language specification can’t be simulated or compiled!

Specification Examples

Sequential (time-dependent) behaviour:

 


$$\vdash \text{Dtype}(ck, d, q) = \forall t. q(t+1) = (\text{if Rise } ck \ t \ \text{then } d \ t \ \text{else } q \ t)$$

$$\vdash \text{Rise } ck \ t = \neg ck(t) \wedge ck(t+1)$$

Formal Specification in HOL

- Consider the following device:

 


This is specified by a boolean term $S[a, b, c, d]$ with free variables $a, b, c,$ and d .

- The idea is that


- a, b, c, d model externally-observable values
- $S[a, b, c, d] = \begin{cases} \text{T} & \text{if } a, b, c, \text{ and } d \text{ could occur} \\ & \text{simultaneously on the} \\ & \text{corresponding external wires of the} \\ & \text{device Dev} \\ \text{F} & \text{otherwise} \end{cases}$

Composing Behaviours

- Consider the following two devices:

 

 - Logical conjunction (\wedge) models the effect of connecting components together:




Specification of the Sampler

- We can specify the sampler formally by


$\forall t: \text{time.}$
 $(\text{dataout}(t) = \text{datain}(t-4))$
 \wedge
 $(\text{out}(t) = \text{if } \text{sample}(t)$
 then [F; F; F; F]
 else [datain(t-4); datain(t-3);
 datain(t-2); datain(t-1)]])

Hiding Internal Structure

- Consider the composite device

 

 - Existential quantification (\exists) models the effect of making wires internal to the design:



- Existential quantification is called a *hiding* operator—it ‘hides’ internal wires.

Specification of the Sampler

- We can specify the sampler formally by

$\forall t: \text{time.}$
 $(\text{dataout}(t) = \text{datain}(t-4))$
 \wedge
 $(\text{out}(t) = \text{if } \text{sample}(t)$
 then [F; F; F; F]
 else [datain(t-4); datain(t-3);
 datain(t-2); datain(t-1)]])

- The formal specification is
 - precise: ‘last four bits input’ doesn’t include current bit
 - complete: can infer that *dataout* equals *datain*(0) during the first three cycles.
 - usable: logic notation can be processed by machine

Hierarchical Verification

The hierarchical verification method:


Level 0

Model:

$$\vdash M = \exists z. S_1 \wedge S_2$$

Correctness:

$$\vdash M \underset{F}{\text{sat}} S$$

 

Level 1

Models:


$$\vdash M_1 = \exists x. P_1 \wedge P_2$$

$$\vdash M_2 = \exists y. P_3 \wedge P_4$$

Correctness:

$$\vdash M_1 \underset{G}{\text{sat}} S_1$$
 
$$\vdash M_2 \underset{G}{\text{sat}} S_2$$



Shallow embedding of Verilog

- Some typical structural Verilog

```
module COMP (p1, ..., pm);
  wire w1, ..., wn;
```

```
  COMP1 M1 (...);
```

```
  COMP2 M2 (...);
```

```
endmodule
```

- Assume formulas for COMP1, COMP2 already defined

- Logical representation:

$$\text{COMP}(p1, \dots, pm) = \exists w1 \dots wn. \text{COMP1}(\dots) \wedge \text{COMP2}(\dots)$$

Hierarchical Design—Advantages

- Each type of module verified only once
 - the statement of its correctness will be reused many times
- Controls complexity through abstraction
 - each verification is done at the appropriate level of complexity

Formulating Correctness

- A key part of formal hardware verification is formalizing what ‘correctness’ *means*.
- The strongest formulation is *equivalence*:

$$\vdash \forall v_1 \dots v_n. M[v_1, \dots, v_n] = S[v_1, \dots, v_n]$$

- For *partial* specifications, use *implication*:

$$\vdash \forall v_1 \dots v_n. M[v_1, \dots, v_n] \Rightarrow S[v_1, \dots, v_n]$$

- In general, the satisfaction relationship

$$\vdash M[v_1, \dots, v_n] \underset{abs}{\text{sat}} S[abs(v_1), \dots, abs(v_n)]$$


must be one of *abstraction*. The specification will be an abstraction of the design model. Various kinds of abstractions on signals (*abs*) will be discussed later.

Design Model and Correctness

- We define the design model using composition and hiding, as follows:

$$\vdash \text{Inv}(i, o) =$$
 
$$\exists g p. \text{Pwr } p \wedge \text{Gnd } g \wedge \\ \text{Ntran}(i, g, o) \wedge \text{Ptran}(i, p, o)$$




- Correctness is formulated by the equivalence:

$$\vdash \forall i o. \text{Inv}(i, o) = (o = \neg i)$$

This follows by purely logical inference...

A Simple Correctness Proof

 - Here is the design of a CMOS inverter:
- Suppose we wish to verify that $o = \neg i$.
- There are three steps:
 - define a model of the circuit in logic
 - formulate the correctness of the circuit
 - prove the correctness of the circuit



The Correctness Proof

- Definition of Inv:

$$\vdash \text{Inv}(i, o) =$$

$$\exists g p. \text{Pwr } p \wedge \text{Gnd } g \wedge \\ \text{Ntran}(i, g, o) \wedge \text{Ptran}(i, p, o)$$

- Expanding with definitions:

$$\vdash \text{Inv}(i, o) =$$

$$\exists g p. (p = \mathbf{T}) \wedge (g = \mathbf{F}) \wedge \\ (i \Rightarrow (o = g)) \wedge (\neg i \Rightarrow (o = p))$$

- By simple logical reasoning:

$$\vdash \text{Inv}(i, o) = (i \Rightarrow (o = \mathbf{F})) \wedge (\neg i \Rightarrow (o = \mathbf{T}))$$

CMOS Primitives

- Formal specifications of primitives:

$$\begin{array}{c} g \\ | \\ \text{---} \text{---} \text{---} \\ | \\ s \text{---} \text{---} \text{---} d \end{array} \vdash \text{Ptran}(g, s, d) = (\neg g \Rightarrow (d = s))$$

$$\begin{array}{c} g \\ | \\ \text{---} \text{---} \text{---} \\ | \\ s \text{---} \text{---} \text{---} d \end{array} \vdash \text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$


$$\begin{array}{c} g \\ | \\ \text{---} \\ | \\ \text{---} \end{array} \vdash \text{Gnd } g = (g = \mathbf{F})$$

$$\begin{array}{c} \text{---} \\ | \\ p \end{array} \vdash \text{Pwr } p = (p = \mathbf{T})$$

- This is the so-called *switch model* of CMOS.

Another Example

- An $(n+1)$ -bit ripple-carry adder:

 

- We wish to prove that:

$$(2^{n+1} \times \text{cout}) + s = a + b + \text{cin}$$

- There are, as usual, three steps:
 - define a model of the circuit in logic
 - formulate the correctness of the circuit
 - prove the correctness of the circuit

The Correctness Proof continued

- Simplifying gives:

$$\vdash \text{Inv}(i, o) = (i \Rightarrow \neg o) \wedge (\neg i \Rightarrow o)$$

- By the law of the contrapositive:

$$\vdash \text{Inv}(i, o) = (o \Rightarrow \neg i) \wedge (\neg i \Rightarrow o)$$

- By the definition of boolean equality:

$$\vdash \text{Inv}(i, o) = (o = \neg i)$$

- Generalizing the free variables gives:

$$\vdash \forall i o. \text{Inv}(i, o) = (o = \neg i)$$

Defining the Model: types

- Specification uses numbers, i.e. values of type *num*
- Implementation uses words – values of type *word*
 - n^{th} bit of w denoted by $w[n]$
 - $w[m : n]$ denotes bits m to n of w
 - $\text{Bv}(b)$ is the number represented by bit b
 - $\text{V}(w)$ is the natural number represented by word w
- Abstraction from words to numbers (data abstraction):

$$\vdash \text{Bv } b \quad = \text{ if } b \text{ then } 1 \text{ else } 0$$

$$\vdash \text{V } w[0 : 0] \quad = \text{Bv } w[0]$$


$$\vdash \text{V } w[n+1 : 0] \quad = 2^{n+1}(\text{Bv } w[n+1]) + \text{V } w[n : 0]$$

Scope of the Method

- The inverter example is, of course, trivial!
- But the same method has been applied to
 - a commercial CMOS cell library
 - several complete microprocessors (e.g. ARM)
 - floating point algorithms and hardware
- Features of the approach:
 - the specification language is just logic
 - * *logic can mimic HDL constructs*
 - the rules of reasoning are also pure logic
 - * *special-purpose derived rules are possible*
 - big formal proofs require machine assistance

Defining the Model

- Recursive view of an $n+1$ -bit adder:

 


- Primitive recursive definition in logic:

$$\text{AdderImp}(0)(a, b, cin, s, cout) = \text{Add1}(a[0], b[0], cin, s[0], cout)$$

$$\begin{aligned} \text{AdderImp } n (a, b, cin, s, cout) = \\ \exists c. \text{Add1}(a[n], b[n], c, s[n], cout) \wedge \\ \text{AdderImp}(n-1)(a[n-1:0], b[n-1:0], cin, s[n-1:0], c) \end{aligned}$$

Defining the Model: recursive definition

 - If $n > 0$ an $(n+1)$ -bit adder is built from an n -bit adder



Formulation of Correctness

- Logical formulation of correctness:

$$\text{Spec } n (a, b, cin, s, cout) = ((2^{n+1} \text{ cout}) + s = a + b + cin)$$

$$\forall n \ a \ b \ cin \ s \ cout.$$

$$\text{AdderImp } n (a, b, cin, s, cout)$$


\Rightarrow

$$\text{Spec } n (\forall a[n:0], \forall b[n:0], \forall cin, \forall s[n:0], \forall cout)$$

- Note the data abstraction (*abs* in an earlier slide)
- This is easy to prove (done later in the course)

Defining the Model: Add1

- Diagram of a 1-bit full adder:

 

- Lines a , b , cin , sum and $cout$ carry boolean values
- Specification (note data abstraction from *bool* to *num*):

$$\begin{aligned} \text{Add1}(a, b, cin, sum, cout) = \\ (2 \times \text{Bv}(cout) + \text{Bv}(sum) = \text{Bv}(a) + \text{Bv}(b) + \text{Bv}(cin)) \end{aligned}$$

Formulating Correctness

- Then correctness is stated by:


$$\begin{aligned} \vdash \forall ck. \text{Inf}(\text{Rise } ck) \Rightarrow \\ \forall d q. \text{Dtype}(ck, d, q) \Rightarrow \\ \text{Del}(d \text{ when } (\text{Rise } ck), q \text{ when } (\text{Rise } ck)) \end{aligned}$$

- Note the formal *validity condition*:

$$\vdash \text{Inf } P = \forall t. \exists t'. t' > t \wedge P t'$$

Temporal Abstraction

- Example—abstracting to unit delay:

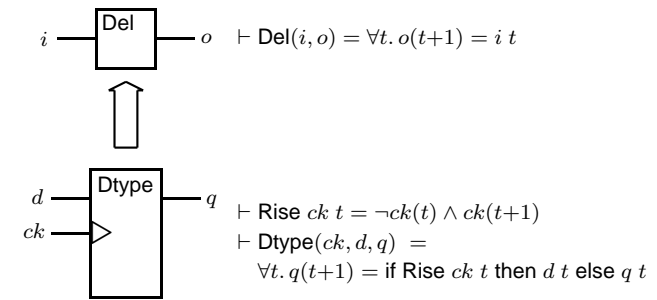

- Notions of time involved:


- coarse grain of time—unit time = 1 clock cycle
- fine grain of time—unit time \approx 1 gate delay

Industry use of theorem proving

- Intel
 - floating point algorithms (uses HOL Light system)
 - hardware (uses internal tools Forte/reFL^{ect})
- AMD
 - floating point (uses ACL2 prover)
- Sun
 - high level architecture verification (PVS)
- Rockwell Collins
 - low level code verification (ACL2)
-
- Use of model checking widespread
 - discussed in latter part of the course

Formulating Correctness

- A mapping between time-scales:

 

- Define the temporal abstraction functions:

$$\begin{aligned} \vdash \text{Timeof } P n &= \text{the time on } t_c \text{ such that } P \text{ true for } n\text{th time} \\ \vdash \text{signal when } P &= \text{signal} \circ (\text{Timeof } P) \\ \text{where } (f \circ g)x &= f(g x) \quad [\circ \text{ is function composition}] \end{aligned}$$

Summary

- Specifying behaviour:
 - predicates— $S[a, b, c, d]$
- Specifying structure:
 - composition— $S_1[a, x] \wedge S_2[x, b]$
 - hiding— $\exists x. S_1[a, x] \wedge S_2[x, b]$
- Formulating correctness:
 - $\vdash \forall v_1 \dots v_n. M[v_1, \dots, v_n] = S[v_1, \dots, v_n]$
 - $\vdash \forall v_1 \dots v_n. M[v_1, \dots, v_n] \Rightarrow S[v_1, \dots, v_n]$
 - $\vdash \forall v_1 \dots v_n. M[v_1, \dots, v_n] \Rightarrow S[abs\ v_1, \dots, abs\ v_n]$
- Abstraction
 - data: $w \mapsto V(w)$
 - temporal: $sig \mapsto sig\ when\ (Rise\ clk)$