1994 Paper 1 Question 3

Self-timed logic circuits may enable an existing technology to achieve higher performance. Explain the principle of self-timed circuits.   [8 marks]

Comment on the possible opportunities for improved performance.   [6 marks]

Is it likely that large logic systems will become easier to design using self-timed logic rather than more traditional arrangements? Explain.   [6 marks]