1993 Paper 1 Question 2

Design a *divide-by-three* counter using T-type flipflops.